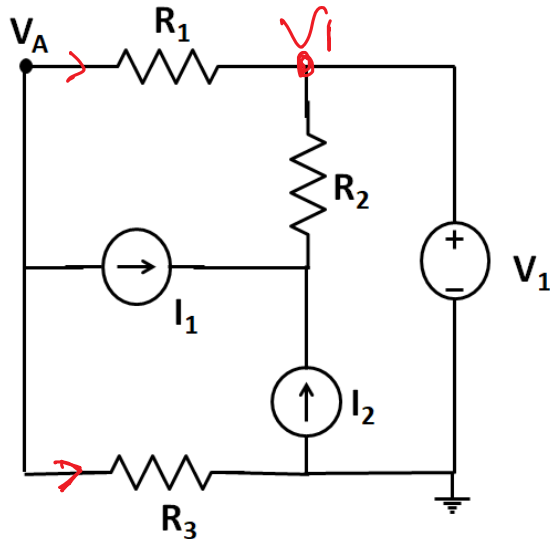


Solutions

10 January 2022 14:43

In the following circuit, find the node voltage V_A (in Volt). Given $R_1 = 8 \Omega$, $R_2 = 7 \Omega$, $R_3 = 8 \Omega$, $V_1 = 9 \text{ V}$, $I_1 = 6 \text{ A}$, $I_2 = 6 \text{ A}$.

From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>



Nodal Analysis at node V_A

$$\frac{V_A - V_1}{R_1} + I_1 + \frac{V_A - 0}{R_3} = 0$$

$$\frac{V_A - 9}{8} + 6 + \frac{V_A}{8} = 0$$


$$\text{or, } V_A - 9 + 48 + V_A = 0$$

$$\text{or, } 2V_A = -39$$

$$V_A = -19.5 \text{ V}$$

In the following circuit, find the voltage V_0 (in Volt) across the resistor R_L . Given $R_1 = 6 \text{ k}\Omega$, $R_2 = 8 \text{ k}\Omega$, $R_3 = 7 \text{ k}\Omega$, $R_L = 7 \text{ k}\Omega$, $V_1 = 9 \text{ V}$, $V_2 = 10 \text{ V}$.

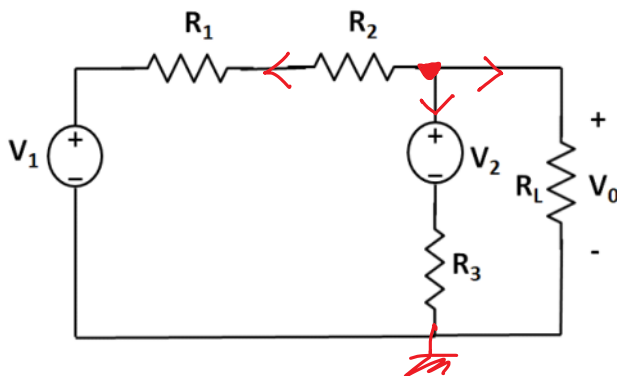From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>



$$\frac{V_0 - V_1}{R_1 + R_2} + \frac{V_0 - V_2}{R_3} + \frac{V_0}{R_L} = 0$$

$$\frac{V_0 - 9}{6 + 8} + \frac{V_0 - 10}{7} + \frac{V_0}{7} = 0$$


$$\text{or, } V_0 - 9 + 2V_0 - 20 + 2V_0 = 0$$

$$\text{or, } 5V_o = 29$$

$$V_o = 5.8V$$

In the following circuit, find the voltage V_2 (in Volt) across the resistor R_2 . Given $R_1 = 7 \Omega$, $R_2 = 6 \Omega$, $R_3 = 6 \Omega$, $R_4 = 6 \Omega$, $I_1 = 6 \text{ A}$, $V_1 = 6 \text{ V}$.

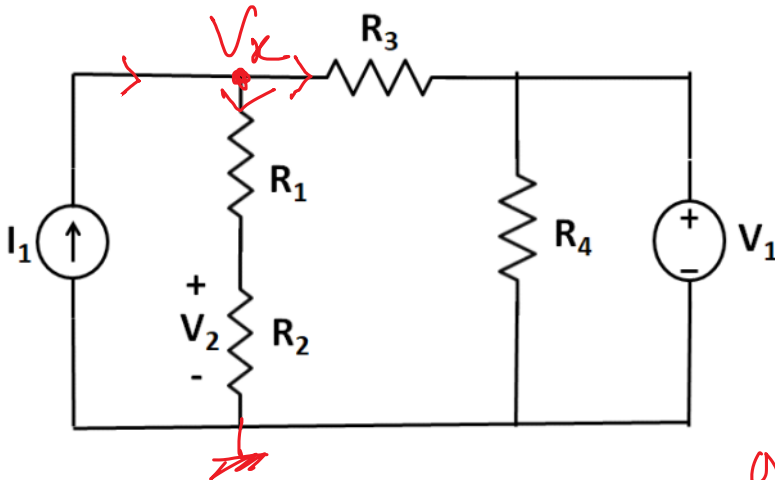From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>



$$\frac{V_x}{R_1 + R_2} + \frac{V_x - V_1}{R_3} - I_1 = 0$$

$$\frac{V_x}{7+6} + \frac{V_x - 6}{6} - 6 = 0$$

$$\text{or, } \frac{V_x}{13} + \frac{V_x - 6}{6} - 6 = 0$$

$$\text{or, } 6V_x + 13V_x - 78 - 468 = 0$$

$$\text{or, } 19V_x = 546$$

$$V_x = 28.7368 \text{ V}$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_x = 28.7368 \times \frac{6}{6+7} = 13.263 \text{ V}$$

The charge flowing through a conductor is given by $q = 47t \sin(4\pi t)$ mC in 0.5 s. Calculate the current (in mA) flowing through the conductor at $t = 0.5 \text{ s}$.

From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>

$$i = \frac{dq}{dt} = \frac{d}{dt} (47t \sin(4\pi t))$$

$$= 47 \sin(4\pi t) + 47 t (4\pi) \cos(4\pi t)$$

$$i|_{t=0.5s} = 0 + 47 (0.5) (4\pi) \cos(2\pi) \\ = 295.16 \text{ mA} \quad (\text{considering } \pi = 3.14)$$

Consider three resistors each having a resistance of 114Ω . Let R_S be the equivalent resistance when the resistances are connected in series. Similarly, R_P be the equivalent resistance when the resistances are connected in parallel. The ratio R_S/R_P is equal to _____.

From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>

Ratio 9,


3 parallel resistor resistance $R/3$

3 series " " $3R$

$$\frac{R_S}{R_P} = \frac{3R}{R/3} = 9$$

A voltage source $V_S = 7.9 \text{ V}$, and two resistors $R_1 = 5.3 \Omega$ and R_L (in Ω) are connected in series to form a circuit. The maximum power (in Watt) that can be transferred to the load resistor R_L is Answer

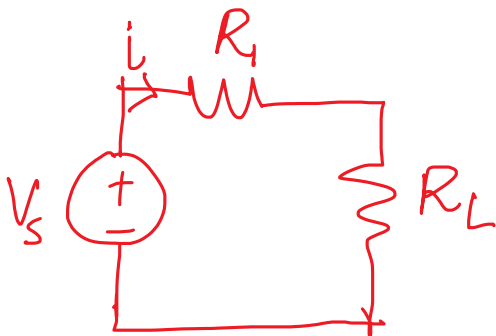From <<https://lms.bennett.edu.in/mod/quiz/review.php?attempt=217221>>



$$i = \frac{V_S}{R_1 + R_L}$$

For maximum power transfer
 $R_1 = R_L$

$$i = \frac{V_S}{2R_1}$$

$$\begin{aligned}
 & 2K_1 \\
 \text{Power dissipated by } R_L &= i^2 R_L \\
 &= \frac{V_s^2}{4R_1^2} R_1 \\
 &= \frac{V_s^2}{4R_1} = \frac{7.9^2}{4 \times 5.3} \\
 &= 2.9438 \text{ mW}
 \end{aligned}$$