

DO NOT WRITE ANYTHING ON QUESTION PAPER EXCEPT YOUR NAME, DEPARTMENT AND ENROLMENT No.

Name of Student ----- Enrolment No. -----

Department / School -----

**BENNETT UNIVERSITY, GREATER NOIDA**  
**End Term Examination, Fall SEMESTER 2019-20**

COURSE CODE: EECE105L

MAX. DURATION: **2 Hours**

COURSE NAME: Fundamentals of Electrical and Electronics Engg.

MAX. MARKS: **40**

**Note : Attempt all the questions. Each question carries 5 marks.**

**Q.1** Find out peak to peak value, average value and RMS value over one period of the waveform shown in Fig. 1. [1+2+2]

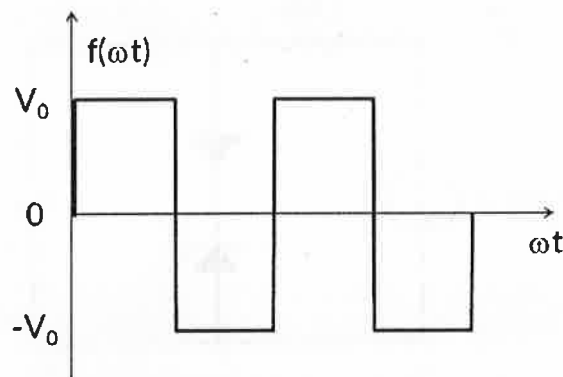


Fig. 1

**Q.2** In Fig. 2, The output of the RC filter is taken between nodes C and D. Find out the transfer function and identify the filter type with proper logic. Also find out the cut-off frequency of the filter. [2+1+2]

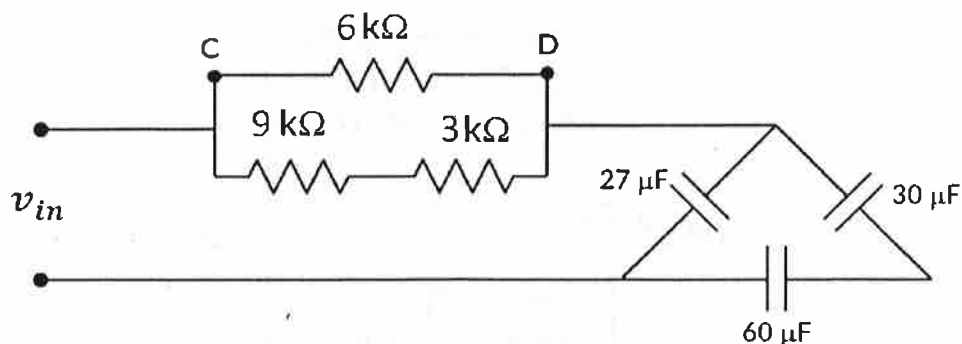


Fig. 2

**Q.3** In Fig. 3, the input voltage varies from 30 V to 50 V. The diodes are made of silicon and Zener breakdown voltage is 5 V. Find out the maximum and minimum current flowing through the Zener diode.

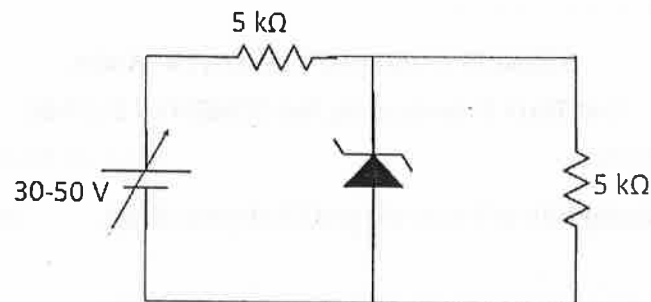


Fig. 3

**Q.4** In Fig. 4, draw the equivalent circuits in positive and negative halves. Also draw the output waveform ( $v_{out}$ ). The diodes are made of silicon and the Zener breakdown voltage is 5 V.

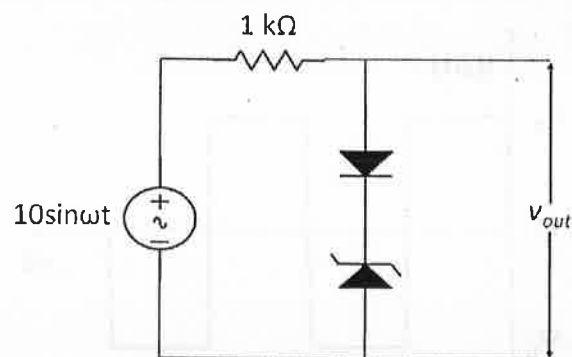


Fig. 4

**Q.5** Using mesh analysis method find out the current through 30 Ω, 40 Ω and 60 Ω resistors in Fig. 5.

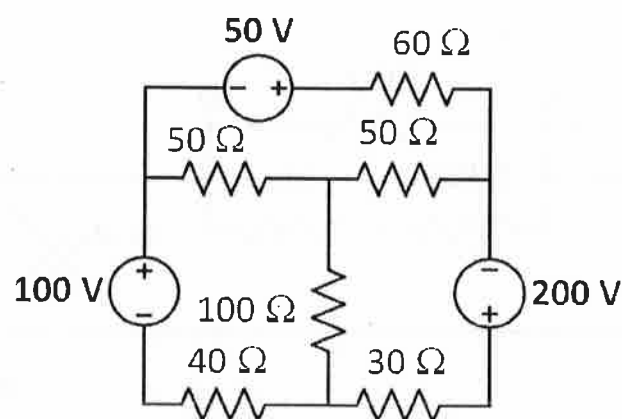


Fig. 5

**Q.6** In Fig. 6, for the given input draw the output voltage across the load resistor  $R_L$  with equivalent circuits for positive and negative halves. Consider the diode is made of silicon.

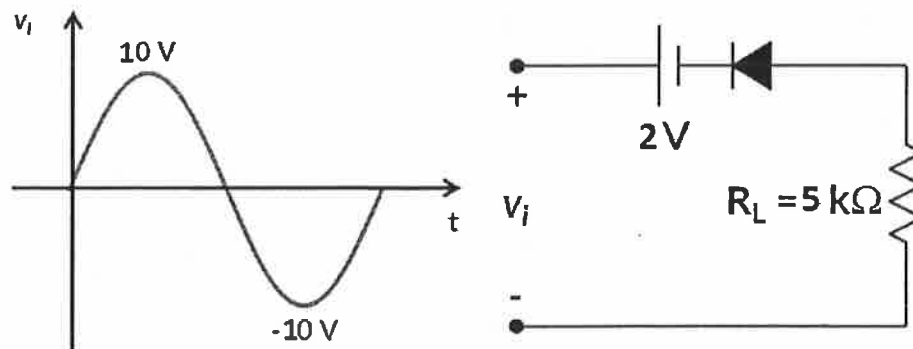


Fig. 6

**Q.7** In Fig. 7, using Norton's Theorem find out the current through the load resistor  $10 \Omega$ .

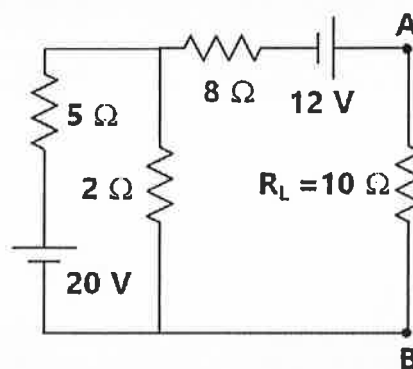


Fig. 7

**Q.8** Convert  $(D68C.4B6)_{16}$  into octal. Realize AND gate, OR gate and Inverter using only NOR Gates. [2+3]

---

