

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24 > EECE105L-Odd 2020 > 25 December - 31 December > Quiz 6

**Started on** Friday, 19 February 2021, 7:04 PM

**State** Finished

**Completed on** Friday, 19 February 2021, 7:34 PM

**Time taken** 30 mins

**Grade** 2.00 out of 5.00 (40%)

### Question 1

Incorrect

Mark 0.00 out of  
1.00

Calculate the current (in mA) flowing through a PN junction diode when voltage across diode is 0.68 Volts. Given the reverse saturation current is  $84 \times 10^{-15}$  A and the non-ideality factor as 1. Assume that the diode is working at 300K.

Constants that may require during calculations: The Boltzmann constant  $(k) = 1.38 \times 10^{-23} \text{ JK}^{-1}$ , charge  $(q) = 1.6 \times 10^{-19} \text{ C}$ .

Select one:

- ☐ 21.869
- ☐ 57.527
- ☒ 38.351 ✖
- ☐ 9.588

Your answer is incorrect.

The correct answer is: 21.869


**Question 2**

Correct

Mark 2.00 out of

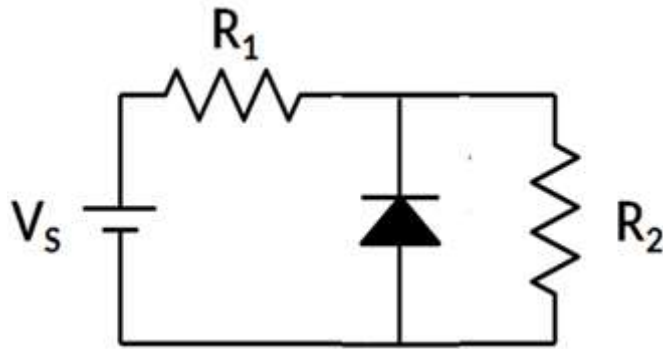2.00

The silicon diodes shown in the circuit have a reverse saturation current of 1 nA. Given that the cut-in voltage of the diode is 0.7 V. The supply voltage is  $V_s = 10$  Volt. Find the voltage (in Volt) across resistor  $R_2$  when  $R_1 = 8.4$  k $\Omega$  and  $R_2 = 3.1$  k $\Omega$ . Assume that the circuit is operating at 300 K.



Select one:

- ☐ 0.7
- ☒ 2.696 ✓
- ☐ 7.304
- ☐ -10.000

Your answer is correct.

The correct answer is: 2.696


**Question 3**

Incorrect

Mark 0.00 out of

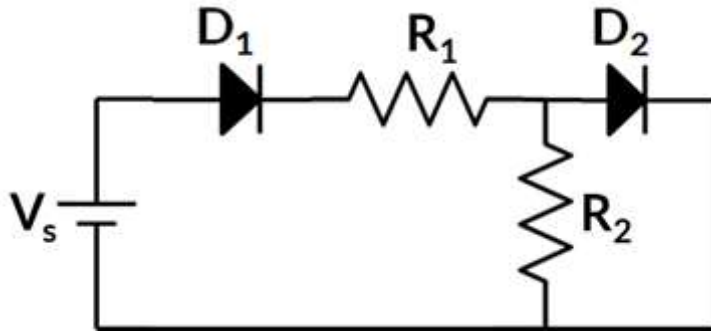2.00

Silicon diodes  $D_1$  and  $D_2$  are having a reverse saturation current of 16 nA. Find the value of  $R_2$  (in k $\Omega$ ) so that 6.1 mA current flows through  $R_2$  when source voltage  $V_s = 6$  Volt and  $R_1 = 3.8$  k $\Omega$ . The cut-in voltage of the diode is 0.7 V and the diode is operating at 300 K.



Select one:

- ☐ 1.395
- ☐ 0.754
- ☒ 0.869 ✖
- ☐ 0.115

Your answer is incorrect.

The correct answer is: 0.115