

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24 > EECE105L-Odd 2020 > 16 October - 22 October > Quiz 2

Started on	Thursday, 17 December 2020, 7:11 PM
State	Finished
Completed on	Thursday, 17 December 2020, 7:41 PM
Time taken	29 mins 56 secs
Grade	4.00 out of 5.00 (80%)


Question 1

Correct

Mark 1.00 out of

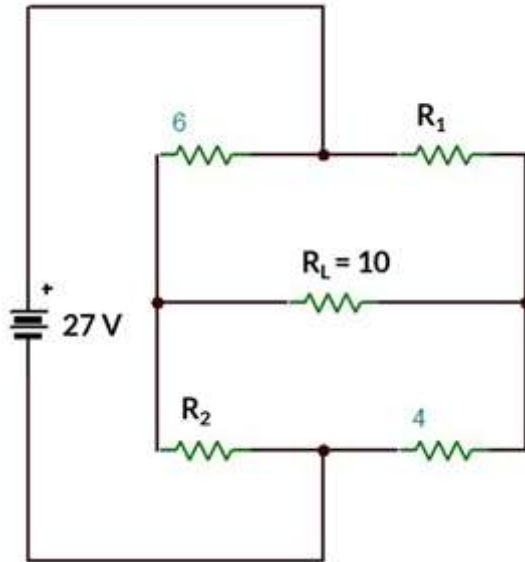1.00

Find the Thevenin's equivalent resistance (R_{th} in Ohm) for the circuit shown in Figure below when $R_1=8.5$ Ohm and $R_2=7.8$ Ohm. (All resistances are in Ohm)



Select one:

- ☐ a. 18.33
- ☒ b. 6.11 ✓
- ☐ c. 12.22
- ☐ d. 3.06

Your answer is correct.

The correct answer is: 6.11




Question 2

Correct

Mark 1.00 out of

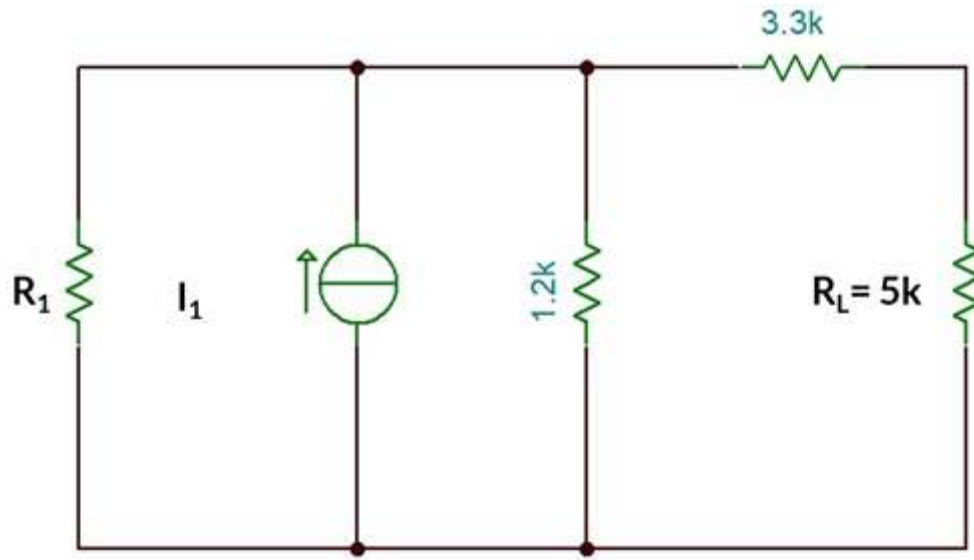1.00

Find the current (in mA) through the resistor R_L for the circuit shown below when $R_1=3.8\text{ k}\Omega$ and $I_1=4.3\text{ mA}$.



Select one:

- ☐ a. 0.21
- ☐ b. 0.85
- ☐ c. 0.71
- ☒ d. 0.43 ✓

Your answer is correct.

The correct answer is: 0.43




Question 3

Incorrect

Mark 0.00 out of

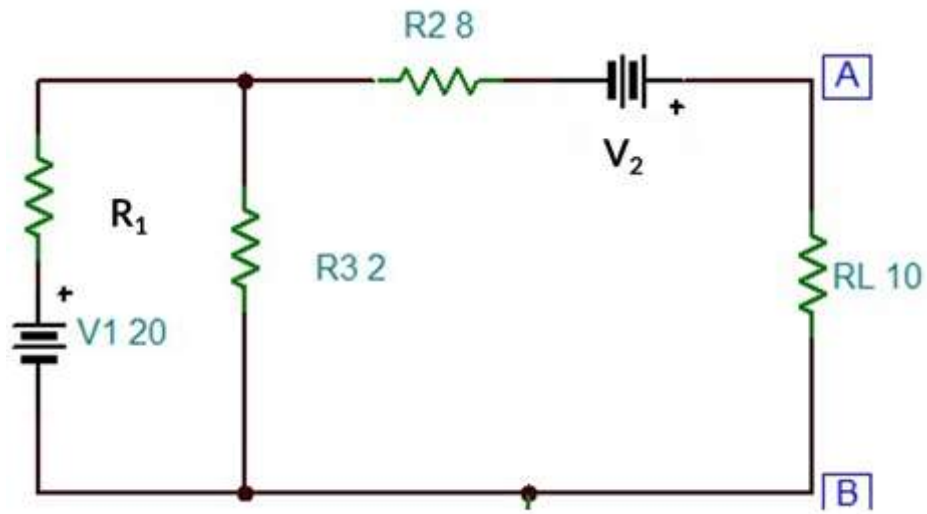1.00

Find the voltage (in Volt) across the resistor R_L for the circuit shown below when $R_1=3.9\ \Omega$ and $V_2=1.7\text{ V}$. (All resistances are in Ohm)



Select one:

- ☒ a. 8.78 ✖
- ☐ b. 2.19
- ☐ c. 4.39
- ☐ d. 1.32

Your answer is incorrect.

The correct answer is: 4.39




Question 4

Correct

Mark 1.00 out of

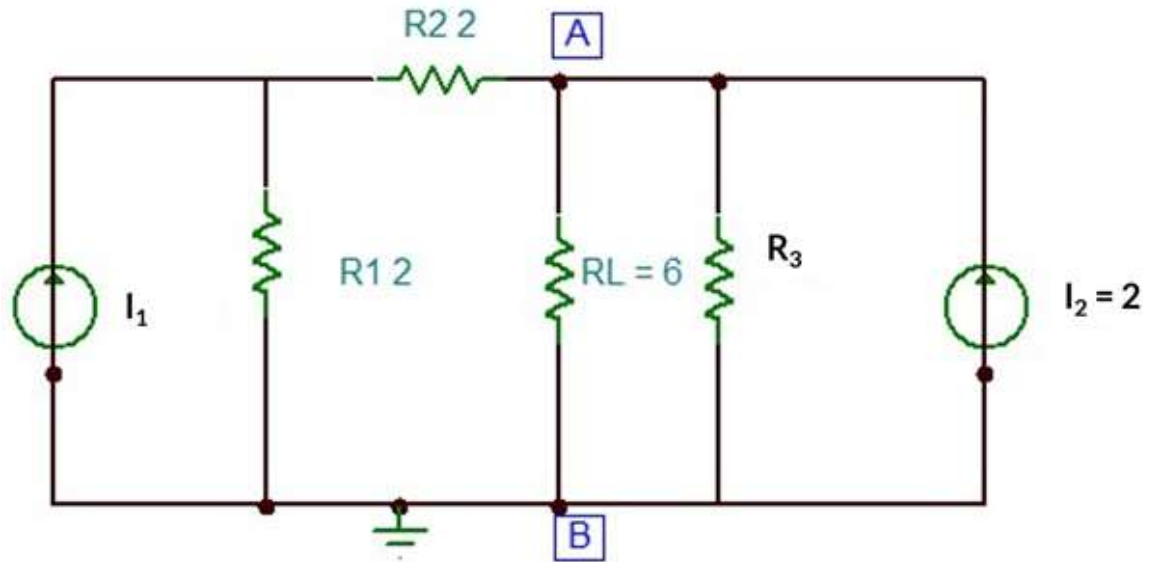1.00

Evaluate the voltage (in Volt) across the load resistor R_L for the given circuit when $R_3=9.7$ Ohm and $I_1=8.7$ A. (All resistances and currents are in Ohm and Ampere, respectively)



Select one:

- ☐ a. 48.87
- ☒ b. 12.22 ✓
- ☐ c. 24.43
- ☐ d. 6.11

Your answer is correct.

The correct answer is: 12.22




Question 5

Correct

Mark 1.00 out of

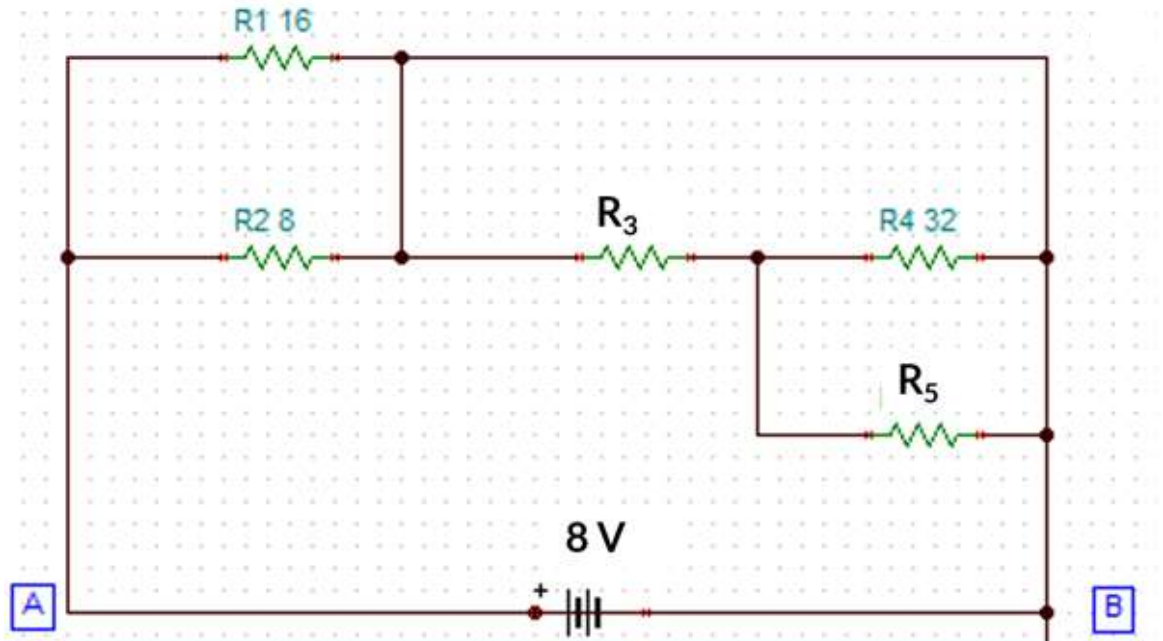1.00

Find the current (in Ampere) flowing through the resistor R_3 in the circuit shown below when $R_3=7.6\text{ Ohm}$ and $R_5=5.1\text{ Ohm}$. (All resistance values are in Ohm).



Select one:

- ☐ a. 0.79
- ☐ b. 0.31
- ☒ c. 0.00 ✓
- ☐ d. 0.63

Your answer is correct.

The correct answer is: 0.00

