

**POSSESSION OF MOBILE IN EXAMINATION IS A UFM PRACTICE**

Name of Student ----- Enrolment No. -----

Department -----

**BENNETT UNIVERSITY, GREATER NOIDA**

**Mid Term Examination, FALL SEMESTER 2018-19**

COURSE CODE: EECE105L

MAX. DURATION: Three Hours

COURSE NAME: Fundamentals of Electrical and Electronics Engineering

COURSE CREDIT: 5

MAX. MARKS: 40

**Note**

- Answer all questions
- Assume any missing data

**Questions**

1. Convert 109.328(10) to binary. After radix point, six positions are desired. **(4 Marks)**  
Radix point: or radix character is the symbol used in numerical representations to separate the integer part of a number from its fractional part.
2. Represent -47 in sign-bit (sign modulus) representation, 1's complement and 2's complement. Use 8-bits. **(4 Marks)**
3. Consider the truth table given in Table 1. Write down logic function,  $F(SOP)$ , as a sum of products. Write down the logic function,  $F(POS)$  as a product of sums. Prove that  $F(POS) = F(SOP)$ . **(4 Marks)**

Table 1: Truth table for problem 3

Inputs			Output
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

4. Consider the logic function described by (1). Simplify the logic function. Draw the logic circuit that implements the function before logic simplification. **(4 Marks)**

$$Y = \overline{A}B + B\overline{C} + BC + A\overline{B}\overline{C} \quad (1)$$

5. Draw a cross-section of an n-channel MOSFET and explain its working. (3 Marks)
6. A  $1\text{ k}\Omega$  resistor is used as a load to a full-wave bridge rectifier which uses silicon diode. If the peak-inverse-voltage of each diode is  $50\text{ V}$ , what is the maximum possible value of the amplitude of the input sine wave? Draw the circuit diagram of a full-wave bridge rectifier. Draw the waveform of the output current. (6 Marks)
7. A Zener diode voltage regulator is shown in fig. 1. The voltage across the  $18\text{ }\Omega$  load stays  $18\text{ V}$  as long as the Zener current is maintained between  $200\text{ mA}$  and  $2\text{ A}$ . Find the power rating of the Zener diode. Find the value of resistance  $R$ . The input voltage may vary between  $22\text{ V}$  to  $28\text{ V}$ . (5 Marks)

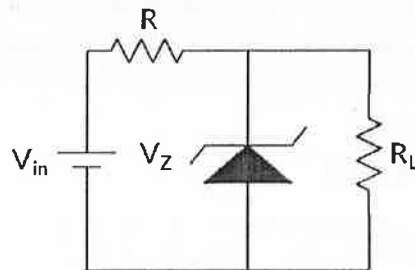


Fig. 1: Circuit for problem 7

8. In the circuit shown in Fig. 2, If  $v(t)$  and  $i(t)$  are in phase, what is the value of  $L$ ? Given that  $\omega = 4000\text{ rad/sec}$ . (4 Marks)

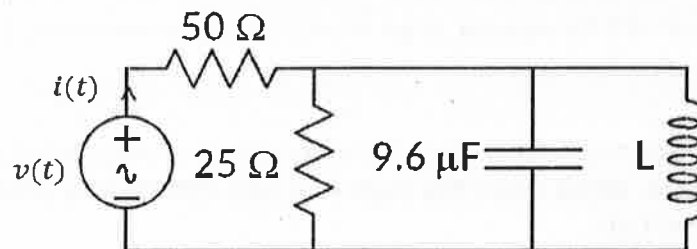


Fig. 2: Circuit for problem 8

9. For the circuit shown in fig. 3, find the maximum power delivered to  $40\text{ }\Omega$  resistance. (6 Marks)

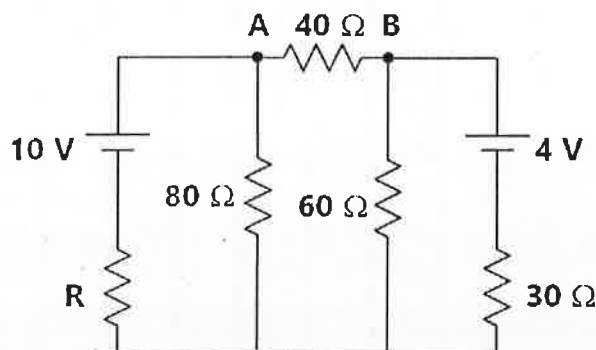


Fig. 3: Circuit for problem 9

----- End of Questions -----