

Department of ECE, Bennett University

CSET102L: Introduction to Electrical and Electronics Engineering

Tutorial Sheet-2

1. For the circuits shown in fig. 1 through 4, find the equivalent resistance R_T between nodes A and B. If the value for any resistor is not provided, assume $1\text{ k}\Omega$ resistance.

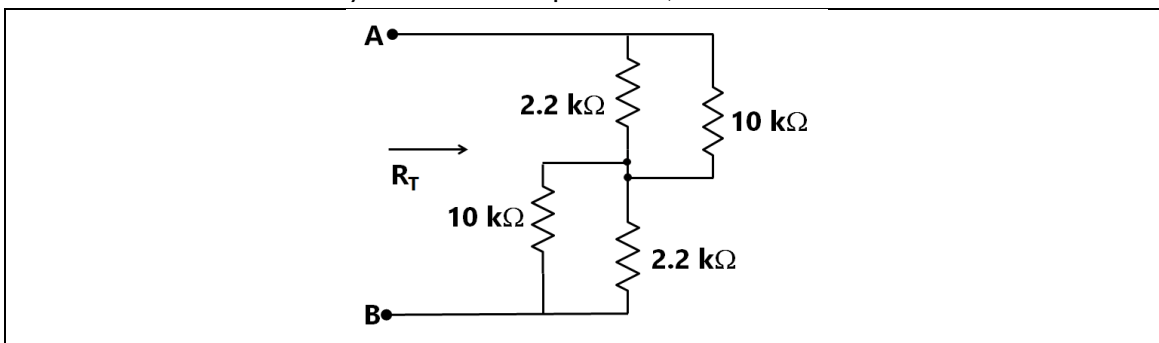


Fig. 1

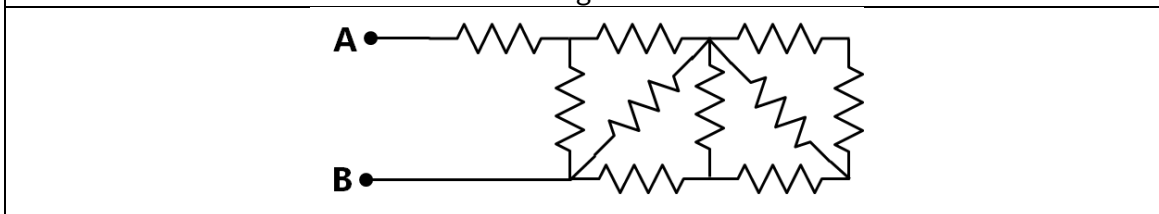


Fig. 2

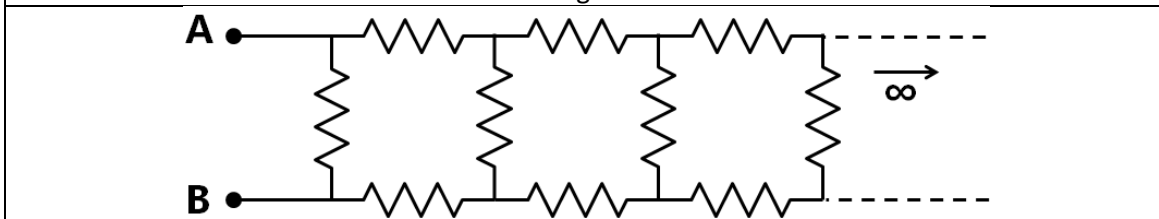


Fig. 3

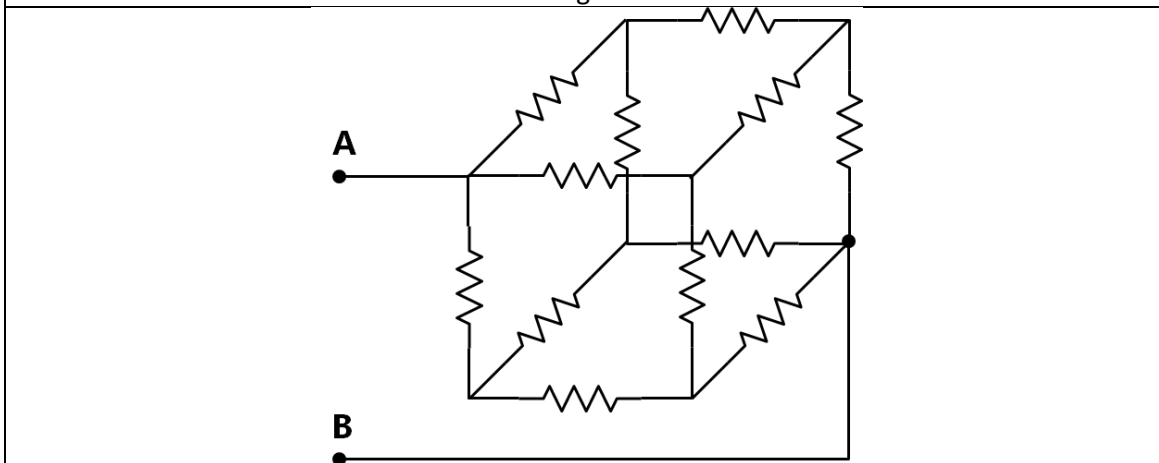


Fig. 4

2. For the circuit shown in fig. 5 through 8, find the equivalent resistance between nodes A and B. Then evaluate current through each resistor and voltage drop across each resistor.

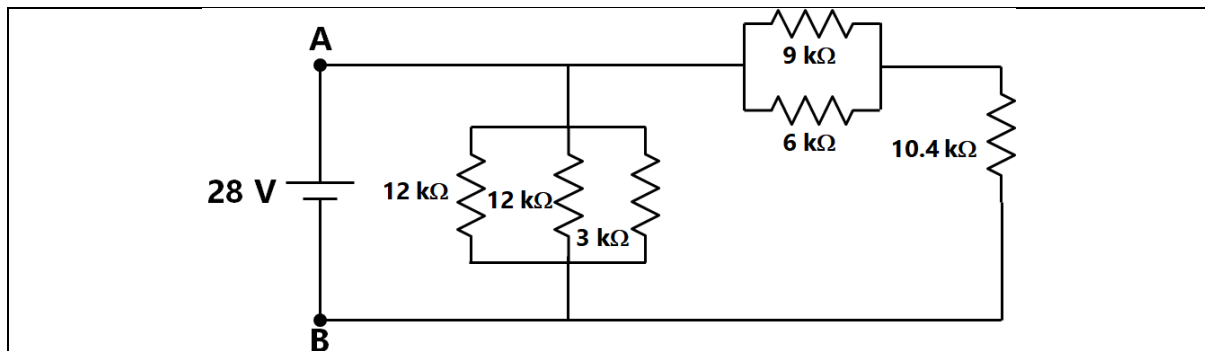


Fig. 5

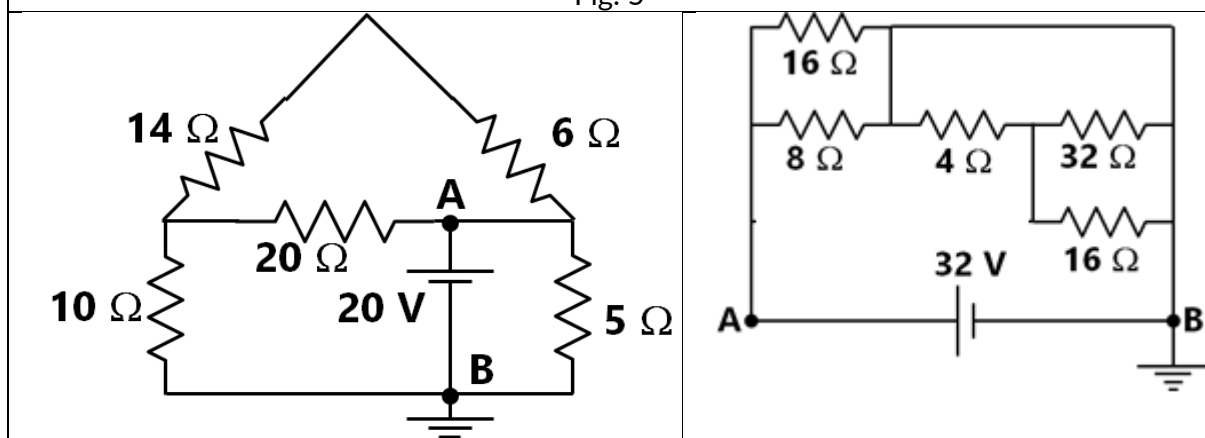


Fig. 6

Fig. 7

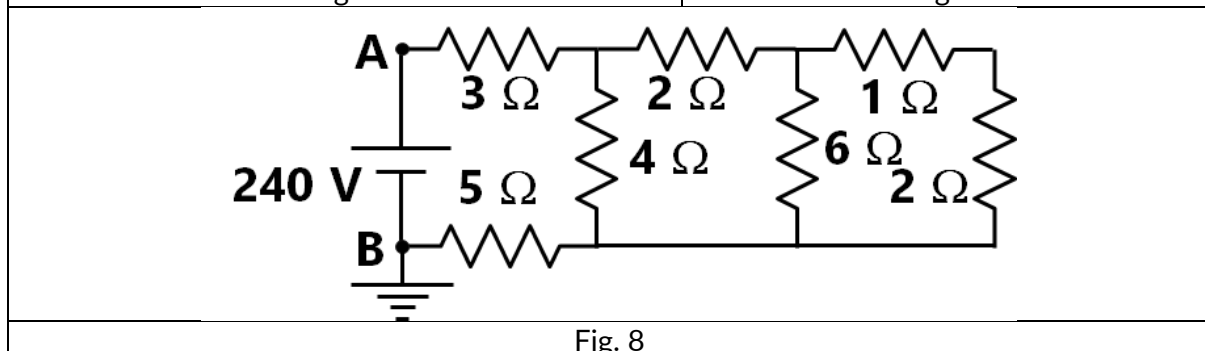


Fig. 8

3. For the circuit shown in fig. 9 and fig. 10, determine current through the resistors, voltage across the resistors and their power rating.

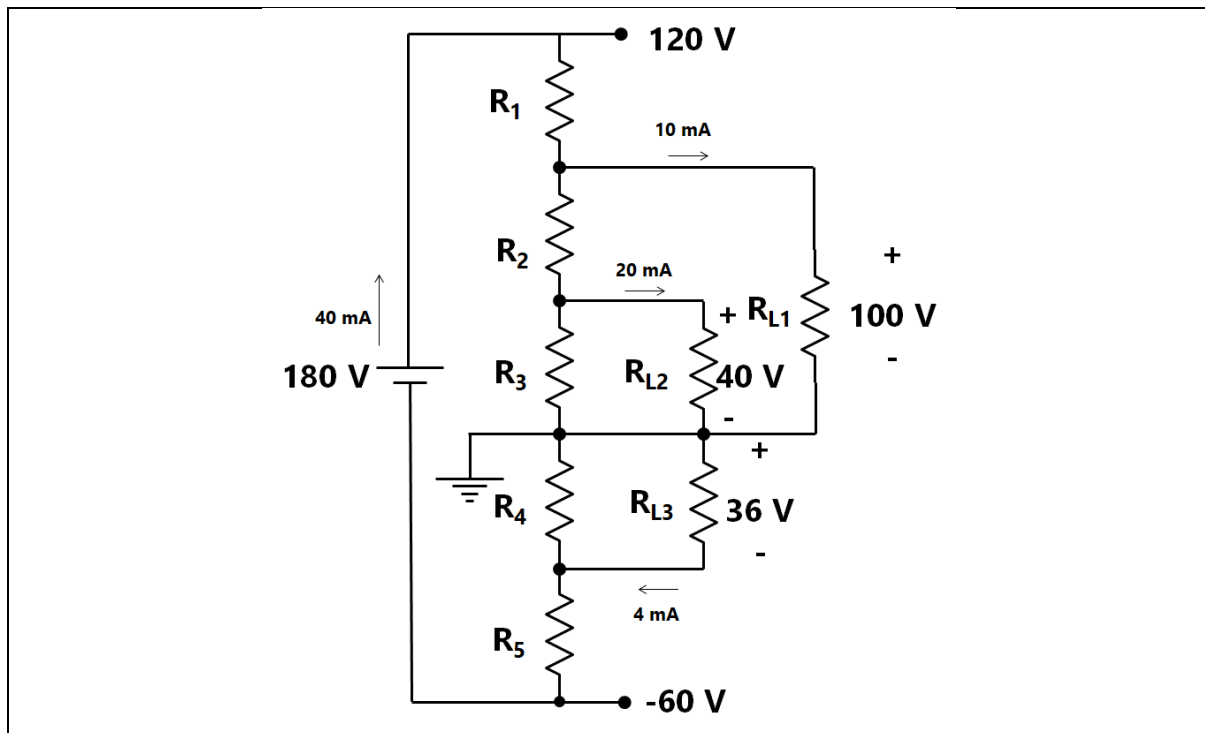


Fig. 9

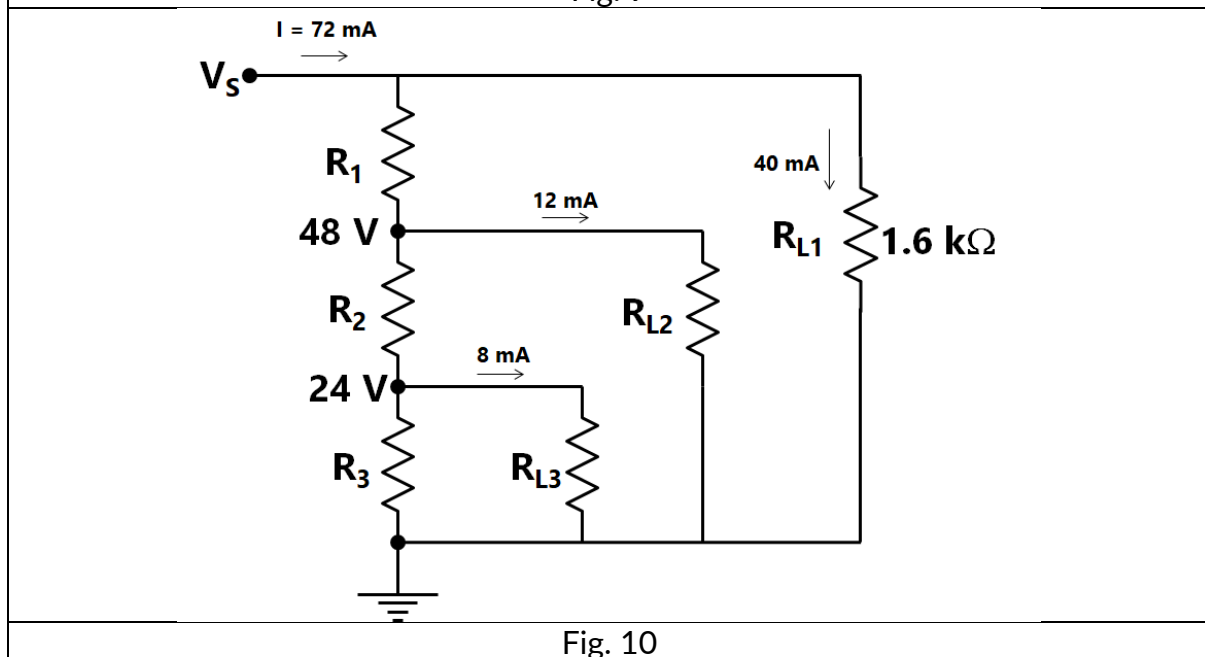


Fig. 10

----- END OF QUESTIONS -----

Answers:

Question 1:

Figure 1: $R_T = 3.6 \text{ k}\Omega$

Figure 2: $R_{AB} = 1.62 \text{ K}\Omega$

Figure 3: $R_{AB} = 0.732 \text{ R}\Omega$

Figure 4: $R_{AB} = (5/6)R \text{ k}\Omega$

Question 2:

Figure 5: $R_{AB} = 1.75 \text{ K}\Omega$

Resistor	Current through the resistor	Voltage across the resistor
10.4 K Ω	2 mA	20.8 V
9 K Ω	0.8 mA	7.2 V
6 K Ω	1.2 mA	7.2 V
12 K Ω	2.33 mA	27.96 V
3 K Ω	9.34 mA	28.02 V

Figure 6: $R_{AB} = 4 \text{ }\Omega$

Resistor	Current through the resistor	Voltage across the resistor
14 K Ω	0.5 A	7 V
10 K Ω	1 A	10 V
6 K Ω	0.5 A	3 V
20 K Ω	0.5 A	10 V
5 K Ω	4 A	20 V

Figure 7: $R_{AB} = 16/3 \text{ }\Omega$

Resistor	Current through the resistor	Voltage across the resistor
16 Ω (R1)	2 A	32 V
8 Ω	4 A	32 V
4 Ω	0	0
32 Ω	0	0
16 Ω (R5)	0	0

Figure 8: $R_{AB} = 10 \Omega$

Resistor	Current through the resistor	Voltage across the resistor
1 Ω	8 A	8 V
2 Ω (R4)	12 A	24 V
2 Ω (R7)	8 A	16 V
3 Ω	24 A	72 V
4 Ω	12 A	48 V
5 Ω	24 A	120 V
6 Ω	4 A	24 V

Question 3:

Figure 9

Resistor	Current through the resistor	Voltage across the resistor	Power rating
R ₁	40 mA	20 V	0.8 W
R ₂	30 mA	60 V	1.8 W
R ₃	10 mA	40 V	0.4 W
R ₄	36 mA	36 V	1.296 W
R ₅	36 mA	24 V	0.96 W

Figure 10

Resistor	Current through the resistor	Voltage across the resistor	Power rating
R ₁	32 mA	16 V	0.512 W
R ₂	20 mA	48 V	0.96 W
R ₃	12 mA	24 V	0.288 W
R _{L1}	40 mA	64 V	2.56 W
R _{L2}	12 mA	48 V	0.576 W
R _{L3}	8 mA	24 V	0.192 W