

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24 > EECE105L-Odd 2020 > 9 October - 15 October > Quiz 1

Started on	Friday, 4 December 2020, 7:19 PM
State	Finished
Completed on	Friday, 4 December 2020, 7:49 PM
Time taken	30 mins 1 sec
Grade	5.00 out of 5.00 (100%)




Question 1

Correct

Mark 1.00 out of

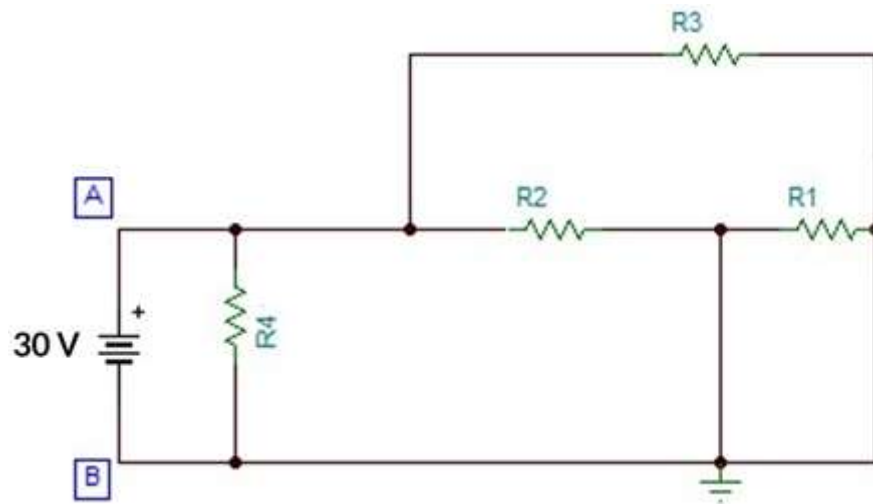1.00

Find the equivalent resistance (in Ohm) of the circuit between A and B. The values of resistances are $R_1=60\ \Omega$, $R_2=46\ \Omega$, $R_3=35\ \Omega$, $R_4=39\ \Omega$.



Select one:

- ☐ a. 9.28
- ☒ b. 13.17 ✓
- ☐ c. 10.02
- ☐ d. 10.88

Your answer is correct.

The correct answer is: 13.17




Question 2

Correct

Mark 1.00 out of

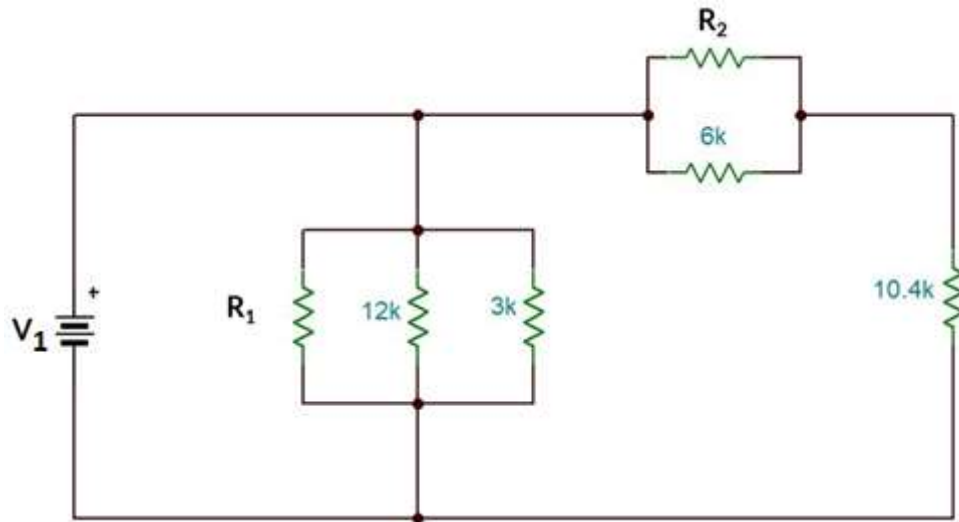1.00

In the circuit given below, find the voltage (in Volt) across the 3K Ohm resistor when $V_1=5.5$ V, $R_1=5.0$ k Ω and $R_2=4.5$ k Ω :



Select one:

- ☐ a. 18.30
- ☒ b. 5.50 ✓
- ☐ c. 20.50
- ☐ d. 3.09

Your answer is correct.

The correct answer is: 5.50




Question 3

Correct

Mark 1.00 out of

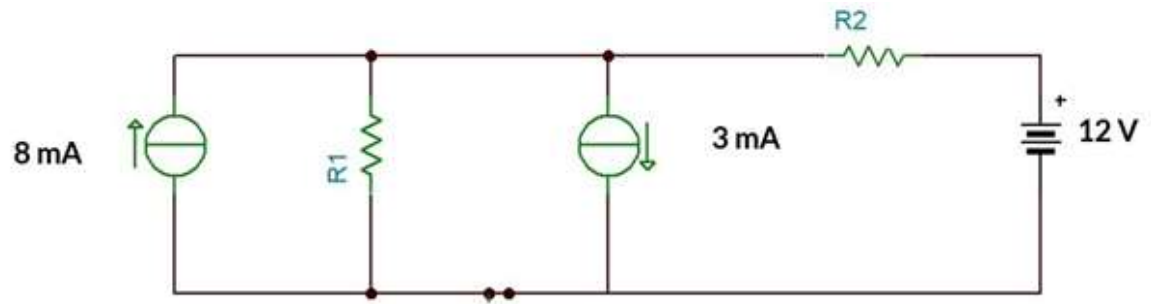1.00

For the circuit shown below, calculate the voltage (in Volt) across the resistor R1 when $R1=12.5\text{ k}\Omega$ and $R2=59.1\text{ k}\Omega$



Select one:

- ☒ a. 53.68 ✓
- ☐ b. 5.20
- ☐ c. 52.46
- ☐ d. 125.91

Your answer is correct.

The correct answer is: 53.68




Question 4

Correct

Mark 1.00 out of

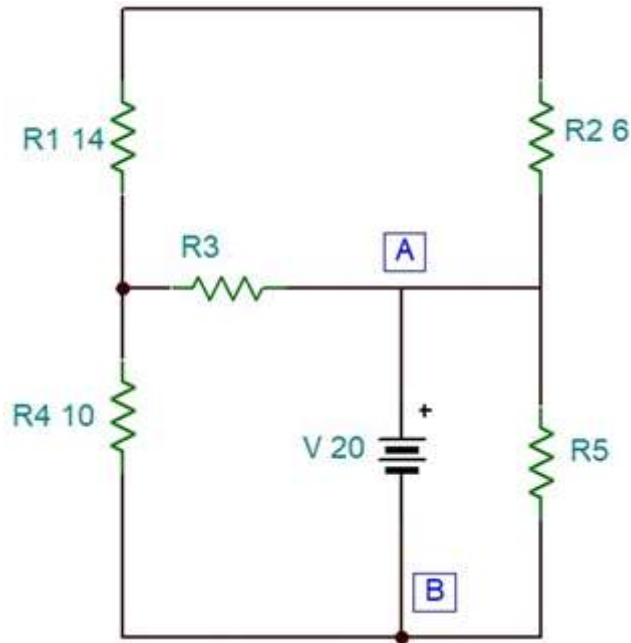1.00

Find the equivalent resistance (in Ohm) across the nodes A, B for the circuit shown below when $R_3=1.7\ \Omega$ and $R_5=6.7\ \Omega$. (All the resistance values given in the figure are in Ohms).



Select one:

- ☒ a. 4.24 ✓
- ☐ b. 3.77
- ☐ c. 4.34
- ☐ d. 5.93

Your answer is correct.

The correct answer is: 4.24




Question 5

Correct

Mark 1.00 out of

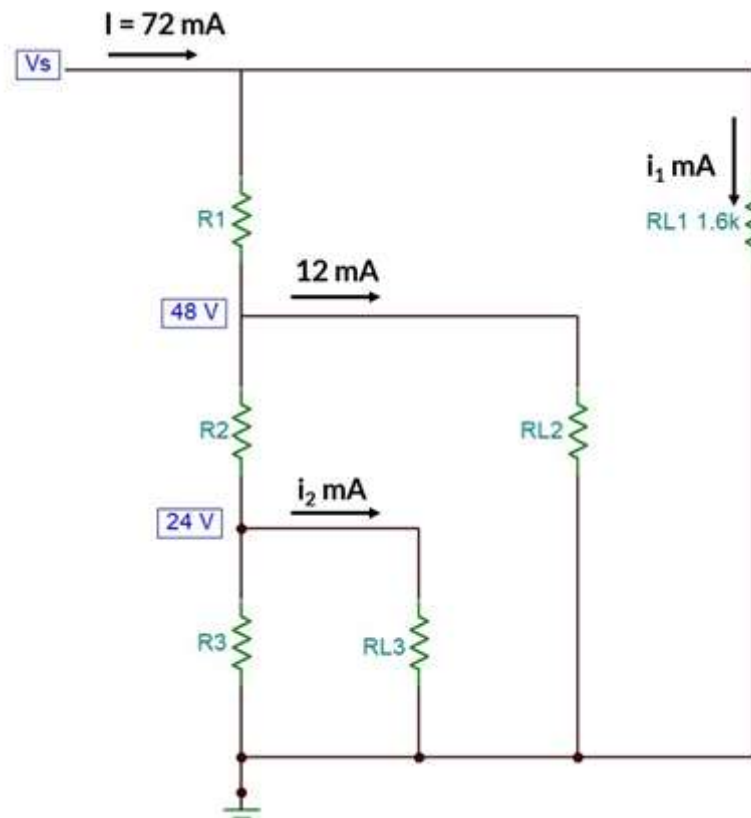1.00

Find the current (in mA) flowing through the resistor R3 for the circuit shown below when $I_1=8.0$ mA and $I_2=5.2$ mA



Select one:

- ☒ a. 46.80 ✓
- ☐ b. 36.80
- ☐ c. 57.20
- ☐ d. 73.20

Your answer is correct.

The correct answer is: 46.80

