

POSSESSION OF MOBILE IN EXAMINATION IS UFM PRACTICE

Name of Student ----- Enrolment No. -----

Department -----

BENNETT UNIVERSITY, GREATER NOIDA

Midterm Examination, SPRING SEMESTER 2018-19

COURSE CODE: **ECSE104L**

MAX. DURATION: **ONE HOUR**

COURSE NAME: **DIGITAL DESIGN**

COURSE CREDIT: **5**

MAX. MARKS: **50**

Note: All the questions are compulsory.

- Please write precisely and neatly. Please make clear diagram wherever required.

Q1. Perform following operation and write all intermediate steps (5 Marks)

- Subtract 25-10 using 2's complement
- Subtract 12 -20 using 1's complement

Q2. Perform the following numbers conversion: (4 Marks)

- $(124.56)_{10} = (?)_8$
- $(ABC.67)_{16} = (?)_4$

Q3. Represent the decimal number 1935 in (2 Marks)

- BCD code
- 8 4 -2 -1 code

Q4. Simplify the following Boolean functions, using four-variable k-maps: (4 Marks)

$$F(A, B, C, D) = AD' + B'C'D' + BC'D' + B'C'D$$

Q5. Identify and analyse the Boolean function with and without don't care condition in terms of number of literals(L), gate input(G) for the following scenario (10 Marks)

$$F(A, B, C, D) = \sum (0, 6, 8, 13, 14)$$
$$d(A, B, C, D) = \sum (2, 4, 10)$$

Q6. Design a BCD to seven-segment display decoder. Prepare the truth table and also the minimized Boolean expression for **one of the output** using K-Map for this problem. (10 Marks)

Q7. Analyse ripple carry adder and carry lookahead adder in terms of power, area and performance (computation time) explain with a real-life example when you will use ripple carry adder and when you will use carry look ahead adder? (5 Marks)



Q8. Write Verilog code of ripple carry adder using full adder.

(10 Marks)

```
module fulladder(S,Cout,A,B,Cin);
```

```
input A,B,Cin;
```

```
output S,Cout;
```

```
** write your code**
```

```
endmodule
```

```
module RCA(S,Cout,A,B,Cin);
```

```
input [3:0]A,B
```

```
input Cin;
```

```
output [3:0]S;
```

```
output Cout;
```

```
** write your code**
```

```
endmodule
```