



Dashboard > My courses > EECE105L : Fundamentals of Electrical and Electronics Engineering (EVEN SEMESTER 2021-22) > 26 May - 1 June > Tutorial Quiz 03

Started on Tuesday, 31 May 2022, 8:51 PM

State Finished

Completed on Tuesday, 31 May 2022, 9:03 PM

Time taken 12 mins 10 secs


Grade 5.00 out of 5.00 (100%)

Question 1

Correct

Mark 1.50 out of 1.50

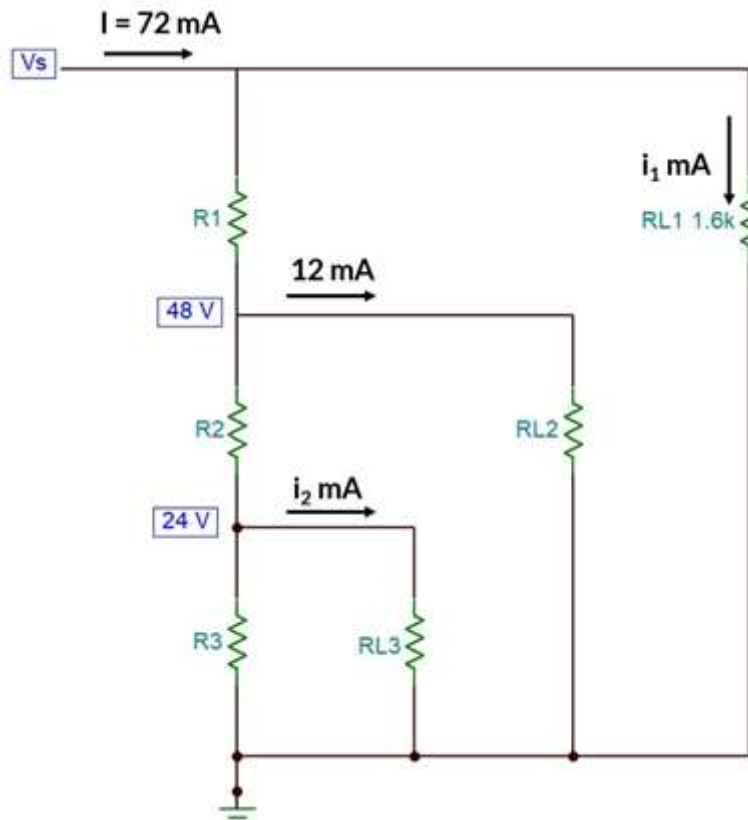Find the current (in mA) flowing through the resistor R3 for the circuit shown below when $I_1 = 9$ mA and $I_2 = 18$ mA



Answer: ✓

The correct answer is: 33.00


Question 2

Correct

Mark 1.50 out of

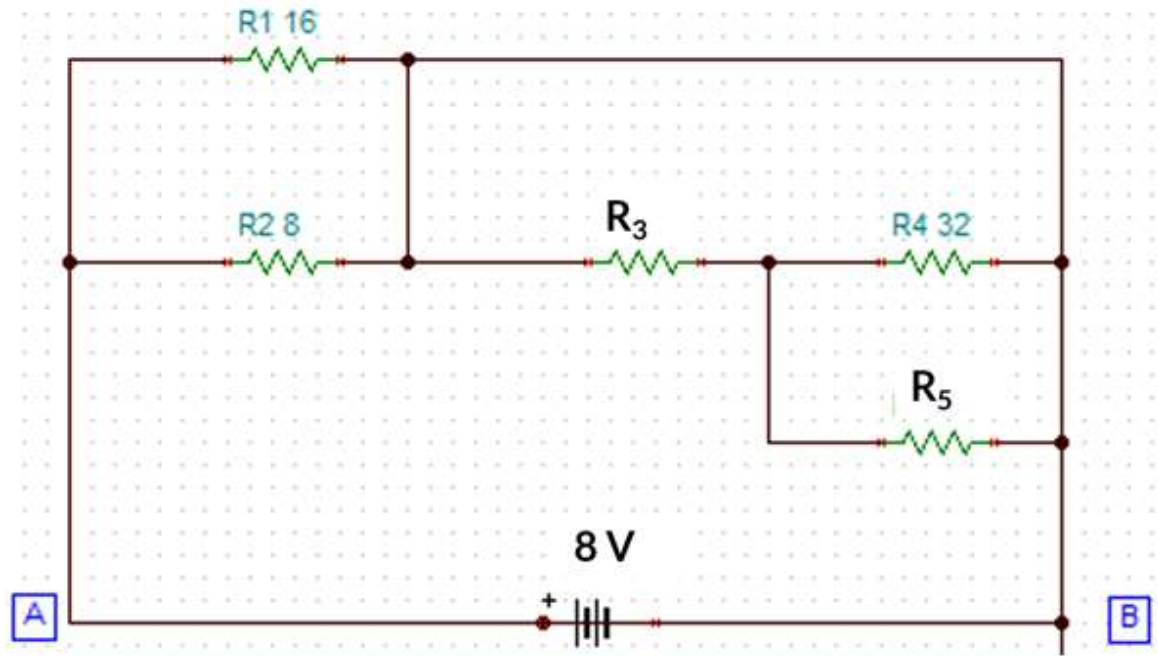1.50

Find the current (in Ampere) flowing through the resistor R_3 in the circuit shown below when $R_3=9\ \Omega$ and $R_5=9\ \Omega$. (All resistance values are in Ω).



Select one:

- ☐ 0.56
- ☐ 0.22
- ☒ 0.00 ✓
- ☐ 0.44

Your answer is correct.

The correct answer is: 0.00


Question 3

Correct

Mark 2.00 out of

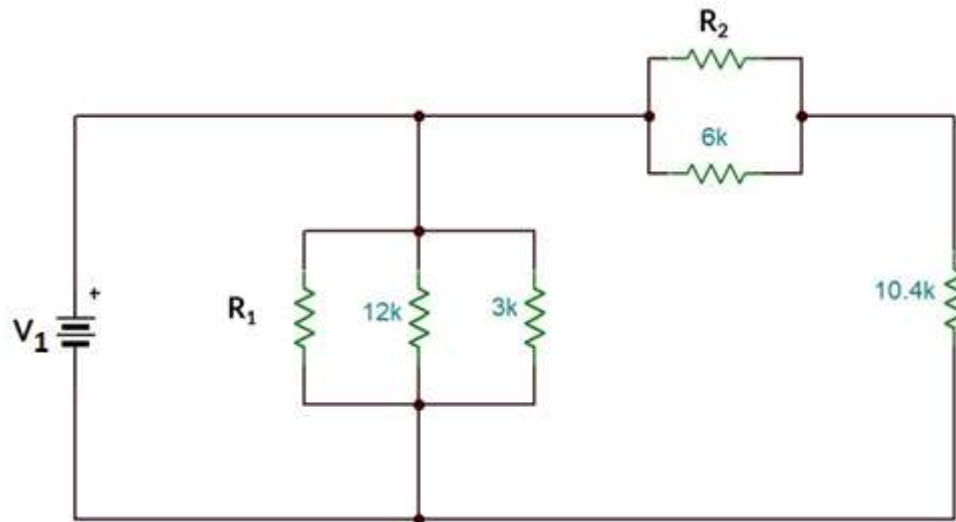2.00

In the circuit given below, find the voltage (in Volt) across the 3K Ohm resistor when $V_1=6$ V, $R_1=7$ k Ω and $R_2=8$ k Ω .



Select one:

- ☐ 21.00
- ☐ 17.57
- ☐ 4.80
- ☒ 6.00 ✓

Your answer is correct.

The correct answer is: 6.00