

Enrolment No: _____

Name of Student: _____

MID-TERM EXAMINATION EVEN SEMESTER 2022-23

COURSE CODE	CSET102	MAX. DURATION	1 HRS
COURSE TITLE	INTRODUCTION TO ELECTRICAL AND ELECTRONICS ENGINEERING	TOTAL MARKS	20
COURSE CREDIT	5		

- 1) Find the voltage V_{ab} and the current i_0 in the circuit shown in Figure 1. (6 Marks)

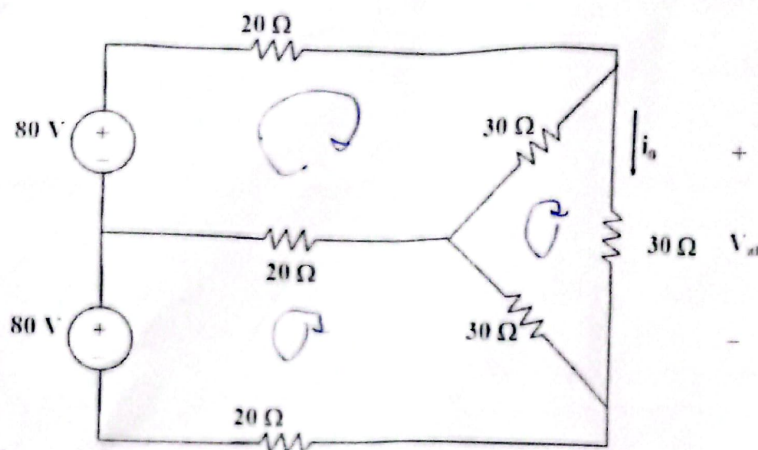


Figure 1

- 2) For the circuit shown in Figure 2, determine the power consumed by the 5Ω resistor. (3 Marks)

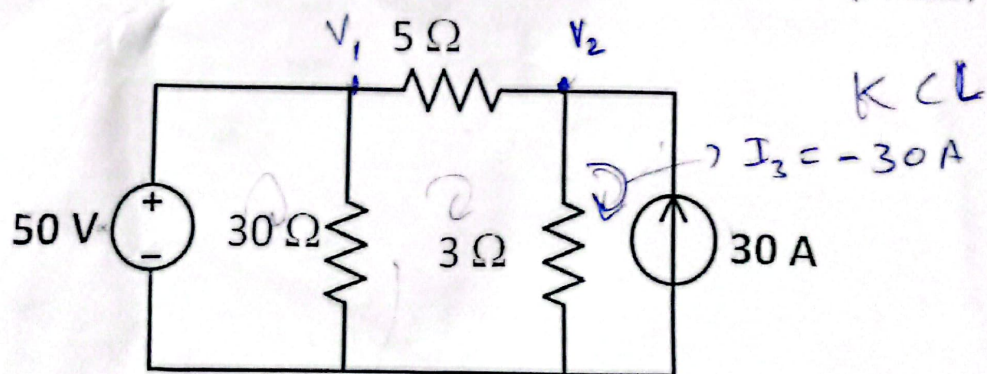


Figure 2

Handwritten calculations:

$$50 - 30(I_1 - I_2) = 0$$

$$50 - 30(I_1 - I_2) = 0$$

$$50 - 30I_1 + 30I_2 = 0$$

$$30I_2 - 30I_1 = -50$$

$$-30I_2 + 30I_1 - 5I_2 = -30(I_2 - I_1) - 3(I_2 + 30)$$

$$-38I_2 = -90$$

$$\rightarrow 38I_2 = 90$$

1 of 2

- 3) Determine the current through the 6Ω resistor for the circuit shown in Figure 3. (2 Marks)

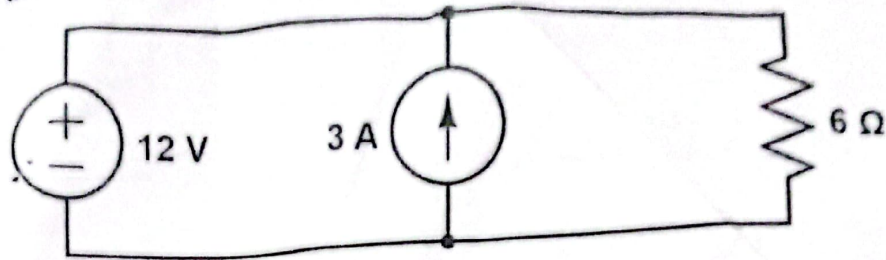


Figure 3

- 4) Replace the circuit between nodes *A* and *B* in Figure 4 with a voltage source in series with a single resistor. Determine the open circuit voltage in the simplified circuit. (5 marks)

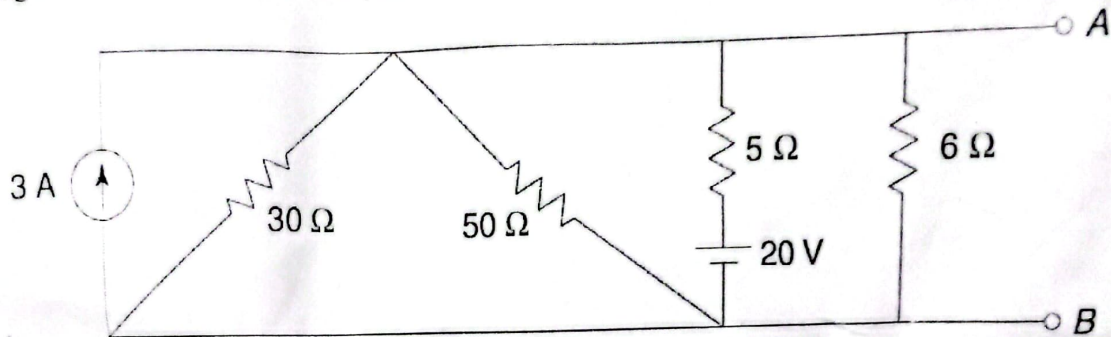


Figure 4

- 5) Simplify the circuit shown in Figure 5 using Thevenin's theorem. The load resistance is connected between nodes *A* and *B*. Find the voltage across the load resistor and the current flowing through the load resistor. (4 Marks)

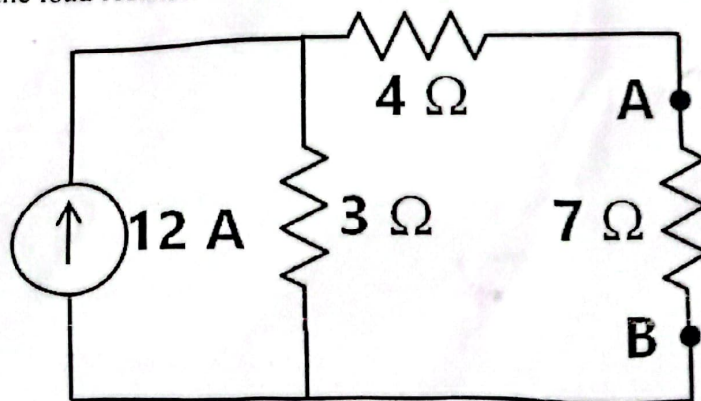


Figure 5

END OF QUESTION PAPER