

Enrolment No: \_\_\_\_\_

Name of Student: \_\_\_\_\_

Department/ School: \_\_\_\_\_

## END TERM EXAMINATION EVEN SEMESTER 2021-22

**COURSE CODE**                      CSET105  
**COURSE TITLE**                    Digital Design  
**COURSE CREDIT**                3-0-2


**MAX. DURATION**    2 HRS

**TOTAL MARKS**        35

### GENERAL INSTRUCTIONS: -

1. Do not write anything on the question paper except **name, enrolment number and department/school.**
2. Carrying mobile phone, smart watch and any other non-permissible materials in the examination hall is an act of UFM.

 **Q1. (a).** Construct truth table of the given logic diagram. Where (D- Input, C- Clock, Q and Q' - Outputs). [3]




**(b).** Explain in one sentence.

1. Drawback with S-R Flipflop.
2. Drawback with J-K Flipflop.

**Q2.** The Following serial data are applied to FF shown in Figure. Determine the resulting serial data that appears at Q output. There is one clock pulse for each bit time. Assume initially Q=0. [4]

CLOCK	J1	J2	K1	K2	Q	$\bar{Q}$
1st	1	1	1	1	?	?
2nd	0	1	0	1	?	?
3rd	1	0	0	0	?	?

 


**Q3.** A new Flip Flop (XY) is designed with the following Truth table. The previous state of XY Flip Flop is  $Q_n$  and the Next State Denoted by  $Q_{n+1}$ . For the New Flip Flop create the Characteristic Table and Excitation Table also Find the Characteristic Equation for Given Flip Flop. [4]

	Input	Input	Output
Clock	X	Y	$Q_{n+1}$
0	Don't care	Don't care	$Q_n$
1	0	0	1
1	0	1	$\overline{Q_n}$
1	1	0	$\overline{Q_n}$
1	1	1	0


Truth Table of XY Flip Flop

**Q4.** Design a 2-bit Synchronous Down Counter with detailed diagram. (Use T Flip Flop). [4]

 **Q5.** In SIPO Register (Given in the Diagram), Find the output (A, B, C, D) after 1<sup>st</sup> clock, 2nd clock, 3rd clock, and 4<sup>th</sup> clock. [4]



 
**Q6.** Design an asynchronous counter using T flipflop for the following sequence. [4]




**Q7.** Convert the S R Flip Flop to T Flip Flop with suitable tables and Logic expression and Logic Diagram. [4]

**Q8.** Design a counter which has no. of states double of no. of Flip Flop used in that counter circuit with the suitable diagram. [4]

 **Q9.** Draw the Output wave form (Q) of the given JK Flip Flop for given Input waveform. Assume previous state is '1' [4]



Input Waveform

 

Logic Symbol

🌀🌀🌀 ALL THE BEST 🌀🌀🌀