

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24  
> EECE105L-Odd 2020 > 6 November - 12 November > Mandatory Mock Quiz 2

**Started on** Saturday, 2 January 2021, 5:00 PM

**State** Finished

**Completed on** Saturday, 2 January 2021, 5:30 PM

**Time taken** 30 mins 1 sec


**Grade** 7.00 out of 10.00 (70%)

**Question 1**

Correct

Mark 3.00 out of  
3.00

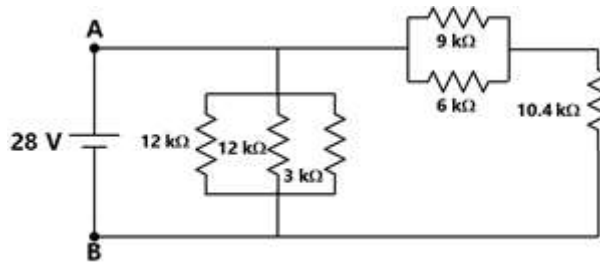Find the current in each parallel path ( $I_2$  through  $10.4 \text{ k}\Omega$ ).



\*  $I_1$  (mA):  ✓

\*  $I_2$  (mA):  ✓




### Question 2

Partially correct

Mark 1.00 out of

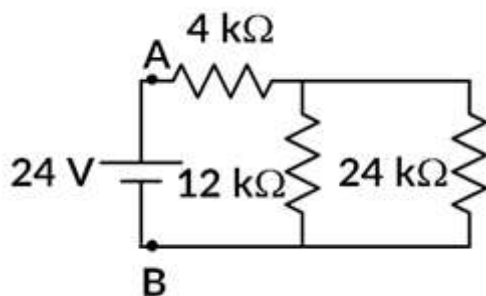2.00

In the figure below, what is the current through the circuit and power delivered by the voltage source?



\* Current (mA):  ✓

\* Power (mW):  ✗


### Question 3

Partially correct

Mark 3.00 out of

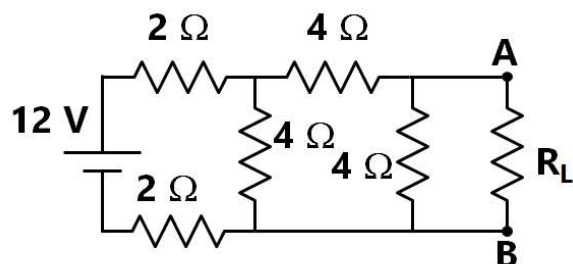5.00

Simplify the circuit using Thevenin's and Norton's theorem. Assume that the load resistance is connected between nodes A and B. Compute the load resistance such that maximum power is transferred to the load. Find the current through the load resistor.



\*  $R_{th}$  or  $R_N$  ( $\Omega$ ):  ✓

\*  $R_L$  ( $\Omega$ ):  ✓

\*  $V_{th}$  (V):  ✗

\*  $I_N$  (A):  ✓

\*  $I_L$  (A):  ✗

