



Dashboard > My courses > EECE105L : Fundamentals of Electrical and Electronics Engineering (EVEN SEMESTER 2021-22) > 9 June - 15 June > Quiz 06

Started on Monday, 13 June 2022, 8:53 PM

State Finished

Completed on Monday, 13 June 2022, 9:03 PM

Time taken 10 mins 8 secs

Grade 4.00 out of 5.00 (80%)


**Question 1**

Correct

Mark 1.50 out of

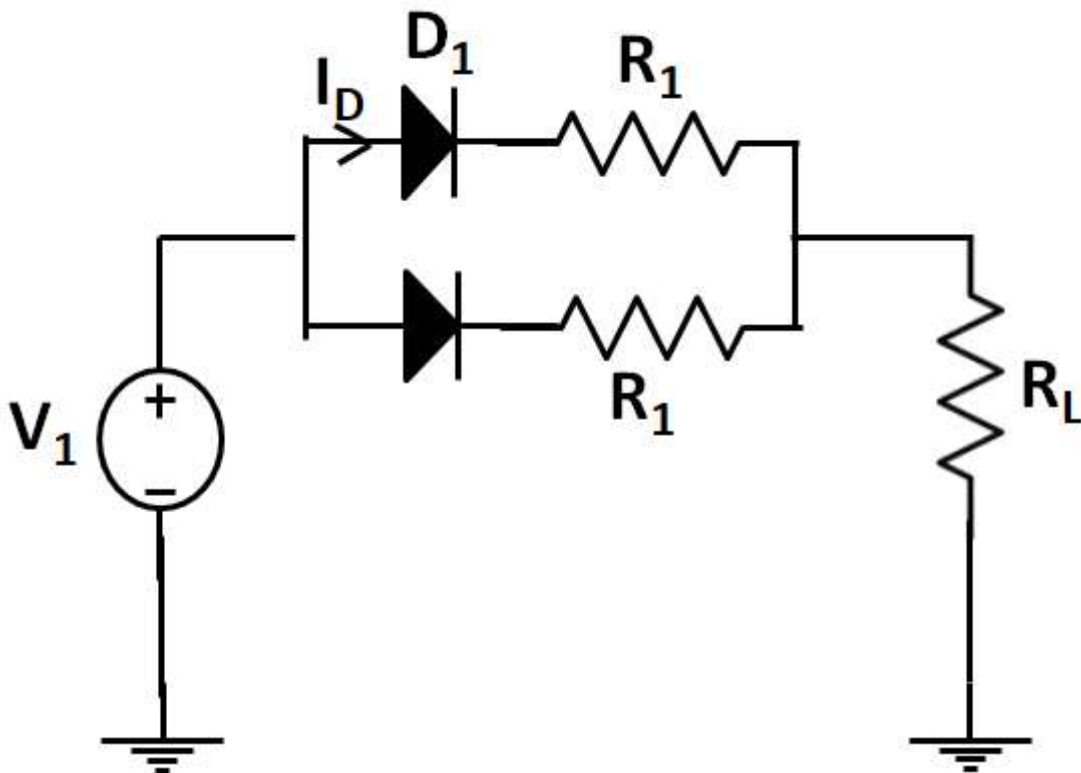1.50

Find the current  $I_D$  (in mA) flowing through the diode  $D_1$ . Given  $V_1=29$  V,  $R_1=5.6$  k $\Omega$ ,  $R_L=4.3$  k $\Omega$  and the diodes are made of silicon and similar V-I characteristics. The cut-in voltage of the diode is 0.7 V.



Answer: 2.008



The correct answer is: 1.99

**Question 2**

Correct

Mark 1.50 out of

1.50

A current of 16 mA flows through an inductor of value 100 mH. The maximum energy (in  $\mu\text{J}$ ) that can be stored in the inductor is  ✓ .

The correct answer is: 12.80


### Question 3

Incorrect





Mark 0.00 out of

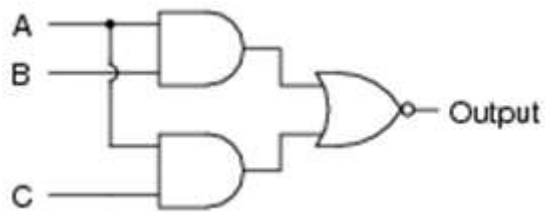1.00


Which of the following gates best represent the logic circuit shown in figure below?



Select one:

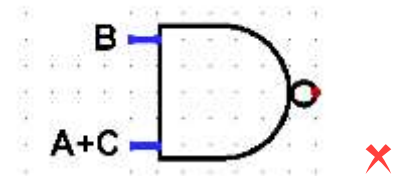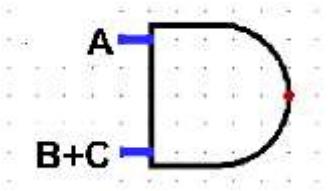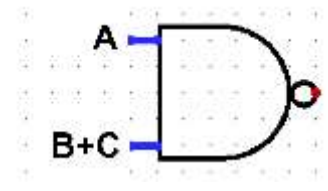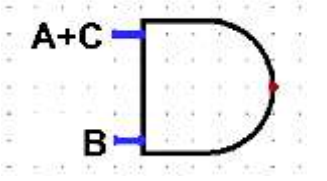- ☒ 
- ☐ 
- ☐ 
- ☐ 

Your answer is incorrect.

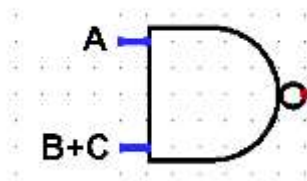

The correct answer is:


**Question 4**

Correct

Mark 1.00 out of

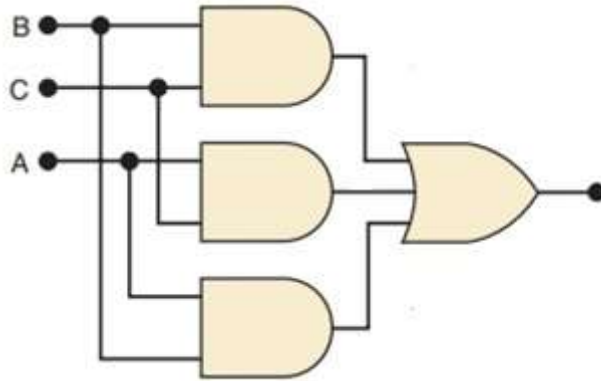1.00

Which of the following expression represents the output of the logic circuit shown in Figure below.



Select one:

- ☐  $A+B+C$
- ☐  $(AB)(BC)(CA)$
- ☒  $AB+BC+CA$  ✓
- ☐  $ABC+BCA$

Your answer is correct.

The correct answer is:  $AB+BC+CA$