

### Question 1

Correct

Mark 1.50 out of

1.50



Flag

question

A current of 20 mA flows through an inductor of value 44 mH. The maximum energy (in  $\mu\text{J}$ ) that can be stored in the inductor is

8.80



## Question 2

Correct

Mark 1.50 out of


1.50



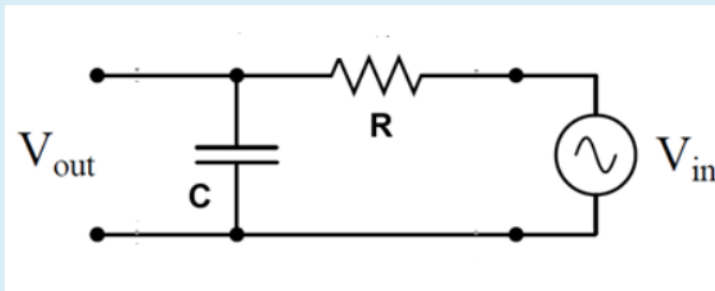question

The circuit shown below is a \_\_\_\_\_ with a cut off frequency of \_\_\_\_\_.

Given  $R=32\text{ k}\Omega$  and  $C=49\text{ nF}$ .



Select one:

- ☐ High pass filter with cut off frequency of 101.553 Hz
- ☐ High pass filter with cut off frequency of 0.102 Hz
- ☐ Low pass filter with cut off frequency of 0.102 Hz
- ☒ Low pass filter with cut off frequency of 101.553 Hz ✓

**Question 3**

Correct

Mark 2.00 out of


2.00



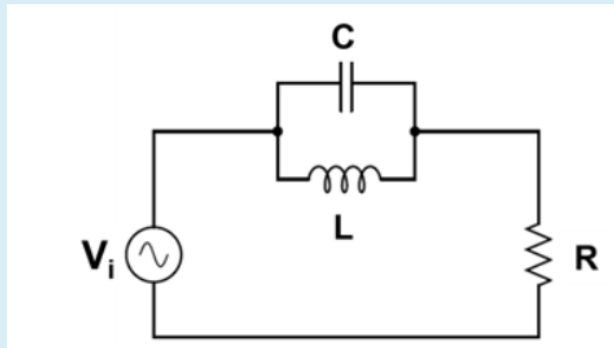question

The equivalent impedance ( $\Omega$ ) of the circuit shown in figure below in Cartesian form can be represented as,  $Z_{eq} = a + jb$  where  $j^2 = -1$ . The input signal to the circuit is  $V_i = V_m \sin \omega t$ . Determine the values of  $a$  and  $b$ .

Given  $V_m = 10.6$  V,  $\omega = 1140$  radians/second,  $R = 129 \Omega$ ,  $C = 3 \mu\text{F}$ ,  $L = 4$  mH.



Select one:

- ☐  $a=380000129.00$  and  $b=386020060.04$
- ☒  $a=129.00$  and  $b=4.63$  ✓
- ☐  $a=129.00$  and  $b=386020060.04$
- ☐  $a=133.56$  and  $b=4.63$