

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24
> EECE105L-Odd 2020 > 20 November - 26 November > Quiz 3

Started on Thursday, 21 January 2021, 7:00 PM

State Finished

Completed on Thursday, 21 January 2021, 7:30 PM

Time taken 30 mins 1 sec

Grade 3.00 out of 5.00 (60%)


Question 1

Correct

Mark 1.00 out of

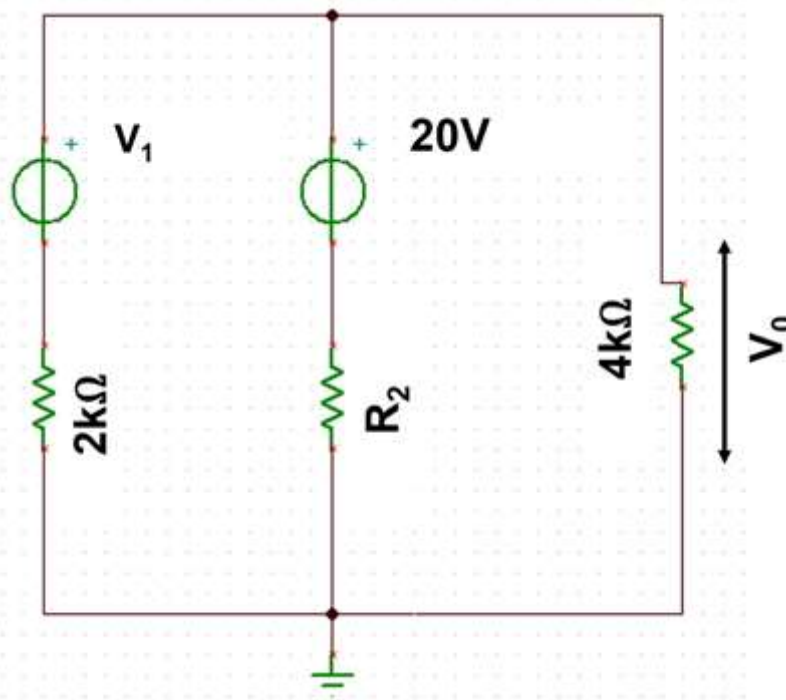1.00

For the circuit shown in Figure below, find the voltage V_0 . Given $V_1=7.8$ V and $R_2=4.4$ k Ω



Select one:

- ☐ a. 4.32
- ☐ b. 17.28
- ☒ c. 8.64 ✓
- ☐ d. 0.33

Your answer is correct.

The correct answer is: 8.64


Question 2

Incorrect

Mark 0.00 out of

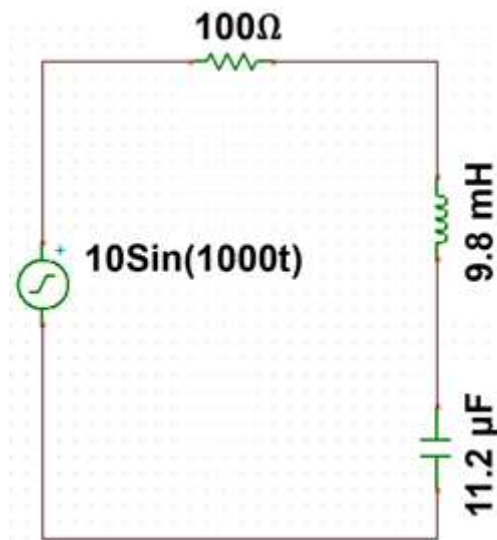2.00

Calculate the current (mA) in polar form flowing through the resistor in the circuit given below



Select one:

- ☒ a. Magnitude=78.3 and Phase=-38.47° ✖
- ☐ b. Magnitude=78.3 and Phase=38.47°
- ☐ c. Magnitude=58.7 and Phase=38.47°
- ☐ d. magnitude=58.7 and angle=-38.47°

Your answer is incorrect.

The correct answer is: Magnitude=78.3 and Phase=38.47°

Question 3

Correct

Mark 1.00 out of

1.00

If a voltage ($At^2 + Bt^{3/2} + C$) V is applied across a $4.8 \mu\text{F}$ capacitor, then evaluate the current (in μA) flowing through the capacitor at $t = 4.2$ seconds. Given $A=1.5$, $B=3.2$, $C=5.6$.

Select one:

- ☐ a. 134.58
- ☐ b. 10.26
- ☒ c. 107.70 ✓
- ☐ d. 2.76

Your answer is correct.

The correct answer is: 107.70


Question 4

Correct

Mark 1.00 out of

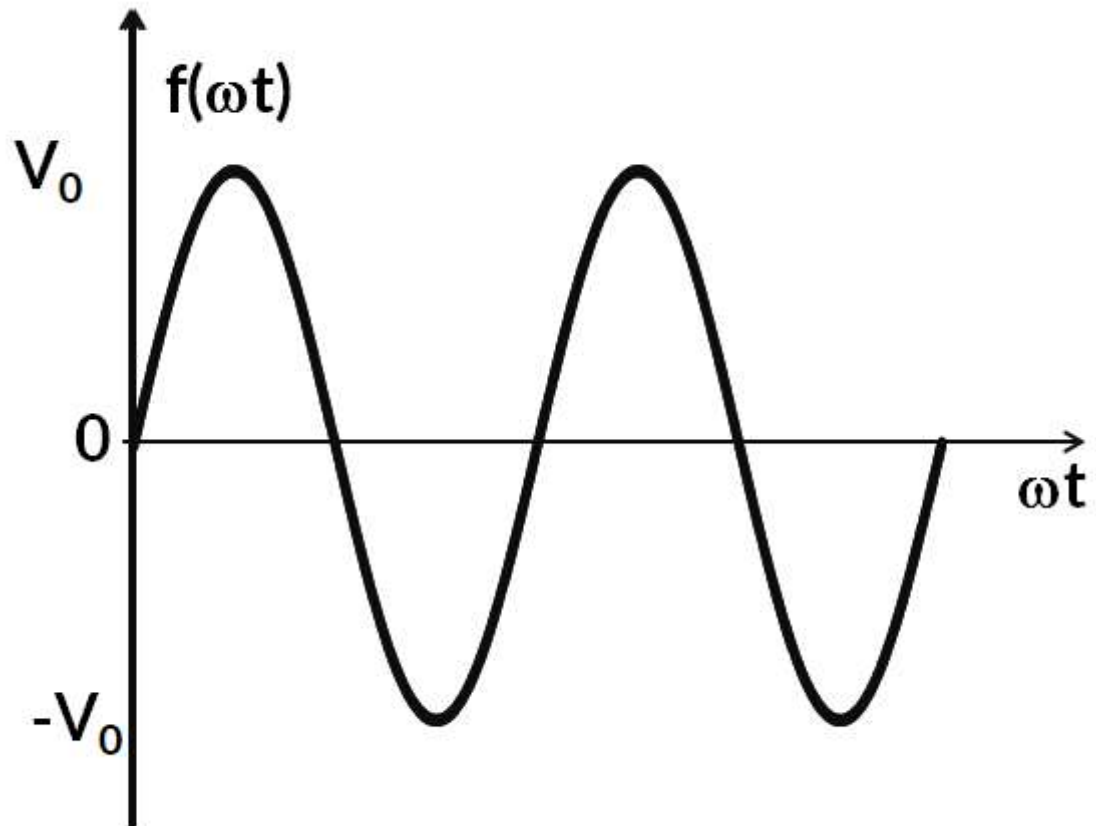1.00

Peak-to-peak value of the following sinusoidal waveform is 10.6 V. The rms value (in Volt) of the waveform is



Select one:

- ☐ a. 14.99
- ☒ b. 3.75 ✓
- ☐ c. 5.30
- ☐ d. 7.50

Your answer is correct.

The correct answer is: 3.75