



Dashboard > My courses > EECE105L : Fundamentals of Electrical and Electronics Engineering (EVEN SEMESTER 2021-22) > 9 June - 15 June > Quiz 05

Started on Friday, 10 June 2022, 8:52 PM

State Finished

Completed on Friday, 10 June 2022, 9:04 PM

Time taken 11 mins 45 secs


Grade 2.00 out of 5.00 (40%)

Question 1

Not answered

Marked out of
2.00

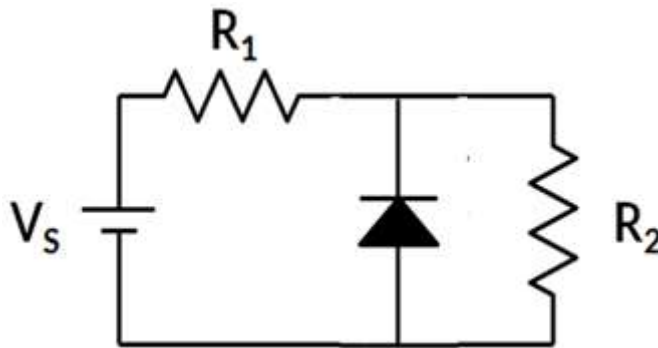The silicon diodes shown in the circuit have a reverse saturation current of 1 nA. Given that the cut-in voltage of the diode is 0.7 V. The supply voltage is $V_s = 7$ Volt. Find the voltage (in Volt) across resistor R_2 when $R_1 = 7.7$ k Ω and $R_2 = 3.9$ k Ω . Assume that the circuit is operating at 300 K.



Answer: ✖

The correct answer is: 2.35

Question 2

Correct

Mark 2.00 out of

2.00

Consider a bar of silicon doped with $1 \times 10^{16} \text{ cm}^{-3}$ Phosphorus atoms and kept at room temperature. The minority carrier type is _____ and concentration (in cm^{-3}) is _____.

Given intrinsic carrier concentration $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$

Note: In the given options 10E(x) represents 10^x

Select one:

- ☐ electrons and 1.00×10^{16}
- ☒ holes and 2.25×10^4 ✓
- ☐ holes and 1.00×10^{16}
- ☐ electrons and 2.25×10^4

Your answer is correct.

The correct answer is: holes and 2.25×10^4

Question 3


Incorrect

Mark 0.00 out of

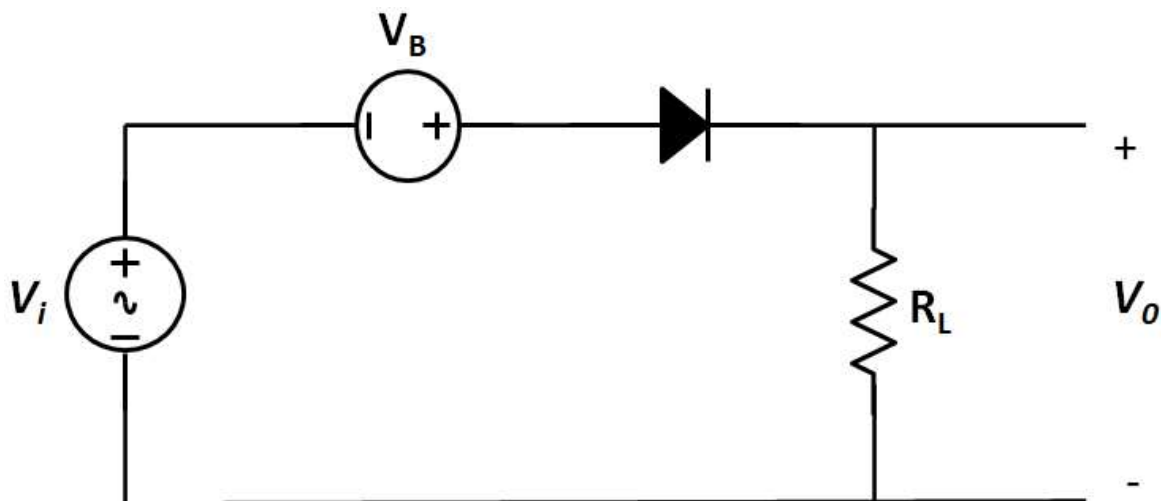1.00

A sinusoidal input of 8 V peak value and bias voltage $V_B = 10 \text{ V}$ is applied in the given circuit. What is the peak value in the positive half of the output waveform?

Consider that the diode is an Ideal Diode.



Answer:



The correct answer is: 18.00