


Question 1


Incorrect


Mark 0.00 out of

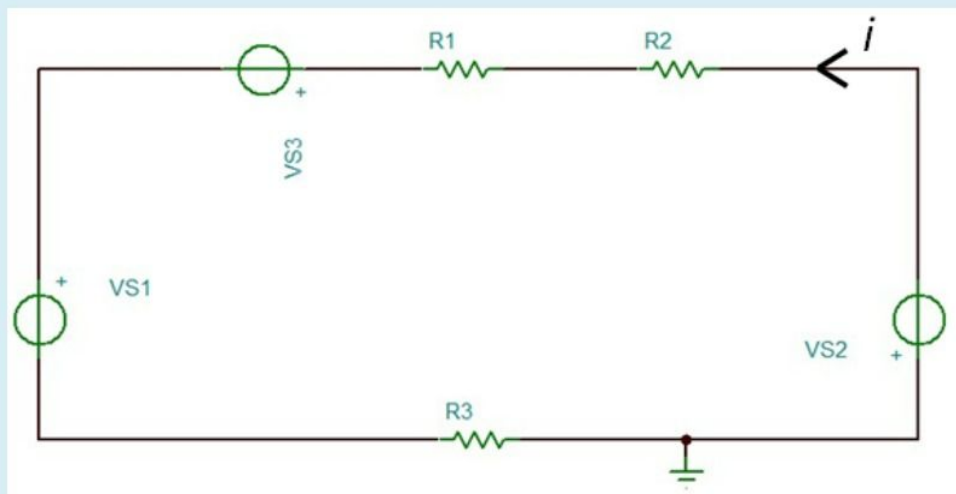1.50

 Flag
question

In the following circuit, Find current i in mA. Given $R_1=31\ \Omega$, $R_2=31\ \Omega$, $R_3=47\ \Omega$, $V_{S1}=9\text{ V}$, $V_{S2}=8\text{ V}$, $V_{S3}=6\text{ V}$.



Answer: 

The correct answer is: -211.00917

Question 2

Correct


Mark 1.50 out of

1.50



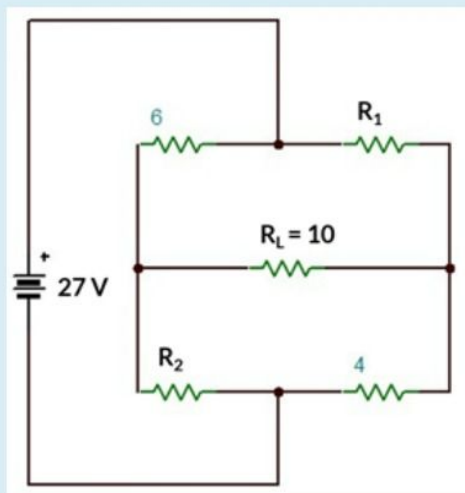question

Find the Thevenin's equivalent resistance (R_{th} in Ω) for the circuit shown in Figure below when $R_1 = 10.5 \Omega$ and $R_2 = 11.7 \Omega$. (All resistances are in Ω)



Select one:

- ☐ 3.43
- ☐ 13.73
- ☐ 20.59
- ☒ 6.86 ✓

Your answer is correct.



Question 3


Correct

Mark 2.00 out of

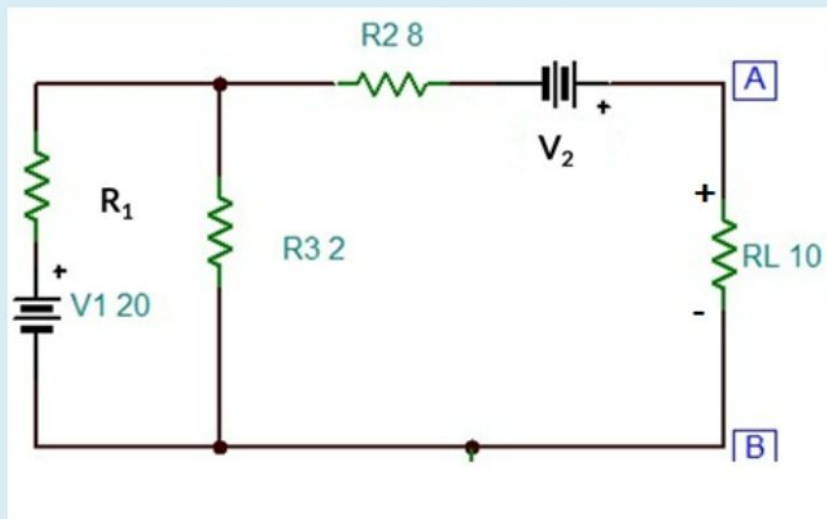2.00

 Flag
question

Find the voltage (in Volt) across the resistor R_L for the circuit shown below when $R_1 = 7\ \Omega$ and $V_2 = 14\text{ V}$. (All resistances are in Ω)



Answer: 9.432



The correct answer is: 9.432