

# CSET102

## Tutorial Sheet - 8 (Solutions)

SNO	Answers
1	<p>Given <math>I_D = 150 \mu A</math> <math>I_S = 10^{-11} A</math> <math>V_D = ?</math></p> $V_D = V_T \ln\left(\frac{I_D}{I_S} + 1\right) = \underline{0.43 V}$
2	<p>Given <math>I_D = -0.9 I_S</math> <math>V_D = ?</math></p> $-0.9 I_S = I_S \left( e^{\frac{V_D}{V_T}} - 1 \right) \quad V_T = 0.026 V = 26 mV$ $V_D = \underline{-0.06 V}$ <p>(<math>\because</math> in reverse bias <math>I_D</math> is opposite to that of original current direction)  <math>I_D = 0.9 I_S</math> results <math>V_D = +0.017 V</math> which is forward bias.</p>

3

$$V_D = 0.2 \text{ V} \quad I_D = I_S (e^{V_D/V_T} - 1) = 2192.4 I_S$$

$$V_D = -0.2 \quad I_D = -0.9995 I_S$$

$$\left| \frac{I_D @ 0.2 \text{ V}}{I_D @ -0.2 \text{ V}} \right| = \underline{2193.4}$$

4



Given  $V = 0.7 \text{ V}$

(i) Applying KVL,  $V_{R1} = 2 - 0.7 = 1.3 \text{ V}$

$V_{R2} = 0.7 \text{ V}$

$$V_{R2} = \frac{2 \cdot R_2}{R_1 + R_2} = 0.7 \text{ V}$$


$$R_2 = 0.35 R_1 + 0.35 R_2 \Rightarrow R_2 = \underline{538 \Omega}$$

ii)  $R_2 = 1 \text{ k}\Omega$


$$V_{R2} = 0.7 \text{ V} = \frac{2 \cdot R_2}{R_1 + R_2} \Rightarrow R_2 = 0.35 R_1 + 0.35 R_2$$

$$\Rightarrow R_1 = \underline{1.86 \text{ k}\Omega}$$


5

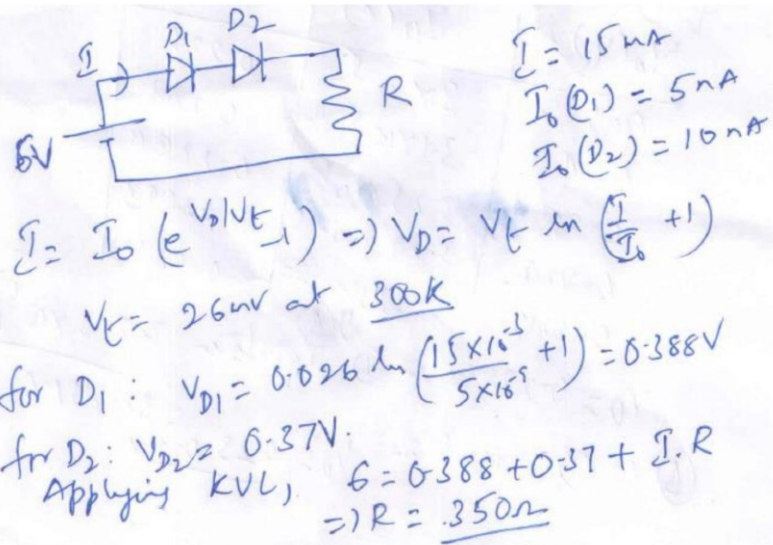


6

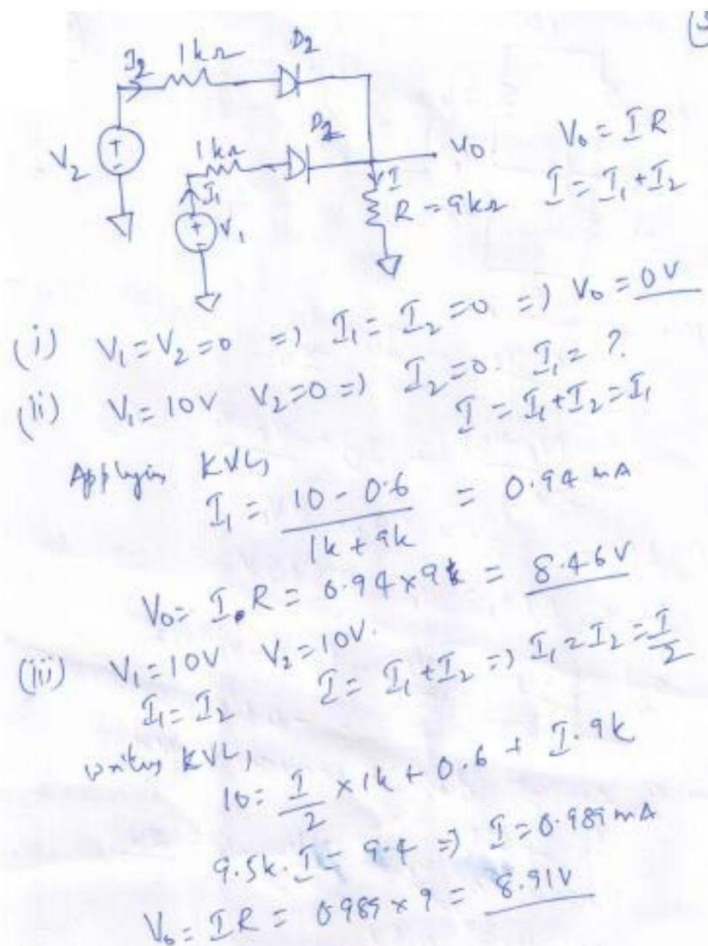


7)

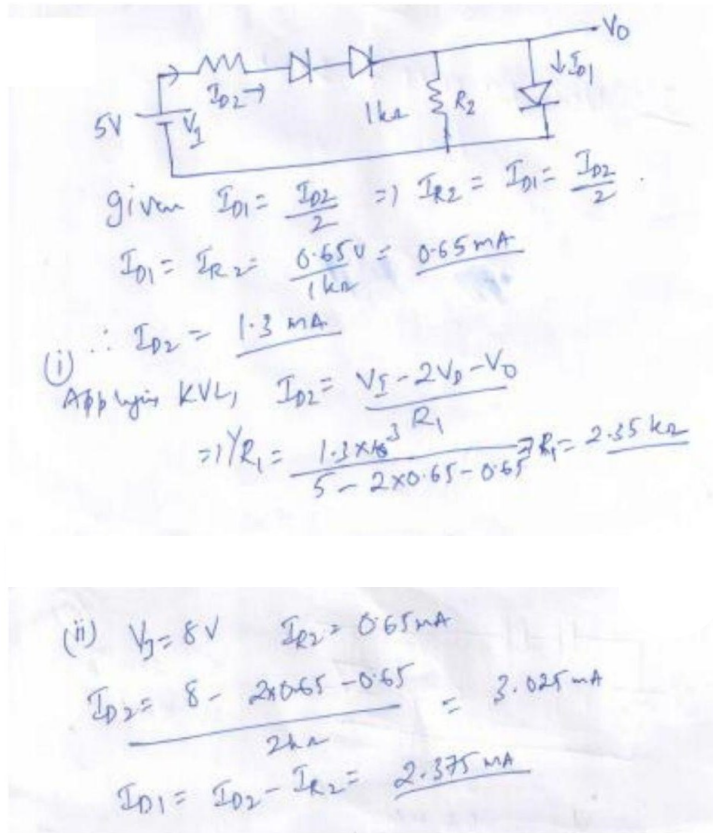

8)

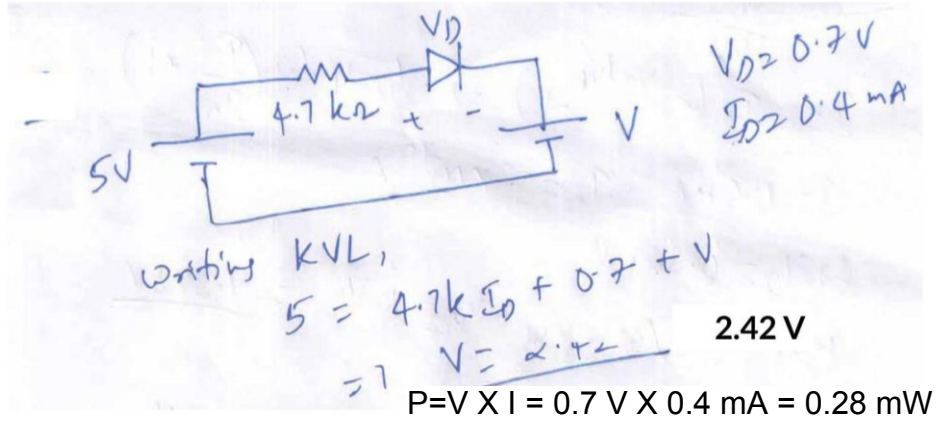


9)

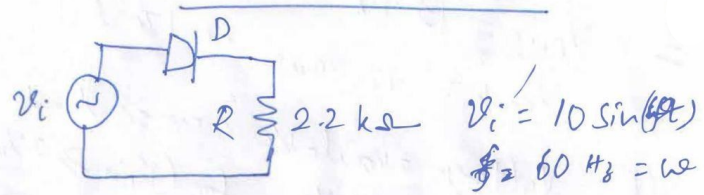


Ideal diode: no voltage drop in forward bias. So voltage drops across  $R$  entire voltage drops across  $D$  in reverse bias.

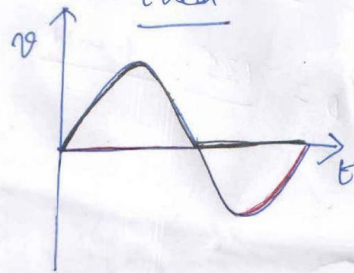Real diode,  $V_D$  is fixed at 0.7V (for Si)  
 when  $v_i \geq 0.7$  then  $V_D = v_i$   
ideal



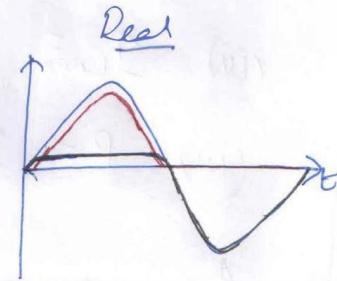—: input ( $v_i$ )  
 —:  $V_R$   
 —:  $V_D$



—:  $v_i$   
 —: across diode  
 —: across  $R$



10)

$$V_{RMS} = 120V$$

$$V_{peak} = \sqrt{2} V_{RMS} \sim 170V$$

(i) Voltage available across load  
 $V_{in} - 2V_D$  for  $(V_{in} \geq 2V_D)$   
 else 0


$$V_{Lmax} = 170 - 2 \times 0.6 = 168.8V$$

(ii) Each reverse biased diode should hold  
 a maximum of  $\frac{V_{Lmax}}{2} = \frac{168.8V}{2} = 84.4V$  in  
 reverse bias

$$(iii) I_{Lmax} = \frac{V_{Lmax}}{R} = \frac{168.8V}{1k\Omega} = 168.8mA$$

$$(iv) P = I_{Lmax} \cdot V_D = 135.04mW$$

11)

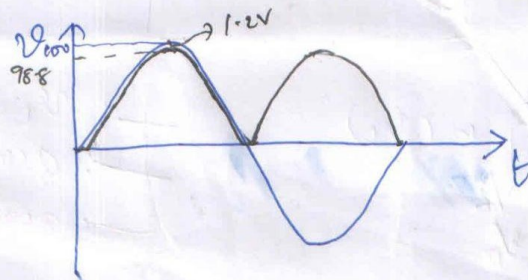

—:  $V_{in}$   
 —:  $V_R$