

Department of ECE, Bennett University

CSET102: Introduction to Electrical and Electronics Engineering


Tutorial Sheet-10

Topics Covered: Operational Amplifier


Note: In all these questions, $|V_{CC}| = |V_{EE}| = 15\text{ V}$.

Inverting Amplifier:

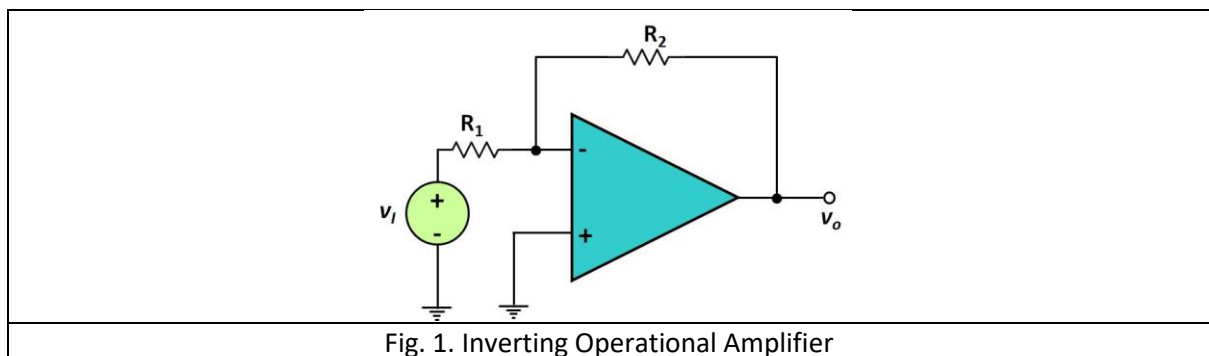- 1) Consider an inverting amplifier, as shown in fig. 1. If $R_1 = 1\text{ k}\Omega$ and $R_2 = 15\text{ k}\Omega$, find the output voltage if the input voltage is 0.5 V .
- 2) Consider an inverting amplifier, as shown in fig.1. If $R_1 = 0.5\text{ k}\Omega$ and the input voltage is 0.25 V . What is the maximum permissible value of the resistor R_2 ?
- 3) Consider an inverting amplifier, as shown in fig. 1. If $R_2 = 7.5\text{ k}\Omega$ and the input voltage is 0.25 V . What is the minimum permissible value of the resistor R_1 ?
- 4) Consider an inverting amplifier, as shown in fig. 1. If $R_1 = 1\text{ k}\Omega$ and $R_2 = 10\text{ k}\Omega$, what is the maximum permissible value of the voltage at the input?



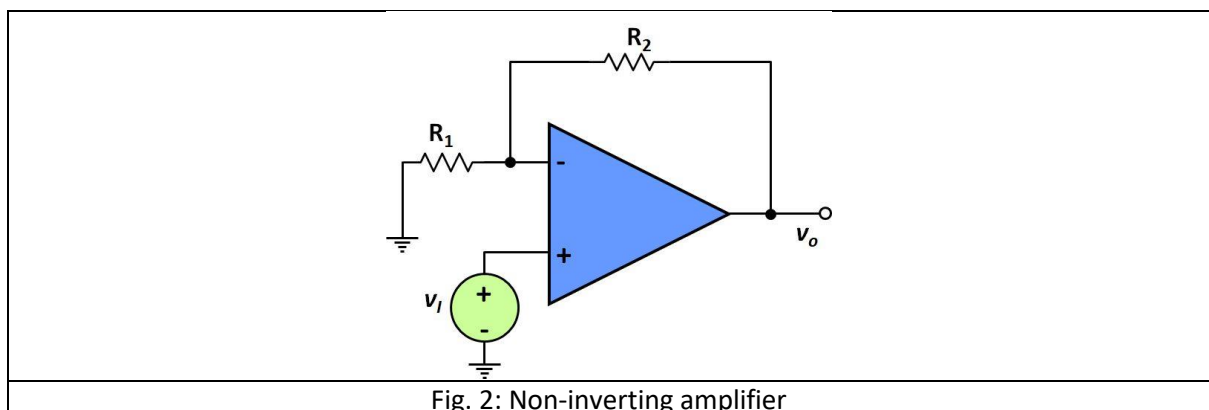- 5) Consider the non-inverting amplifier, as shown in fig. 2. Given that $R_1 = 1\text{ k}\Omega$, and $R_2 = 10\text{ k}\Omega$, find the output voltage if the input voltage is 0.5 V .
- 6) Consider the non-inverting amplifier, as shown in fig. 2. If $R_1 = 0.5\text{ k}\Omega$ and the input voltage is 0.25 V . What is the maximum permissible value of the resistor R_2 ?
- 7) Consider an inverting amplifier, as shown in fig. 2. If $R_2 = 7.5\text{ k}\Omega$ and the input voltage is 0.25 V . What is the minimum permissible value of the resistor R_1 ?
- 8) Consider an inverting amplifier, as shown in fig. 2. If $R_1 = 1\text{ k}\Omega$ and $R_2 = 15\text{ k}\Omega$, what is the maximum permissible value of the voltage at the input?



9) Consider a summing amplifier shown in fig. 3. Given that $R_1 = 1 \text{ k}\Omega$, $R_2 = 1.5 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, and $R_F = 10 \text{ k}\Omega$. If $v_{I1} = 0.5 \text{ V}$, $v_{I2} = 0.75 \sin(60\pi t)$ and $v_{I3} = 1.0 \sin(30\pi t)$, find the output voltage?

10) Consider a summing amplifier shown in fig. 3. Given that the gain of the amplifier is 5. If $v_{I1} = 0.25 \text{ V}$, $v_{I2} = 0.75 \sin(60\pi t)$ and $v_{I3} = 1.2 \sin(30\pi t)$. Find the output voltage.

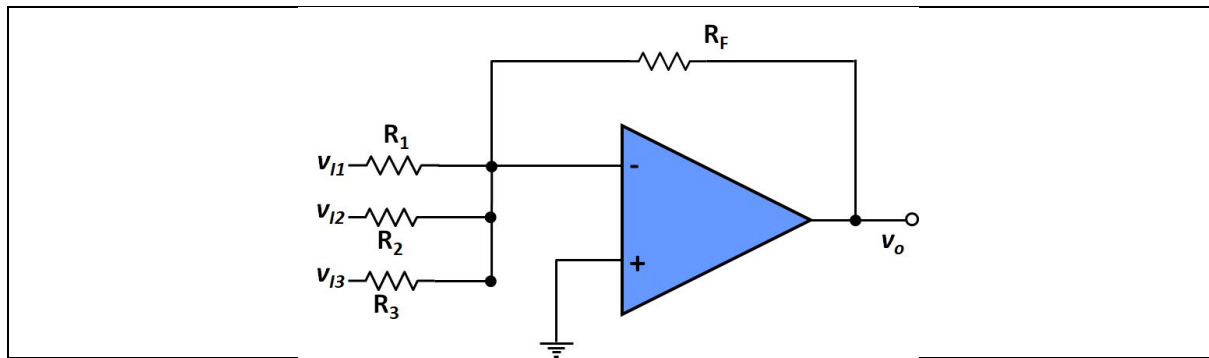


Fig. 3: Summing amplifier

11) Consider the difference amplifier shown in fig. 4. Find the output voltage when $V_{I1} = 0.5 \text{ V}$, $V_{I2} = 0.55 \text{ V}$, $R_1 = 1 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_3 = 3 \text{ k}\Omega$ and $R_4 = 9 \text{ k}\Omega$.

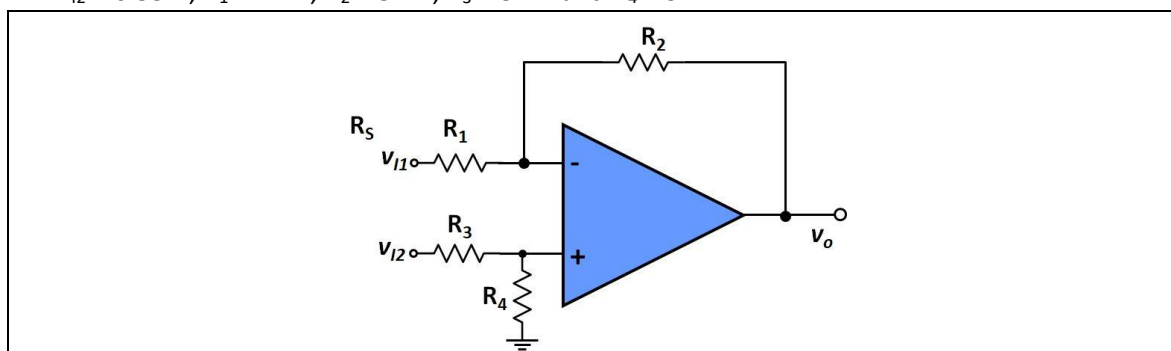


Fig. 4: Difference Amplifier

12) Consider the circuit shown in fig. 5. The input voltage v_s is given by $v_s = 1.0 \sin(120\pi t)$. What will be the output voltage. Given $R = 1 \text{ k}\Omega$ $C = 1 \mu\text{F}$.

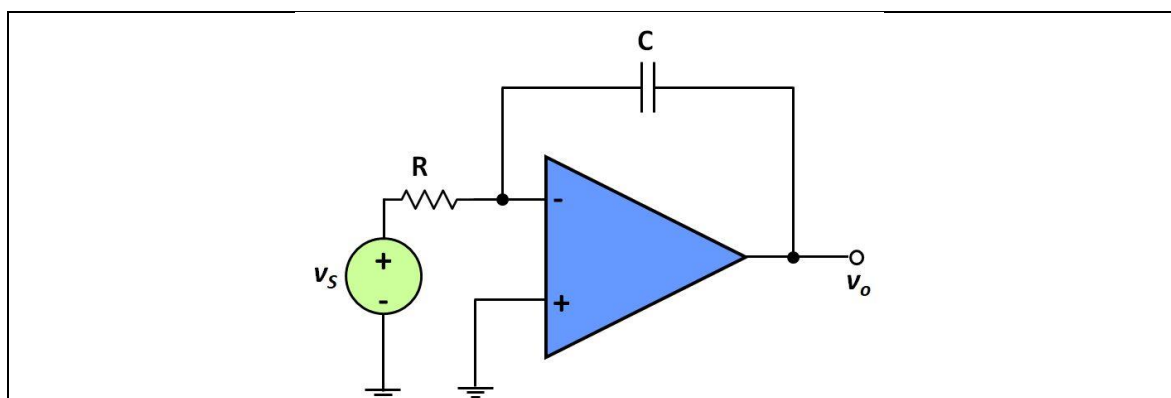


Fig. 5: Operational Amplifier Integrator

- 13) Consider the circuit shown in fig. 6. The input voltage v_s is given by $v_s = 1.0 \sin(120\pi t)$. What will be the output voltage. Given $R = 1 \text{ k}\Omega$ $C = 1 \text{ }\mu\text{F}$.

