

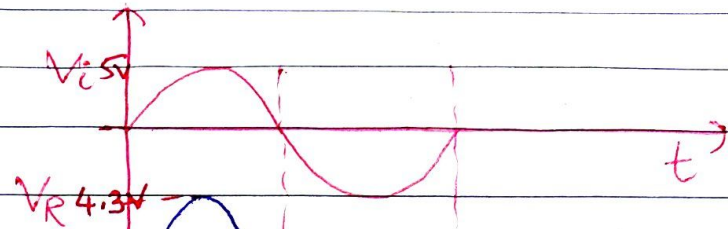


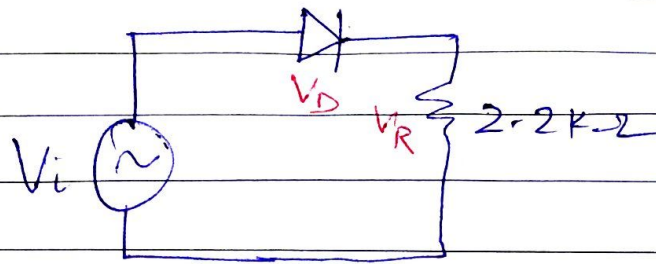Q1. Solution Given  $V_i = 5 \sin 60t$ ,  $V_D = 0.7V$ ,  $R_L = 2.2k\Omega$



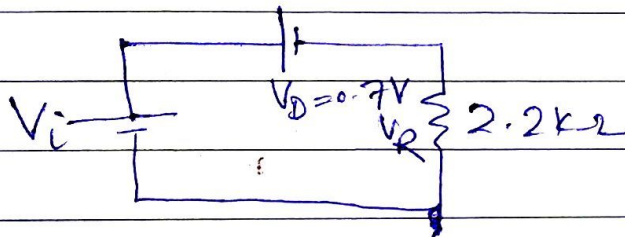
→ When diode is forward biased during positive half cycle of input waveform, the equivalent circuit is



Here  $V_D = 0.7$

$$V_R = V_i - V_D = (V_i - 0.7)V$$

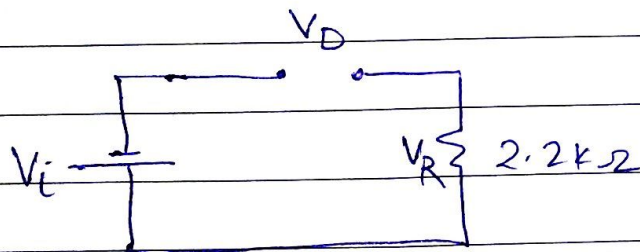
→ During negative half cycle of input waveform, diode is reverse biased. The equivalent circuit is



Here  $I = 0$ ,  $V_R = I \times 2.2 = 0$

$$V_D = V_i$$

Q2

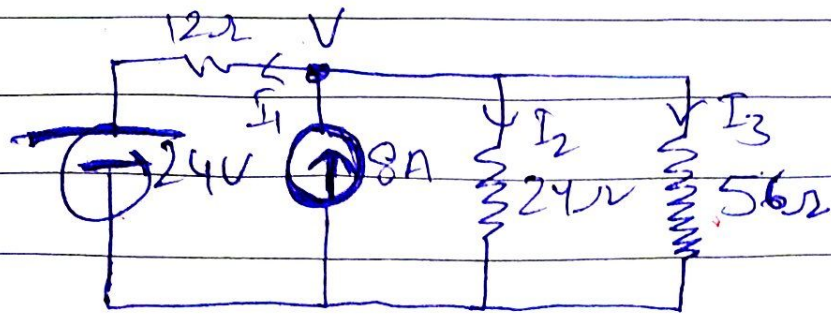

4	12, 24, 56
3	3, 6, 14
2	1, 2, 14
	1, 1, 7

$$\frac{V-24}{12} + \frac{V}{24} + \frac{V}{56} = 8$$

$$LCM = 4 \times 3 \times 2 \times 7$$

$$\frac{14(V-24) + 7V + 3V}{168} = 8$$

$$= 12 \times 14 = 168$$

$$14V - 336 + 10V = 8 \times 168 = 1344$$

$$24V = 1344 + 336 = 1680$$

$$V = \frac{1680}{24} = 70 \rightarrow \textcircled{3}$$

$$I_1 = \frac{70-24}{12} = \frac{46}{12} = 3.833 \text{ A}$$




superposition

$$I_2 + \frac{24 \times 56}{24+56} = 28.8$$

3.833

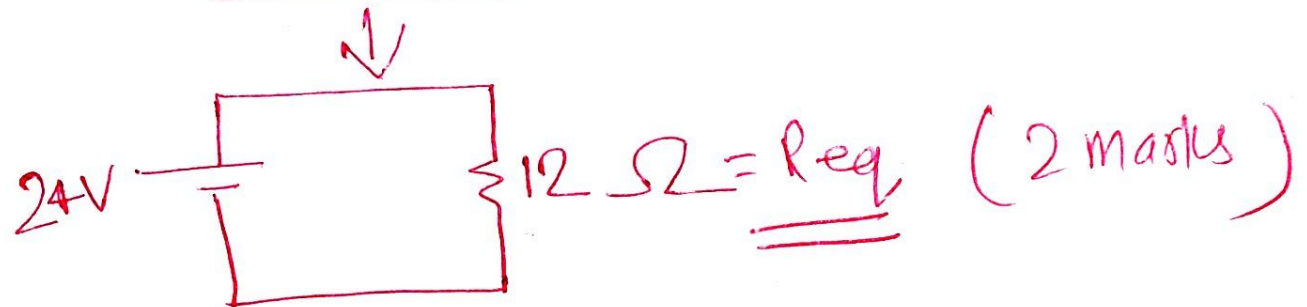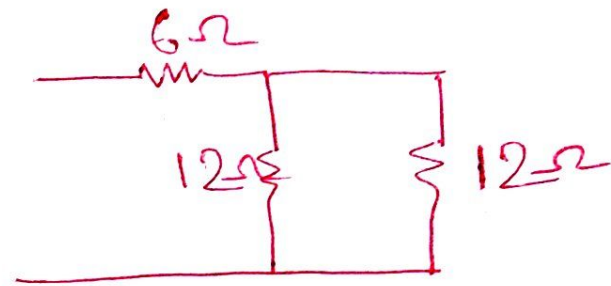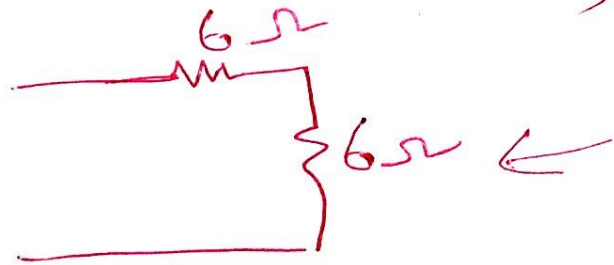Q 4. Solution

$$\frac{1}{R_{eq}} = \frac{1}{6\Omega} + \frac{1}{12\Omega} = \frac{3}{12} = \frac{1}{4\Omega}$$





$$I = 2 \underline{A}$$

$$P = 4 \times 12 = \underline{48} \text{ W} \quad (2 \text{ marks})$$




Q3

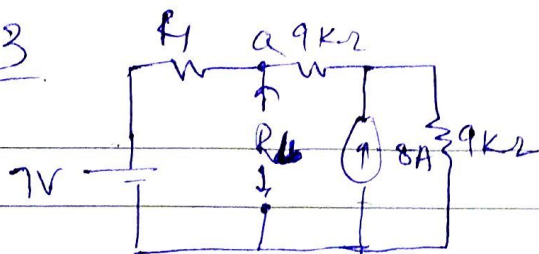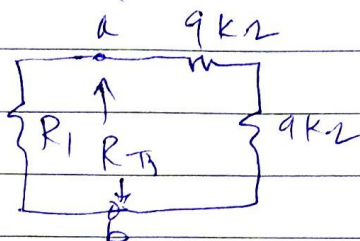For  $R_{Th}$ 

For max. power transfer

$$R_L = R_{Th}$$

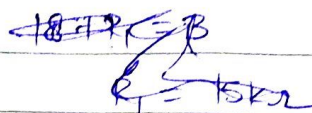


$$\frac{R_1 \times 18}{18 + R_1} = 3$$

$$18R_1 = 54 + 3R_1$$

$$15R_1 = 54$$

$$R_1 = \frac{54}{15} = 3.6 \text{ k}\Omega$$
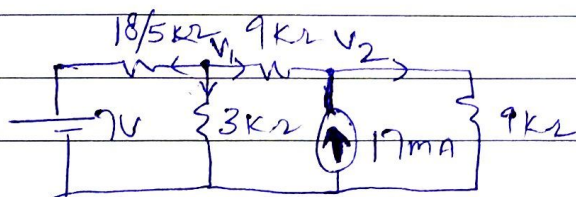
$$\frac{18}{5} = 3.6 \text{ k}\Omega = R_1 \quad (2 \text{ marks})$$



$$V_1 - 7 + \frac{V_1}{3} + \frac{V_1 - V_2}{9} = 0$$

$$3(V_1 - 7) + 3.6V_1 + 1.2(V_1 - V_2) = 0$$

$$3V_1 - 21 + 3.6V_1 + 1.2V_1 - 1.2V_2 = 0$$

$$7.8V_1 - 1.2V_2 = 21 \quad (1)$$

$$\frac{V_1 - V_2}{9} + 17 = \frac{V_2}{9}$$

$$\frac{V_1 - V_2}{9} - \frac{V_2}{9} = -17$$

$$\frac{V_1 - V_2 - V_2}{9} = -17$$

$$V_1 - 2V_2 = -153 \quad (2)$$

$$7.8V_1 - 15.6V_2 = -1193.4$$

$$7.8V_1 - 1.2V_2 = 21$$


$$-14.4V_2 = -1214.4$$

$$V_2 = 84.33$$

$$V_1 = 2V_2 - 153 = 2 \times 84.33 - 153 = 15.66 \text{ V}$$


Students may apply  
superposition also

Q.5

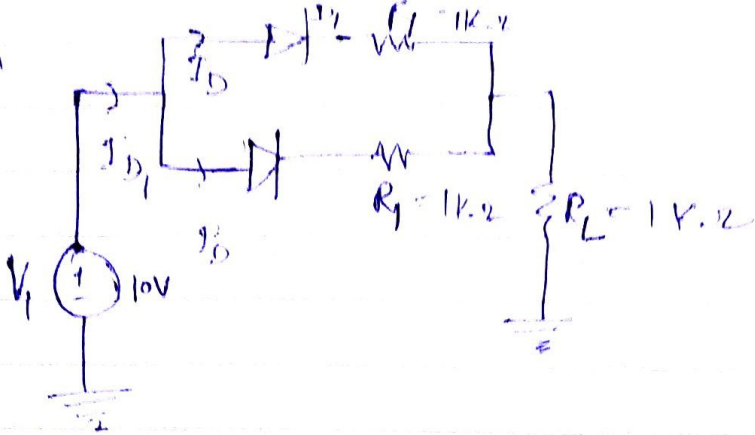

$$I_{D1} = I_{D2} \Rightarrow I_{D1} = 2I_{D2}$$

$D_1$  is F.B.

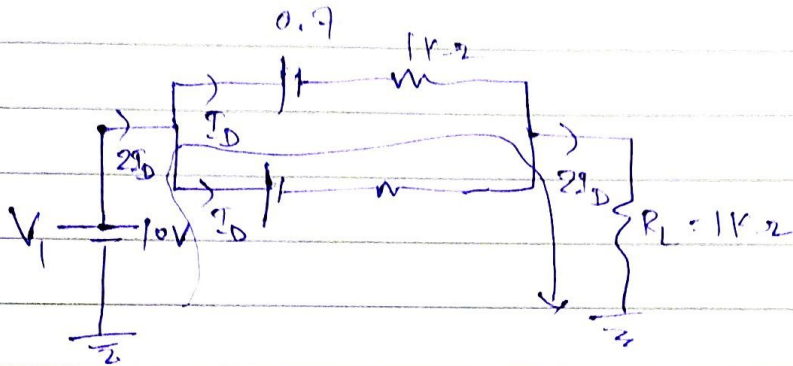


$$-10 + 0.7 + I_{D1} + 2I_{D2} = 0$$

$$3I_{D2} = 10 - 0.7 = 9.3$$

$$I_{D2} = \frac{9.3}{3} = 3.1 \text{ mA}$$

$$I_{D1} = 3.1 \text{ mA}$$

Q.6

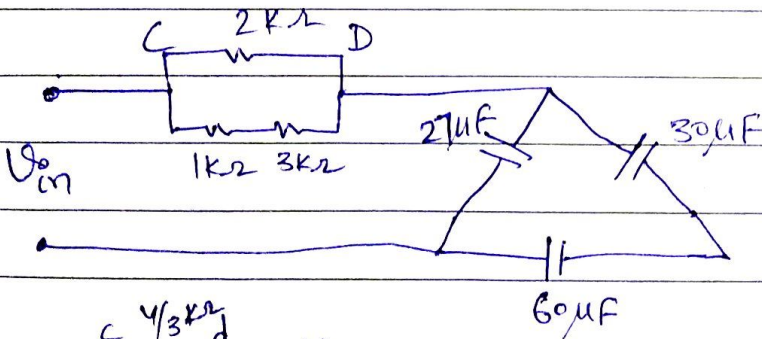

$$C_{eq} = 27 + \frac{30 \times 60}{30 + 60}$$

$$= 27 + \frac{1800}{90}$$

$$C_{eq} = 47 \mu F$$

$$R_{eq} = \frac{4 \times 2}{63} = \frac{4}{3} \text{ k}\Omega$$

$$H(j\omega) = \frac{4}{3} \times \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega RC}}$$



$$H(j\omega) = \frac{1}{1 + \frac{1}{j\omega RC}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC}\right)^2}}$$

$$|H(0)| = \frac{1}{\sqrt{1 + \frac{1}{0}}} = \frac{1}{\infty} = 0$$

$$|H(\infty)| = \frac{1}{\sqrt{1 + \frac{1}{\infty}}} = 1$$

1

It is HPF.


$$f_c = \frac{1}{2\pi RC} = \frac{1}{2 \times 3.14 \times 47 \times 10^{-6} \times 10^3}$$

$$f_c = \frac{10^3}{393.55} = 2.541 \text{ Hz}$$

$$f_c = 2.541$$

1


7

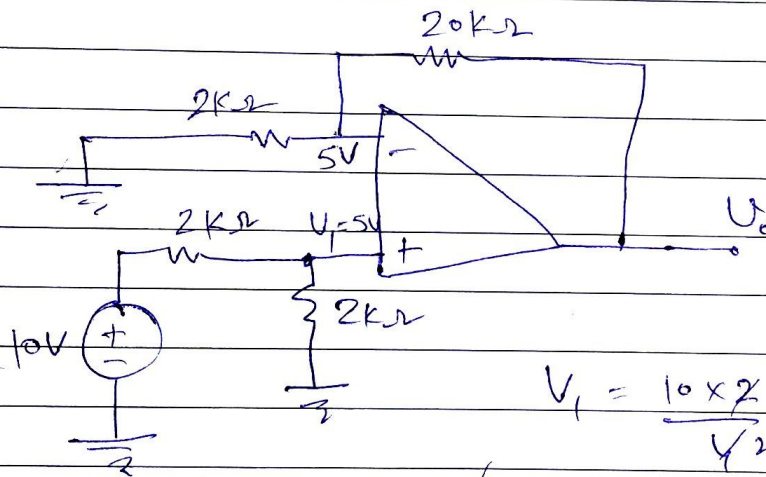

$$V_1 = \frac{10 \times 2}{4} = 5V$$

$$V_o = \left(1 + \frac{R_f}{R_1}\right) \cdot V_1 = \left(1 + \frac{20}{2}\right) 5$$

$$V_o = 11 \times 5 = 55V$$

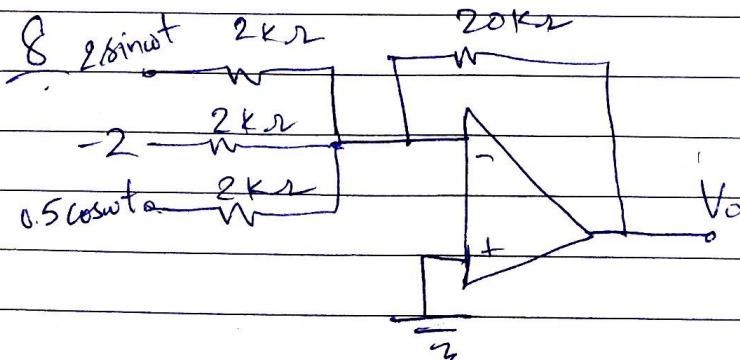

$$V_o = -\frac{R_f}{R_1} (V_1 + V_2 + V_3)$$

$$= -\frac{20}{2} (2 \sin \omega t - 2 + 0.5 \cos \omega t)$$

$$V_o = -20 \sin \omega t + 20 - 5 \cos \omega t$$