

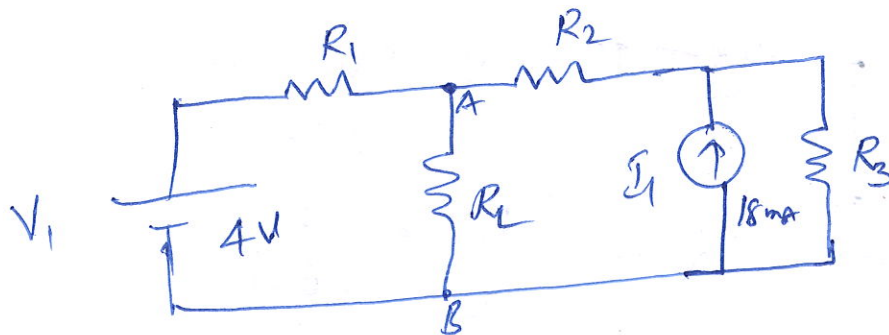


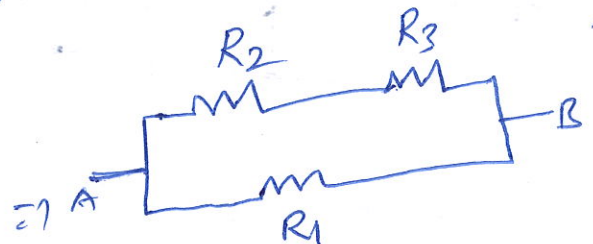- 1) For the circuit shown below, calculate the value of P_{R_L} (in mW) such that the power delivered to the resistor is maximized.



$$\begin{aligned} R_2 &= 7 \text{ k}\Omega \\ R_3 &= 9 \text{ k}\Omega \\ R_L &= 2 \text{ k}\Omega \end{aligned}$$

To find R_{TH} between A and B nodes:

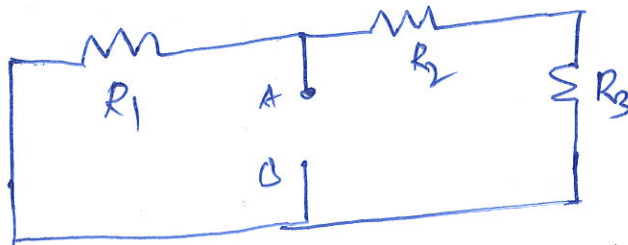


$$R_{TH} = R_1 \parallel (R_2 + R_3)$$

$$R_{TH} = R_L = 2 \text{ k}\Omega = R_1 \parallel (16 \text{ k}\Omega)$$

$$\frac{1}{2} = \frac{1}{R_1} + \frac{1}{16} \quad \frac{1}{R_1} = \frac{1}{2} - \frac{1}{16} = \frac{14}{2 \times 16}$$

$$R_1 = \frac{16}{7} \text{ k}\Omega$$

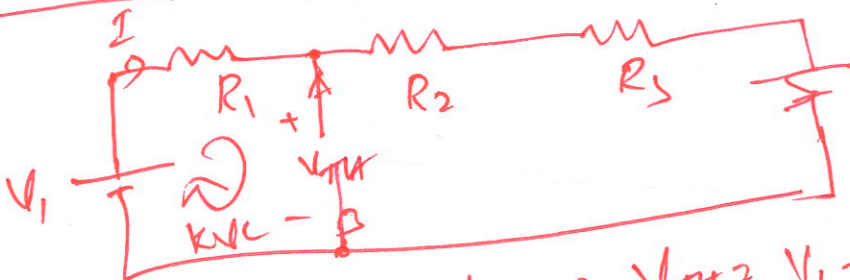To find V_{TH} : Use source transformation.



$$I = \frac{4 - 18 \text{ mA} \times 9 \times 10^3}{\left(\frac{16}{7} + 7 + 9\right) \text{ k}} \quad I \cdot R_3$$


$$\text{KVL} \quad V_1 = I R_1 + V_{TH} \Rightarrow V_{TH} = V_1 - I R_1 = 95 \text{ V} = -8.64 \text{ mA}$$

$$R_L = R_{TH} = 2 \text{ k}\Omega$$

$$P_{R_L} = \frac{V_{TH}^2}{4 R_L} = 70.51 \text{ mW}$$

2) $E_g = \frac{hc}{\lambda} = \frac{6.626 \times 10^{-34} \times 3 \times 10^8}{594 \times 10^9 \times 1.6 \times 10^{-19}} = 2.092 \text{ eV}$

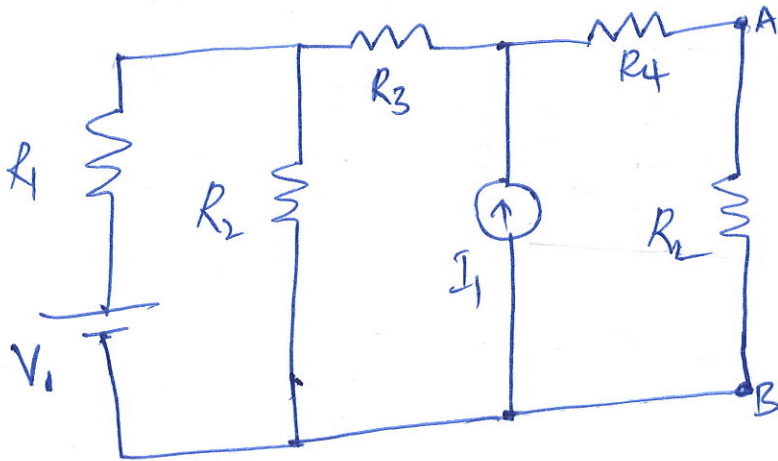3) For the circuit given below, find the voltage across the current source I_1 .



$V_1 = 5 \text{ V}$

$I_1 = 0.3 \text{ A}$

$R_1 = 66 \Omega$

$R_2 = 146 \Omega$

$R_3 = 239 \Omega$

$R_4 = 89 \Omega$

$R_5 = 282 \Omega$


Source transformation between V_1, R_1 :

$I_{11} = \frac{5}{66} = 75.76 \text{ mA}$

$R_1 || R_2 = \frac{66 \times 146}{66 + 146} = 45.45 \Omega$

} Source transformation

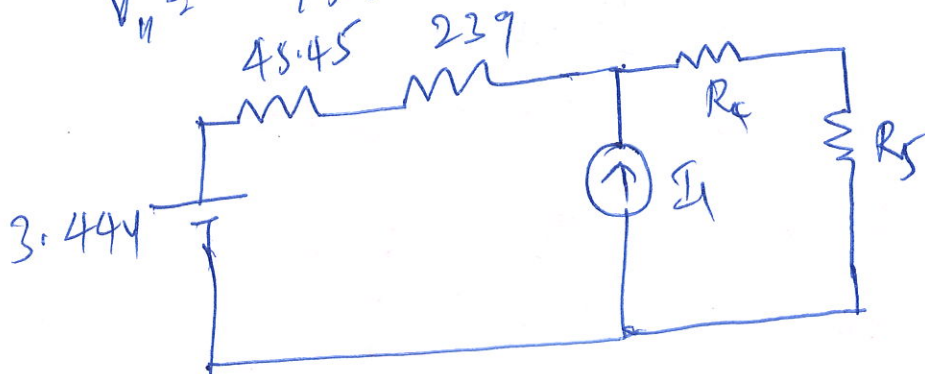
$V_{11} = \frac{75.76 \times 45.45 \times 10^{-3}}{239} = 23.44 \text{ V}$



Source transformation:

$I_{12} = \frac{3.44}{45.45 + 239} = 12.10 \text{ mA}$

3

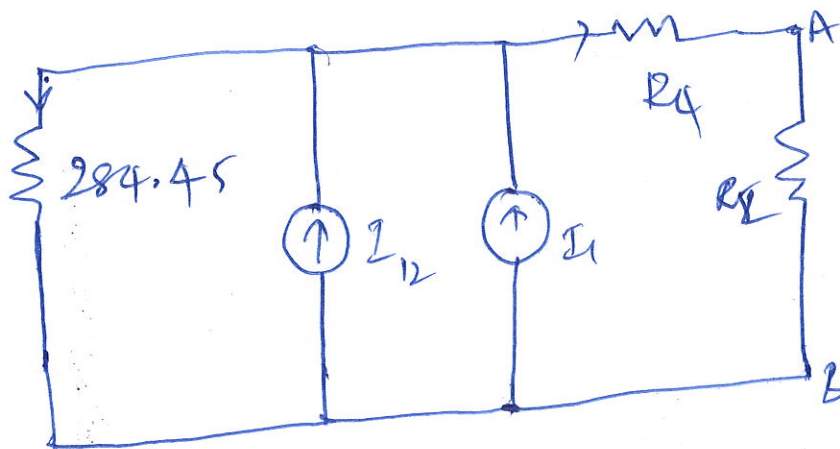


$$R_4 + R_2 = 371 \Omega$$

$$I_1 + I_2 = 0.3121 \text{ A}$$

$$I_{R_4+R_2} = 0.3121 \times \frac{284.45}{371 + 284.45} = 0.135 \text{ A}$$

$$V_{R_4+R_2} = V_{R_2} = 0.135 \times 371 = 50.25 \text{ V}$$

4)

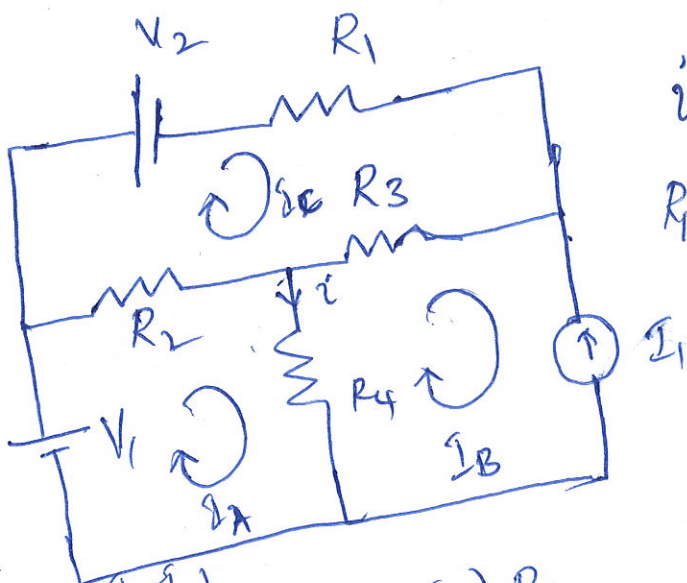

$$I = \frac{?}{?} \text{ mA}$$

$$R_1 = 7 \text{ k}\Omega \quad R_3 = 7 \text{ k}\Omega$$

$$R_2 = 4 \text{ k}\Omega \quad R_4 = 4 \text{ k}\Omega$$

$$V_1 = 8 \text{ V} \quad V_2 = 6 \text{ V}$$

$$I_1 = 4 \text{ mA}$$

$$I_B = -I_1 = -4 \text{ mA}$$

$$V_1 = (I_1 R_1 + (I_1 - I_4) R_4 + (I_1 - I_3) R_3 + I_2 R_2)$$

$$-V_2 = I_2 R_2 + (I_2 - I_3) R_3 + R_2 (I_2 - I_1)$$


$$8 = 4 I_1 - 4 I_2 + 4 I_3 + 4.4$$

$$8 I_1 - 4 I_2 = -8 \quad \text{--- (1)}$$

$$+4 I_1 + 18 I_2 = -6 - 28 = -34 \quad \text{--- (2)}$$

$$I_A = -\frac{35}{16} \text{ mA} \quad I_C = -\frac{17}{8} \text{ mA}$$
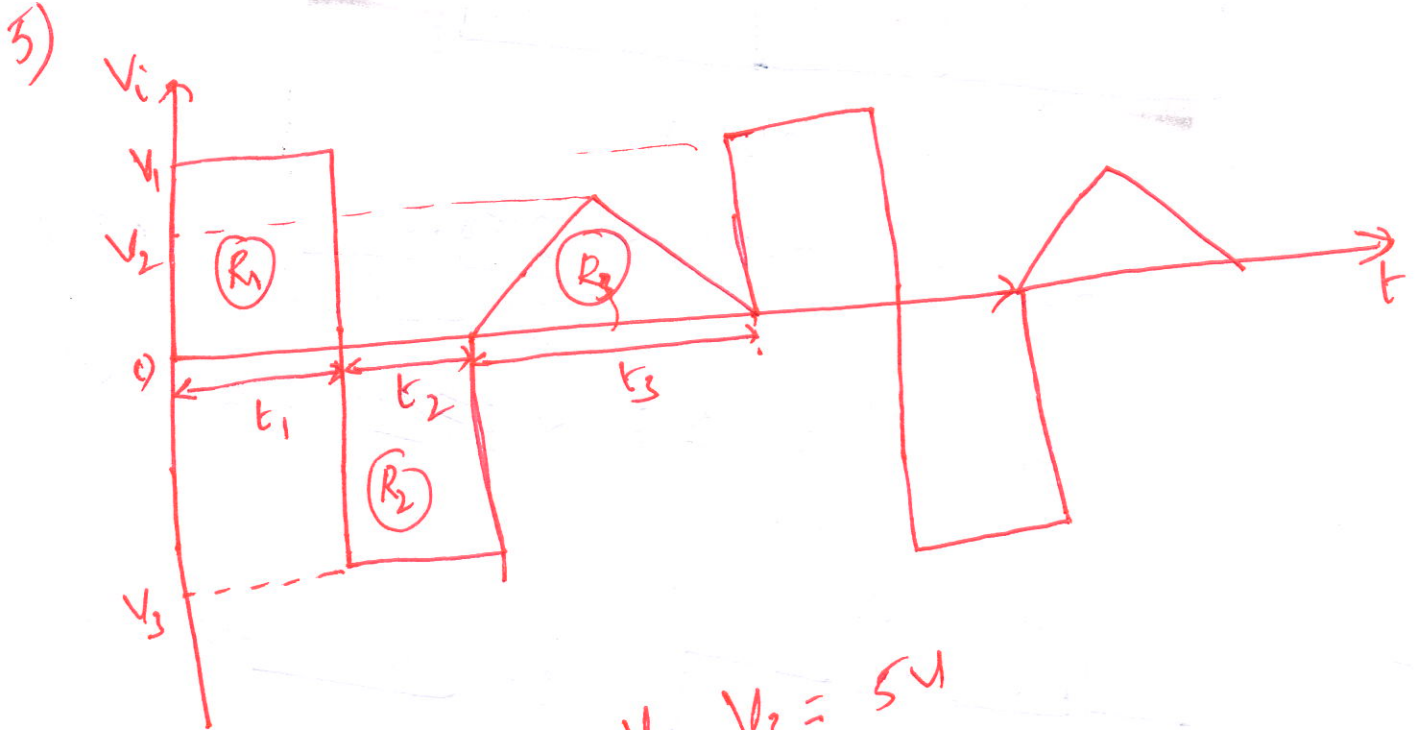
$$i = I_A - I_B = -\frac{35}{16} + 4 = \underline{1.8125 \text{ mA}}$$




$$V_1 = 12 \text{ V} \quad V_2 = 4 \text{ V} \quad V_3 = 5 \text{ V}$$

$$t_1 = 6 \text{ s} \quad t_2 = 3 \text{ s} \quad t_3 = 6 \text{ s}$$

$$\text{Avg Value} = \frac{12 \times 6 + (-5) \times 3 + \frac{1}{2} \times 4 \times 6}{6 + 3 + 6} = 4.6 \text{ V}$$
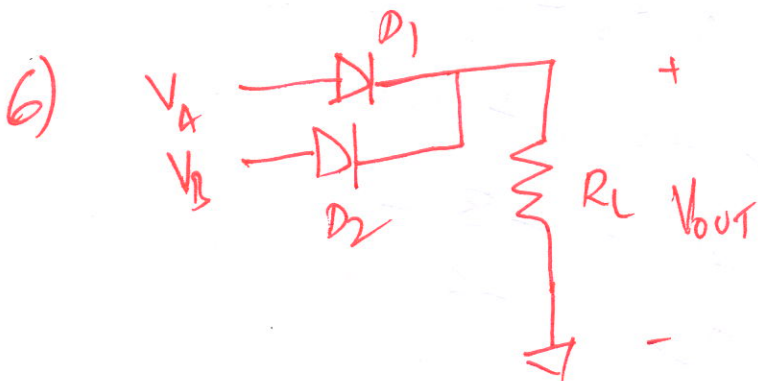
$$\text{Peak Amplitude} = 12 - 4.6 = \underline{7.4 \text{ V}}$$



$$R_L = 1240 \Omega$$

$$V_A = 9.6 \text{ V}$$


$$V_B = 7.7 \text{ V}$$

5

$$I_R = \frac{9.6 - 0.3 + 7.7 - 0.3}{1240} = 13.47 \text{ mA}$$

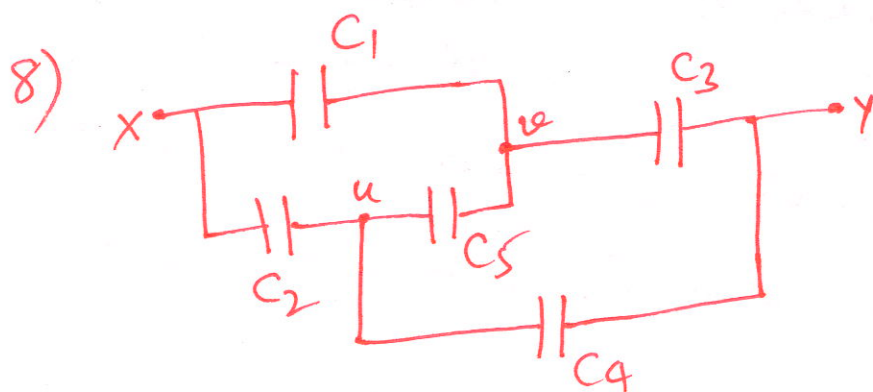
7)

$$f_c = \frac{R}{2\pi L} \Rightarrow L = \frac{R}{2\pi f_c} = \frac{3.3 \text{ k}\Omega}{2\pi \times 54 \text{ kHz}} = 9.73 \text{ nH}$$




$$C_i = C$$

redrawing the circuit,

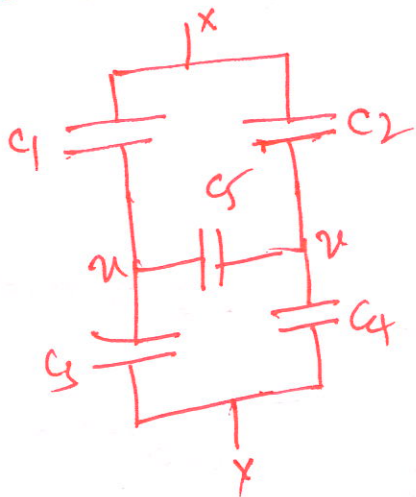

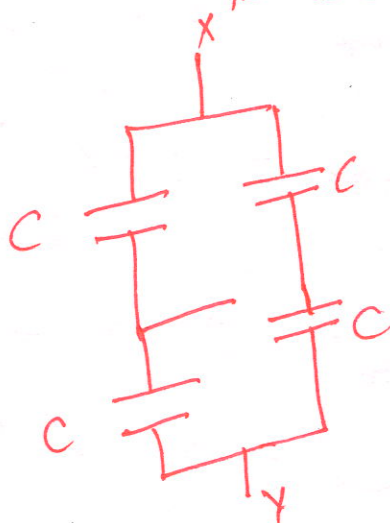Since $C_i = C$, u, v acts like open. redrawing the circuit,




$$\Rightarrow C_{XY} = C$$

$$C = 123 \text{ pF}$$

9)

6

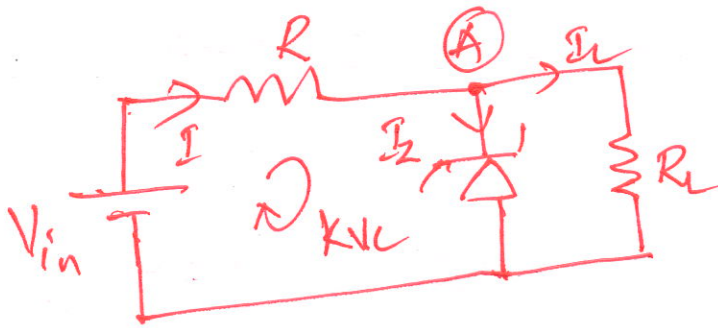

$$R_L = 5 \text{ k}\Omega$$

$$V_Z = 53 \text{ V}$$

$$V_{L2} \quad V_Z = 53 \text{ V} \quad I_{L2} = \frac{V_L}{R_L} = \frac{53}{5\text{k}} = 10.6 \text{ mA}$$

Apply KVL at node A,

$$V_{in, \min} = 178 \text{ V}$$

$$V_{in, \max} = 232 \text{ V}$$

$$I = I_Z + I_L$$

$I_{Z, \max}$ happens when I is max., when V_{in} is max.

$I_{Z, \min}$ happens when I is min., when V_{in} is min.

Apply KVL,

$$V_{in} = IR + V_Z$$

$$I = \frac{V_{in} - V_Z}{R}$$

$$I_{\min} = \frac{178 - 53}{6\text{k}} = 20.833 \text{ mA}$$


$$I_{\max} = \frac{232 - 53}{6\text{k}} = 29.833 \text{ mA}$$

$$I_{Z, \max} = 29.833 - 10.6 = 19.23 \text{ mA}$$

$$I_{Z, \min} = 20.833 - 10.6 = 10.23 \text{ mA}$$


10)

(7)

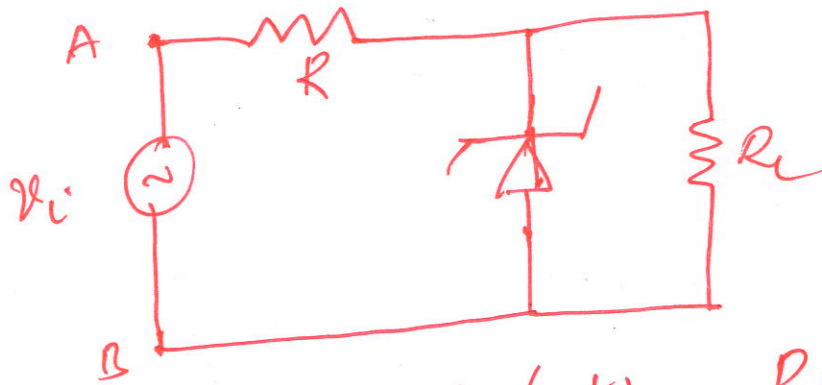

$v_i = 19.3 \sin(\omega t)$ $R \ll R_L$
 negative half cycle, $V_{R_L} = 0.7V$
 positive half cycle, $V_{R_L} = V_2 = \underline{3.7V}$

11)

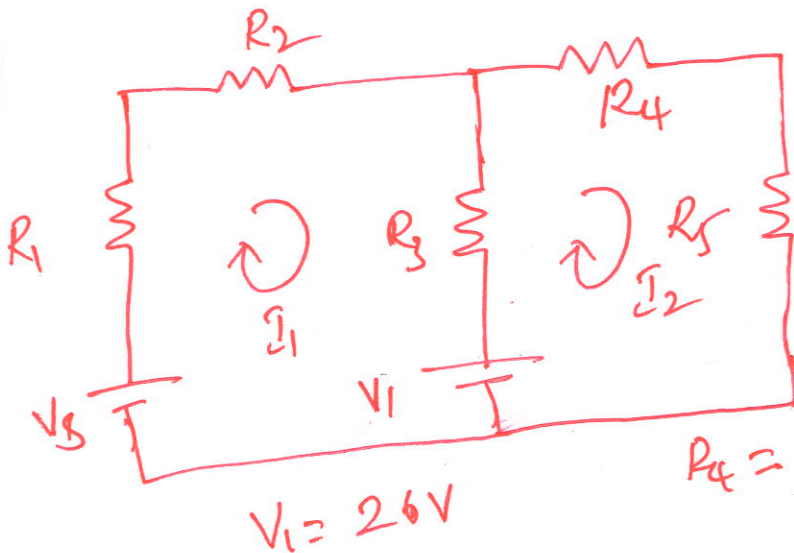

$I_2 = 11 \text{ mA}$
 $R_1 = 1412 \Omega$
 $R_2 = 748 \Omega$
 $R_3 = 2234 \Omega$
 $R_4 = 3492 \Omega$ $R_5 = 1384 \Omega$

In Mesh 1;

$$V_S = I_1 R_1 + I_2 R_2 + R_3 (I_1 - I_2) + V_1$$

$$4994 I_1 - 24.574 + 26 = V_S$$

$$4994 I_1 + 1.426 = V_S \quad \text{--- (1)}$$

In Mesh 2,

$$V_1 = R_3 (I_2 - I_1) + I_2 (R_4 + R_5)$$

$$26 = 78.21 - 2234 \cdot I_1$$

$$I_1 = 23.37 \text{ mA} \quad (2)$$

(8)

Substitute I_1 in (1), $V_S = 104.114 \text{ V}$

$$V_S = 113.88 \text{ V}$$

$$\text{Power} : \underline{2433 \text{ mW}}$$