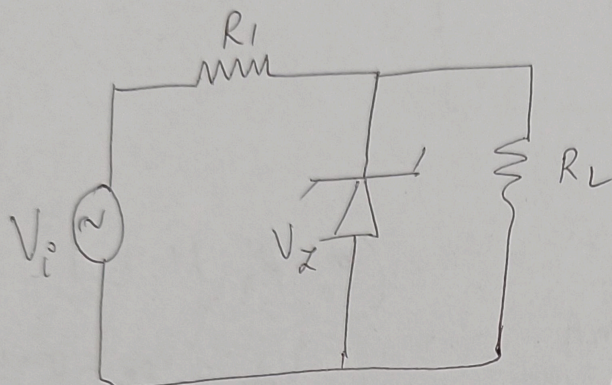


Quiz 5 Solutions

①



$$V_i = 14.4 \sin(\omega t)$$

Since  $V_Z = 7.4V$

at the output  $\rightarrow$  in positive half cycle  $V_{out} = V_Z = 7.4V$

in negative half cycle  $\rightarrow$  Zener diode is forward biased & it behaves as a PN Junction diode, so  $V_{out} = 0.7V$  (Cut in voltage of diode)

②


$$I_d = I_s \left[ e^{\frac{V_d}{nV_t}} - 1 \right]$$

$$= 59 \times 10^{-15} \left[ e^{\frac{0.65}{0.026}} - 1 \right]$$

$$I_d = 4.81 \text{ mA}$$



③

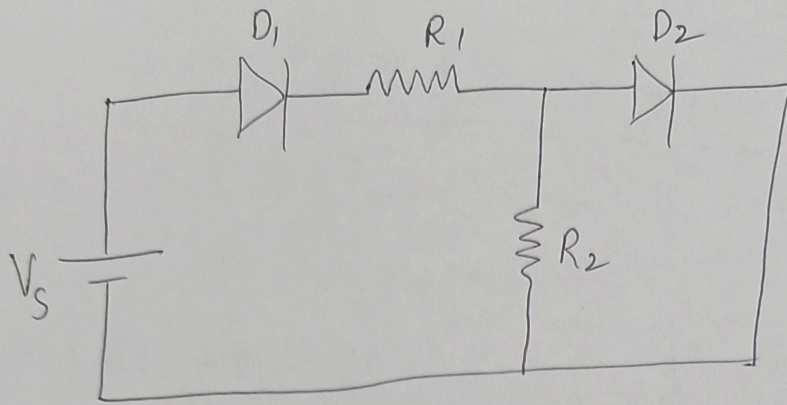


$$R_2 = \frac{V_{R_2}}{I_{R_2}} = \frac{0.7V}{12mA}$$

( $\because R_2 \parallel D_2$ )

$$V_{R_2} = V_{D_2} = 0.7V$$

$$R_2 = 58.33 \Omega$$

④

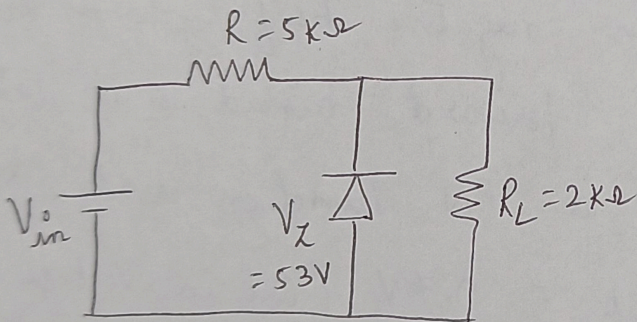

$$I_{dmax} = ?$$

$$I_{dmin} = ?$$

$$V_{in} = 170 - 230V$$

$$V_{R_L} = V_Z = 53V \Rightarrow \underline{I_{R_L}} = \frac{V_{R_L}}{R_L} = \frac{53}{2K} = \underline{26.5mA}$$

$$V_{in} = V_R + V_Z \Rightarrow V_{in,min} = V_{R,min} + V_Z \Rightarrow V_{R,min} = 170 - 53 = \underline{117V}$$

$$V_{in,max} = V_{R,max} + V_Z \Rightarrow V_{R,max} = 230 - 53 = \underline{177V}$$

$$I_{R,min} = \frac{V_{R,min}}{R} = \frac{117}{5K} = \underline{23.4mA}$$

$$I_{R,max} = \frac{V_{R,max}}{R} = \frac{177}{5K} = \underline{35.4mA}$$

$$I_R = I_Z + I_{R_L} \Rightarrow I_Z = I_R - I_{R_L} \Rightarrow \underline{I_{Z,max}} = I_{R,max} - I_{R_L} = \underline{8.9mA}$$

$$\underline{I_{Z,min}} = I_{R,min} - I_{R_L} = \underline{-3.1mA}$$