

Question 1

Incorrect


Mark 0.00 out of

2.00



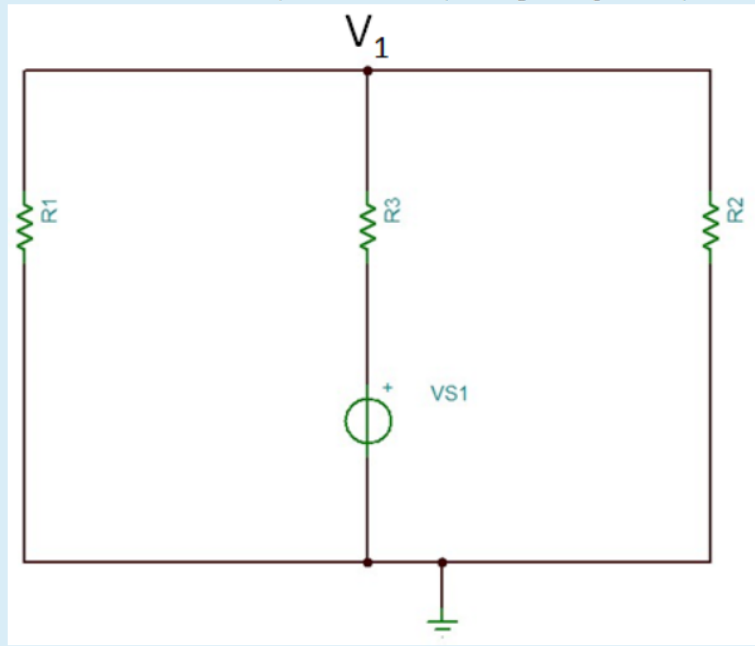question

In the following circuit, Find V_1 in Volts. Given $R_1=9\ \Omega$, $R_2=6\ \Omega$, $R_3=6\ \Omega$, $VS_1=9\text{ V}$.



Answer:



The correct answer is: 3.38

Question 2

Correct


Mark 1.50 out of

1.50



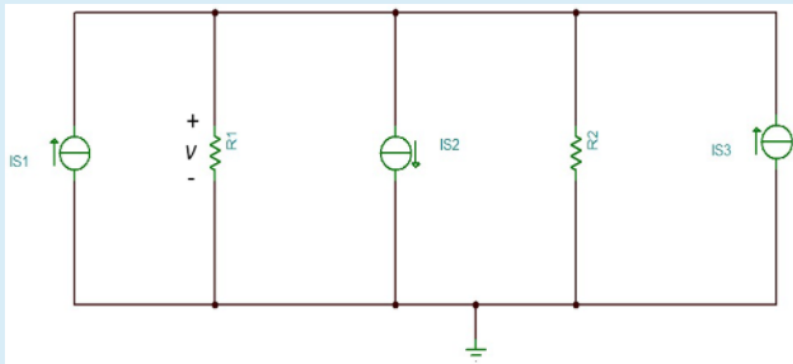question

In the following circuit, find voltage v in Volt across R_1 . Given $R_1=8\ \Omega$, $R_2=9.1\ \Omega$, $I_{S1}=6\text{ A}$, $I_{S2}=7\text{ A}$, $I_{S3}=12\text{ A}$.



Answer: 46.816



Question 3

Incorrect


Mark 0.00 out of

1.50



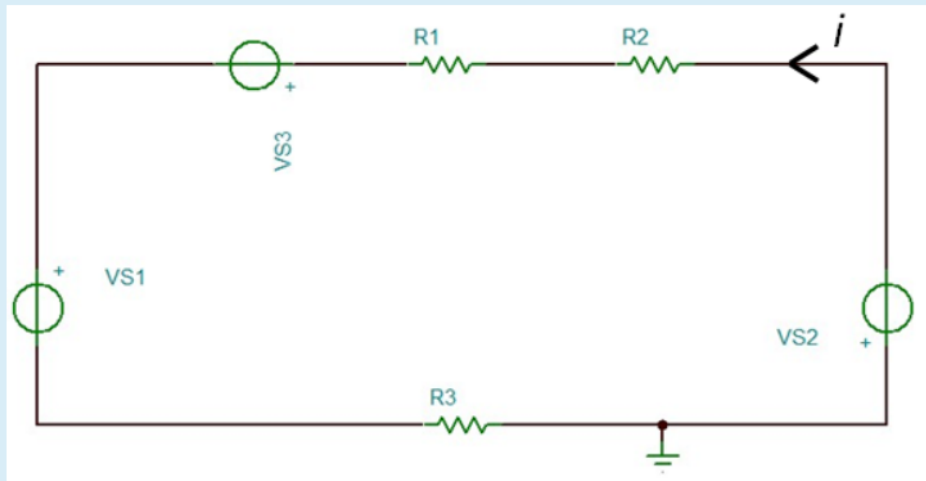question

In the following circuit, Find current i in mA. Given $R_1=24\ \Omega$, $R_2=23\ \Omega$, $R_3=40\ \Omega$, $V_{S1}=5\text{ V}$, $V_{S2}=9\text{ V}$, $V_{S3}=9\text{ V}$.



Answer:



The correct answer is: -264.36782