



Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2021-2025 > Semester-II Cohort 2021-25  
> CSET105(EVEN SEMESTER 2021-22) > 20 June - 26 June > QUIZ-2

**Started on** Saturday, 18 June 2022, 11:05 AM

**State** Finished

**Completed on** Saturday, 18 June 2022, 11:17 AM

**Time taken** 11 mins 38 secs

**Marks** 11.00/14.00

**Grade** 11.79 out of 15.00 (79%)

### Question 1

Complete

Mark 1.00 out of

1.00

A mod-12 counter must have: [2]

Select one:

- ☒ a. 4 flip flops
- ☐ b. 5 flip flops
- ☐ c. 10 flip flops
- ☐ d. 2 flip flops

The correct answer is: 4 flip flops


## Question 2

Complete

Mark 0.00 out of

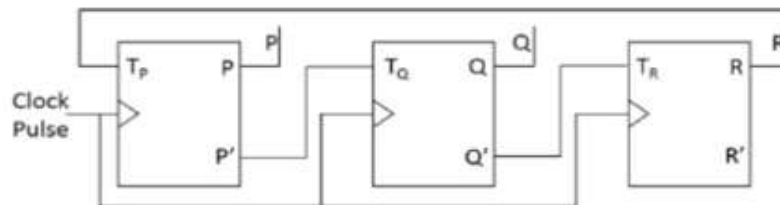2.00

Consider a 3-bit counter, designed using T flip-flops, as shown below:



Assuming the initial state of the counter given by PQR as 000, what are the next three states?

Select one:

- ☐ a. 011, 101, 111
- ☐ b. 001, 010, 000
- ☐ c. 011, 101, 000
- ☒ d. 001, 010, 111

The correct answer is: 011, 101, 000

## Question 3

Complete

Mark 1.00 out of

1.00

If the input to a T flip-flop is a 264 MHz signal, the final output of three T flip-flop in a series is

Select one:

- ☐ a. 30 MHz
- ☐ b. 12.5 MHz
- ☐ c. 520 MHz
- ☒ d. 33 MHz

The correct answer is: 33 MHz

**Question 4**

Complete

Mark 1.00 out of

1.00

Five T flip-flops are connected to form a counter. The maximum states possible for the counter?

Select one:

- ☐ a. 16
- ☐ b. 40
- ☒ c. 32
- ☐ d. 64

The correct answer is: 32

**Question 5**

Complete

Mark 1.00 out of

1.00

Consider a 4-bit johnson counter with an initial value of 0000. The counting sequence of this counter is.

Select one:

- ☐ a. 0, 1, 3, 5, 7, 9, 11, 13, 15, 0
- ☐ b. 0, 1, 3, 7, 15, 14, 12, 8, 0
- ☐ c. 0, 2, 4, 6, 8, 10, 12, 14, 0
- ☒ d. 0, 8, 12, 14, 15, 7, 3, 1, 0

The correct answer is: 0, 8, 12, 14, 15, 7, 3, 1, 0

**Question 6**

Complete

Mark 0.00 out of

1.00

A 10-bit counter is used to count from 0, 1, 2,...,n. The value of n is \_\_\_\_\_?

Select one:

- ☐ a. 255
- ☒ b. 511
- ☐ c. 1023
- ☐ d. 2047

The correct answer is: 1023


**Question 7**

Complete

Mark 2.00 out of

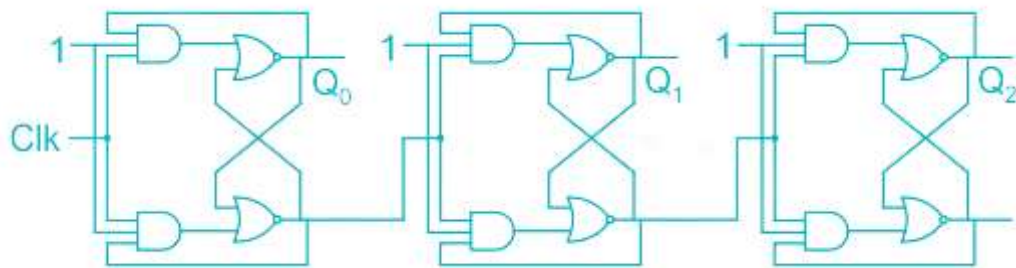2.00

The current state of  $Q_2Q_1Q_0 = 100$  for the circuit below. The next-to-next state will be:



Select one:

- ☒ a. 101
- ☐ b. 011
- ☐ c. 010
- ☐ d. 100

The correct answer is: 101

**Question 8**

Complete

Mark 1.00 out of

1.00

In which counter the output of the last flip-flop is connected to the input of the first flip-flop?

Select one:

- ☐ a. BCD Counter
- ☐ b. Parallel Counter
- ☒ c. Ring Counter
- ☐ d. Ripple Counter

The correct answer is: Ring Counter

**Question 9**

Complete

Mark 1.00 out of

1.00

A minimum number of D ff needed to design a mod-258 counter is

Select one:

- ☒ a. 9
- ☐ b. 8
- ☐ c. 258
- ☐ d. 512

The correct answer is: 9

**Question 10**

Complete

Mark 1.00 out of

1.00

When two asynchronous active low inputs PRESET and CLEAR are applied to a J-K flip-flop the output will be \_\_\_\_\_?

Select one:

- ☐ a. Previous state
- ☒ b. Undefined
- ☐ c. 0
- ☐ d. 1

The correct answer is: Undefined

**Question 11**

Complete

Mark 1.00 out of

1.00

Race around condition is occurs in:

Select one:

- ☐ a. Multiplexer
- ☐ b. Sequential circuits
- ☒ c. Sequential circuits with level triggering
- ☐ d. Encoder

The correct answer is: Sequential circuits with level triggering

**Question 12**

Complete

Mark 1.00 out of

1.00

In a SR flip-flop, if  $R=S'$ , then it acts as a:

Select one:

- ☐ a. RS flip-flop
- ☐ b. T flip-flop
- ☐ c. JK flip-flop
- ☒ d. D flip-flop

The correct answer is: D flip-flop