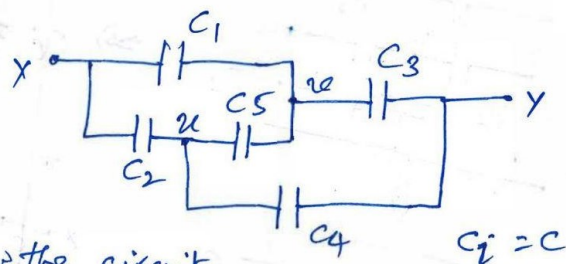


# CSET102L


## Tutorial Sheet - 7 (Solutions)

1)  
Fig. 4




Re draw the circuit

$$C_i = C$$

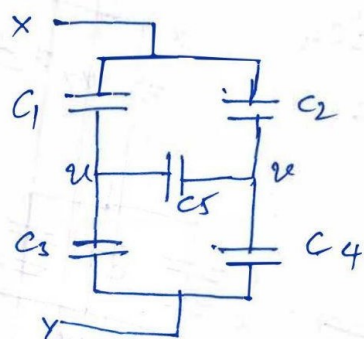


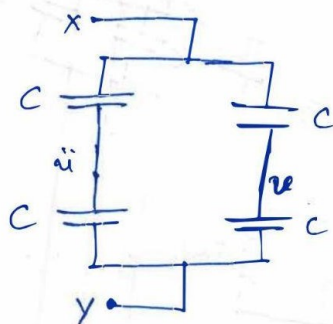$\therefore C_i = C$ ,  
Capacitors between  
u and v act like  
a open. Thus,  
re-draw the  
circuit,




$$\Rightarrow C_{xy} = C$$

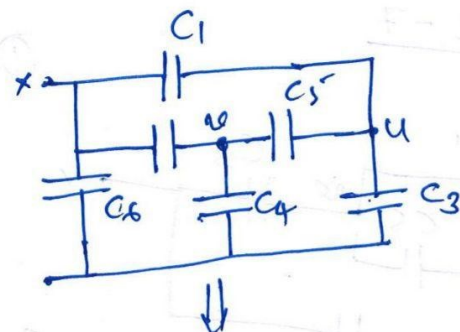Note: Fig. 8 is similar except one more capacitor  
in parallel





$$\Rightarrow C_i = C$$

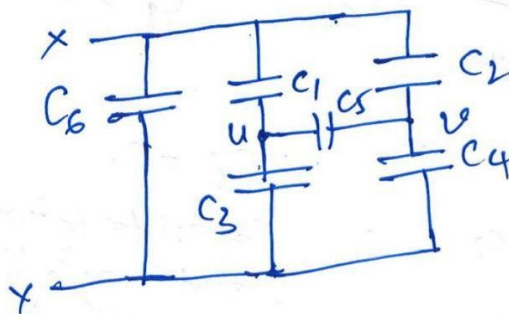


$$\Rightarrow C_{xy} = \frac{2C}{3}$$


Fig. 5

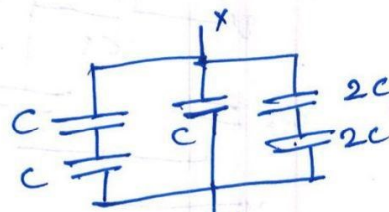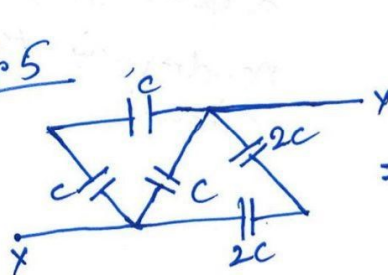

$$C_{eq} = 2.5C$$

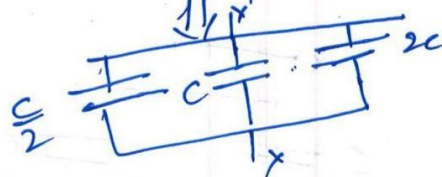

3

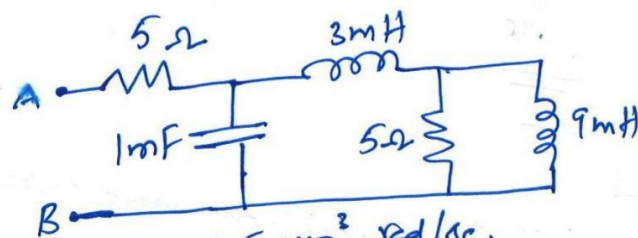

$$\omega = 2.5 \times 10^3 \text{ rad/sec.}$$

$$X_{1mF} = -\frac{j}{\omega C} = -j0.4 \Omega$$

$$X_{3mH} = j\omega L = j7.5 \Omega$$

$$X_{9mH} = j\omega L = j22.5 \Omega$$

$$5 \parallel X_{q_{mH}} = \frac{5 \times j22.5}{5 + j22.5} = \frac{j112.5 (5 - j22.5)}{(5 + j22.5)(5 - j22.5)}$$

$$= \frac{562.5j + 2531.25}{(5)^2 + (22.5)^2} = 4.76 + j1.05$$

$$(5 \parallel X_{q_{mH}}) + X_{3mH} = 4.76 + j1.05 + j7.5$$

$$= 4.76 + j8.55$$

$$X_{inf} \parallel [(5 \parallel X_{q_{mH}}) + X_{3mH}] =$$

$$= \frac{(4.76 + j8.55)(-j0.4)}{(4.76 + j8.55 - j0.4)}$$

$$= \frac{3.42 - j1.904}{(4.76 + j8.15)}$$

writing in  $|z| \angle \theta$  or  $r \angle \theta$  form,

$$\frac{3.42 - j1.904}{4.76 + j8.15} = \frac{3.91 \angle -29.1^\circ}{9.438 \angle 59.71^\circ} \quad \theta = \tan^{-1}(b/a) \quad r = \sqrt{a^2 + b^2}$$


$$X = \frac{3.91 \angle -29.1^\circ}{9.438 \angle 59.71^\circ} = 0.414 \angle -88.81^\circ$$

$$= -0.414 + j0.014$$

$$Z = 5 \Omega + X = 4.586 + j0.014$$

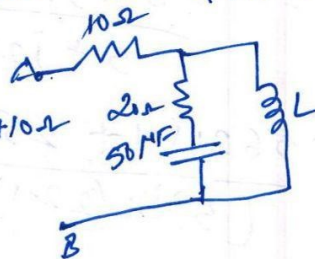4) Given  $Z_{AB} = 25 + j10 \Omega$   $\omega = 4 \times 10^3 \text{ rad/sec.}$

$$Z_{AB} = [j\omega L \parallel (20 - \frac{j}{\omega C})] + 10 \Omega$$



$$25 + j10 = 10 + j\omega L$$

$$\omega C =$$

$$20 - \frac{j}{\omega C} = 20 - j5$$

$$j\omega L \parallel (20 - j5) = \frac{j\omega L (20 - j5)}{(20 - j5 + j\omega L)}$$

$$25 + j10 - 10 = \frac{j20\omega L + 5\omega L}{(20 + j(\omega L - 5))}$$

$$(15 + j10)[20 + j(\omega L - 5)] = 5\omega L + j20\omega L$$

Equating real parts

$$300 - 10\omega L + 50 = 5\omega L \Rightarrow L = \underline{5.83 \text{ mH}}$$

Equating imaginary parts,


$$200j - 75j + j15\omega L = 20\omega L$$

$$125 = 5\omega L \Rightarrow L = \underline{6.25 \text{ mH}}$$

So two inductance values are possible.



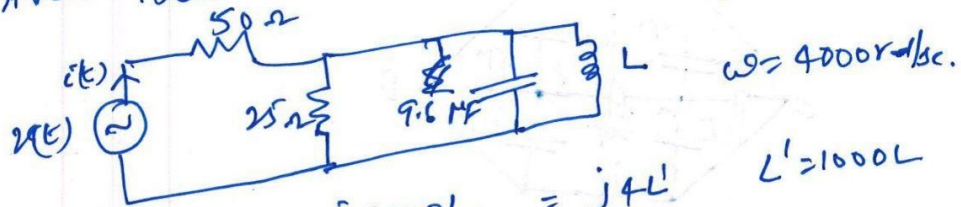3) Given that  $v(t)$  and  $i'(t)$  are in phase



$$X_L = j\omega L = j4000L = j4L' \quad L' = 1000L$$

$$X_C = \frac{-j}{\omega C} = -26.04j$$

$$Z_{eq} = 50 + (X_L \parallel X_C \parallel 25)$$

for phase to be zero, imaginary part needs to be zero.

$$X_L \parallel X_C \parallel 25 = \frac{X_C X_L * 25}{X_C X_L + X_C 25 + X_L 25}$$

$$\frac{2604 L'}{104.16 L' + j100 L' - 651j} + 50$$

$$= \frac{2604 L' (104.16 L' - j(100 L' - 651)) + 50}{(104.16 L')^2 + (100 L' - 651)^2}$$


Equating imaginary parts to zero,

$$104.16 L' - 100 L' - 651 = 0$$

$$L' = \frac{651}{100} = 6.51 \text{ mH}$$

$$L' = 1000L \therefore L = \underline{6.51 \text{ mH}}$$


b)

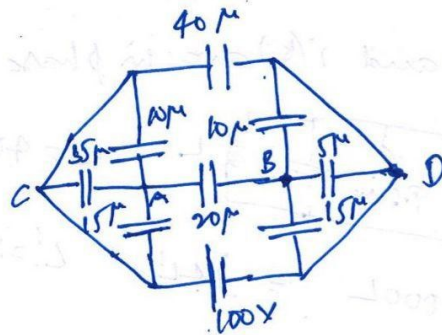

$$10\mu \parallel 35\mu \parallel 15\mu = 60\mu F$$

$$5\mu \parallel 15\mu \parallel 10\mu = 30\mu F$$

re-drawing circuit,

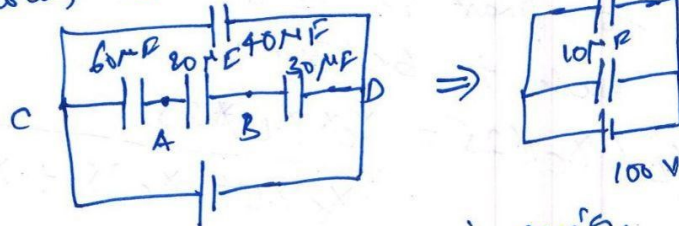

As  $60\mu F, 20\mu F, 30\mu F$  are in series,

$$C_s = \left[ \frac{1}{60} + \frac{1}{20} + \frac{1}{30} \right]^{-1} = 10\mu F$$

$$10\mu F \parallel 40\mu F = 30\mu F$$

$$Q = C_s V = 30 \times 10^{-6} \times 100 = 3000\mu C$$


Charge in  $10\mu F$  capacitance is  
 $100 \times 10\mu F = 1000\mu C$

So charge on  $20\mu F$  capacitance is  
 $1000\mu C$


So voltage across  $20\mu F$  capacitance is

$$V = \frac{Q}{C} = 50V$$

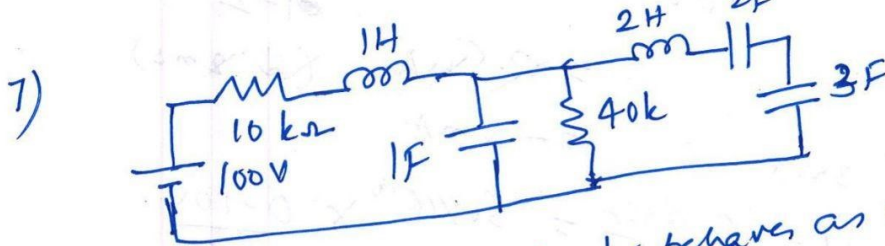So energy stored is  $\frac{1}{2} CV^2 = \frac{0.025W}{2F}$



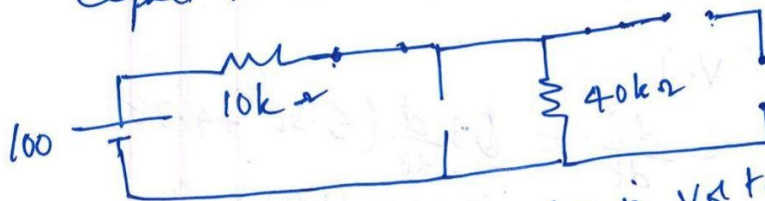In steady state, inductor behaves as a short, capacitor as a open. Redrawing the circuit




So voltage across  $40k\Omega$  is voltage across  $2F, 3F$  capacitors combined.

$$V_{40k} = \frac{100 \times 40}{10 + 40} = 80V$$


$$V_{2F} = \frac{80}{C_2} \left/ \left( \frac{1}{C_2} + \frac{1}{C_3} \right) \right. = \frac{80 \times 3}{5} = 48V$$

8

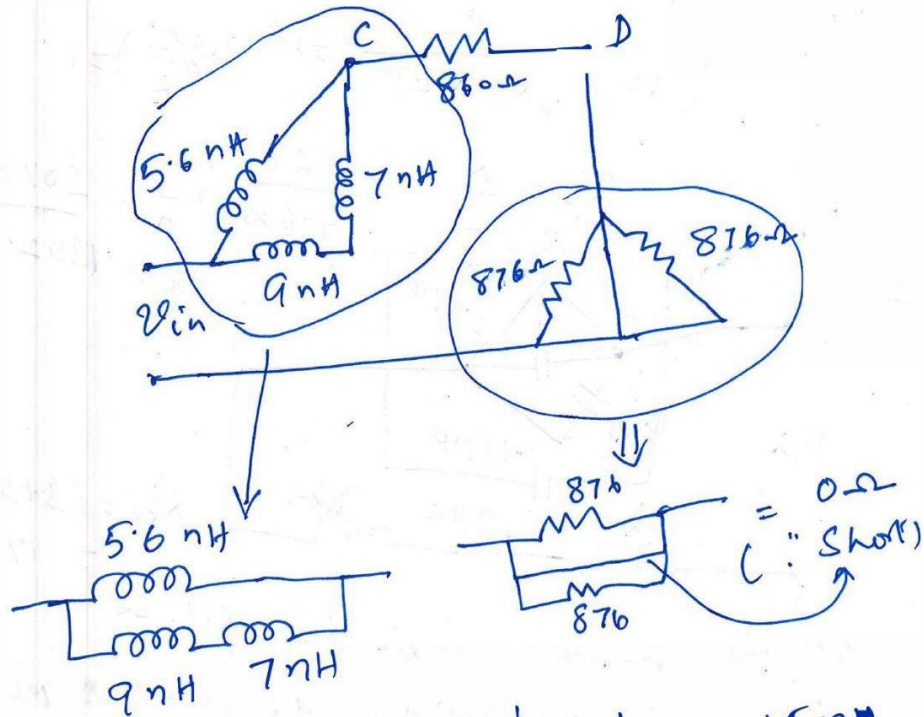

$$\frac{1}{L_{eq}} = \frac{1}{(9 \text{ nH} + 7 \text{ nH})} + \frac{1}{(5.6 \text{ nH})} \Rightarrow L_{eq} = 4.15 \text{ nH}$$

Re-drawing the circuit

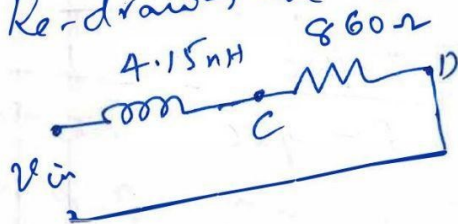

$$H(\omega) = \frac{V_R}{V_R + V_L}$$

$$= \frac{R}{R + j\omega L}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{(1 + \omega^2 \cdot 2.38 \times 10^{-22})^{1/2}}$$

at  $\omega = 0$ ,  $|H(\omega)| = 1$   
 at  $\omega \rightarrow \infty$ ,  $|H(\omega)| = 0$  } Thus a low-pass filter




when  $|H(\omega)| = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}} = \frac{R}{\sqrt{R^2 + (\omega L)^2}} \Rightarrow \omega \left( \frac{L}{R} \right) = 1$$

$$\omega_c = \frac{R}{L} = \frac{860}{4.6 \times 10^{-9}} \frac{1}{s} = 207.3 \text{ GHz}$$

$$f_c = 32.98 \text{ GHz}$$

9

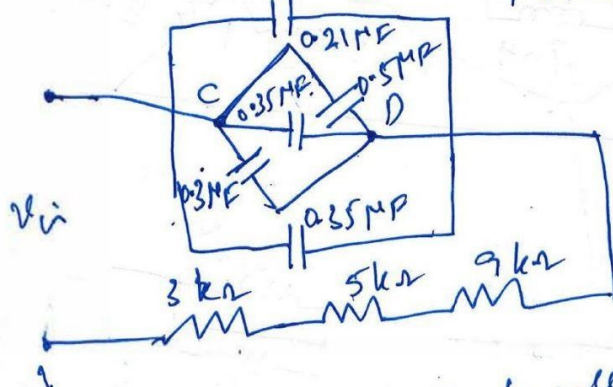


$$R_{eq} = (3 + 5 + 9) \text{ k}\Omega = 17 \text{ k}\Omega$$

All the capacitors are in parallel. so

$$C_{eq} = (0.21 + 0.5 + 0.35 + 0.35) \mu\text{F} = 1.71 \mu\text{F}$$

Re-drawing the circuit

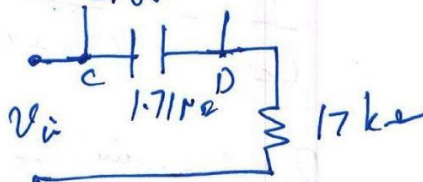

$$H(\omega) = \frac{V_C}{V_R + V_C} = \frac{-j/\omega C}{R - j/\omega C} = \frac{1}{1 + j\omega RC}$$


$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \quad \text{when } \omega = 0 \quad |H(\omega)| = 1$$

Low pass filter  $\Leftrightarrow \begin{cases} |H(\omega)| = 1 \\ |H(\omega)| = 0 \text{ for } \omega = \infty \end{cases}$

$$|H(\omega)| = \frac{1}{\sqrt{2}} \Rightarrow \omega_c RC = 1 \quad f_c = \frac{1}{2\pi RC}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (0.029)^2 \omega^2}} \quad f_c = 5.47 \text{ Hz}$$


10

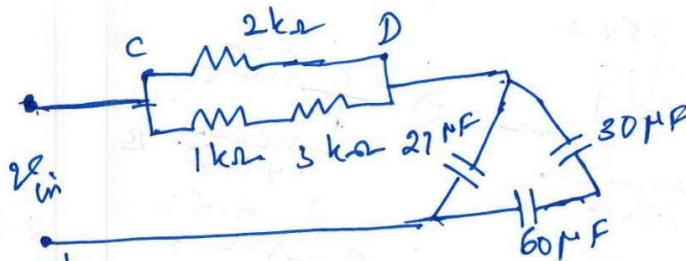

$$R_{eq} = \frac{1}{2k} + \frac{1}{(1k+3k)} \Rightarrow R_{eq} = \frac{4}{3} k\Omega$$

$$C_{eq} = 27nF + \frac{1}{\left(\frac{1}{60n} + \frac{1}{30n}\right)} = (27+20)nF = 47nF$$

Equivalent circuit: 47nF

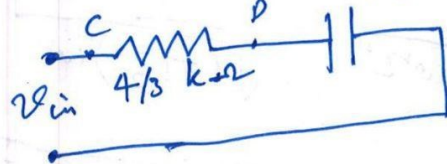


$$H(\omega) = \frac{V_R}{V_R + V_C}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{1}{\sqrt{1 + \frac{1}{(\omega RC)^2}}} = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$


$$\left. \begin{array}{l} \omega \rightarrow 0 \Rightarrow H(\omega) \rightarrow 0 \\ \omega \rightarrow \infty \Rightarrow H(\omega) \rightarrow 1 \end{array} \right\} \rightarrow \text{High pass filter}$$

$$|H(\omega)| = \frac{0.063\omega}{\sqrt{1 + 4 \times 10^3 \omega^2}} \quad f_c = \frac{1}{2\pi RC} = 2.54 \text{ kHz}$$


11

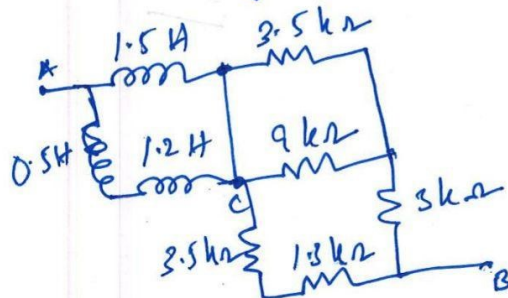
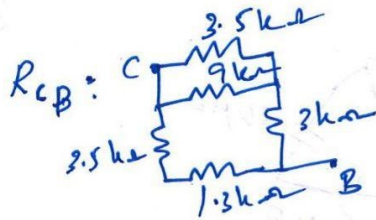
$$L_{eq} = \frac{1}{\frac{1}{1.5} + \frac{1}{(1.2+0.5)}} \Rightarrow L_{eq} = 0.8H$$



$\Rightarrow$

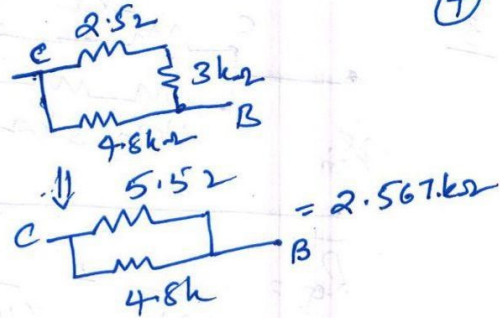

Equivalent circuit:  $A \xrightarrow{0.8H} C \xrightarrow{2.567k\Omega} B$

$$H(\omega) = \frac{V_R}{V_L + V_C} = \frac{R}{j\omega L + R}$$

$$|H(\omega)| = \frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{1 + \left(\frac{L}{R}\right)^2 \omega^2}}$$

$$= \frac{1}{\sqrt{1 + 0.097 \omega^2 \times 10^{-6}}}$$

$\omega \rightarrow 0 \quad |H(\omega)| \rightarrow 1$   
 $\omega \rightarrow \infty \quad |H(\omega)| \rightarrow 0$  }  $\Rightarrow$  low pass filter

$f_c: |H(\omega)| = \frac{1}{\sqrt{2}} \Rightarrow \frac{1}{2} = \frac{1}{1 + 0.097 \omega^2 \times 10^{-6}}$

$$\omega_c = \frac{1}{\sqrt{0.97}} \quad f_c = \frac{1}{2\pi \times \sqrt{0.97} \times 10^{-6}} = 510 \text{ Hz}$$

