

DO NOT WRITE ANYTHING ON QUESTION PAPER EXCEPT YOUR NAME, DEPARTMENT AND ENROLMENT No.

Name of Student ----- Enrolment No. -----

Department / School -----

**BENNETT UNIVERSITY, GREATER NOIDA**

**Supplementary Examination, Fall SEMESTER 2019-20**

COURSE CODE: EECE105L

MAX. DURATION: **3 Hours**

COURSE NAME: Fundamentals of Electrical and Electronics Engg.

MAX. MARKS: **100**

**Note : Attempt all the questions. Each question carries 10 marks.**

**Q.1** For the circuit shown in Fig. 1, determine current through the resistors, voltage across the resistors and their power rating.

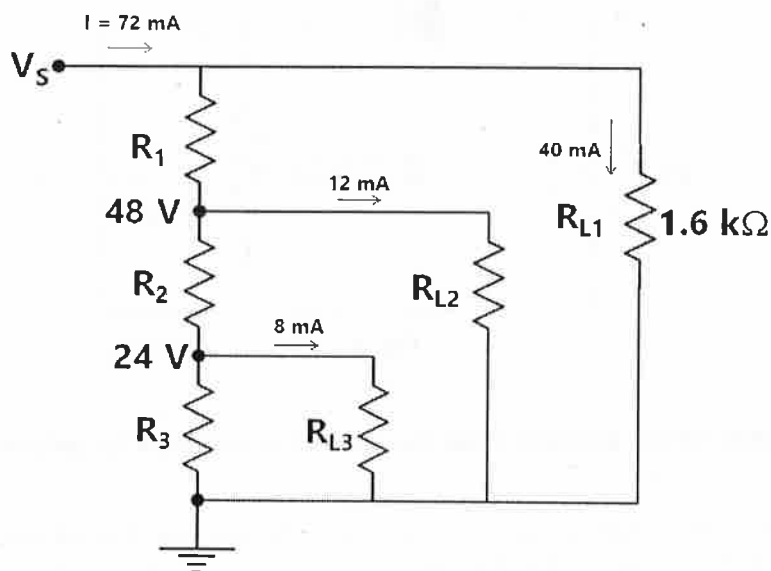


Fig. 1

**Q.2 (a)** With the help of proper circuit diagram, explain the working principle of bridge type full wave rectifier.

**(b)** Using Source Transformation method, find the voltage  $V_s$  and current through 12 V source in Fig. 2. [5+5]

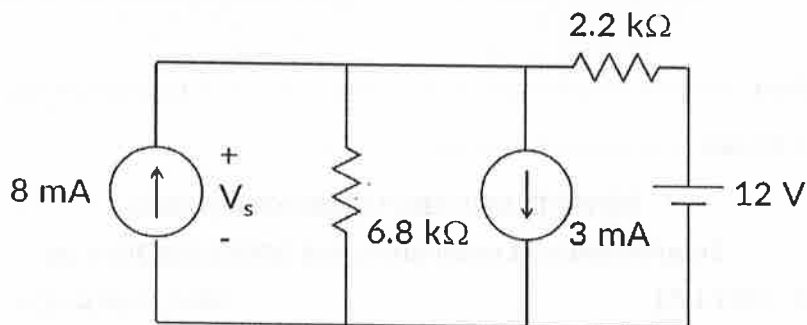


Fig. 2

**Q.3 (a)** Prove the Maximum Power Transfer Theorem theoretically.

**(b)** Assume a sinusoidal waveform with an amplitude of 10 V and 60 Hz is applied to the circuit shown in Fig. 3. Draw the output waveform across the resistor and diode by assuming the diode is (i) ideal (ii) non-ideal. [5+5]

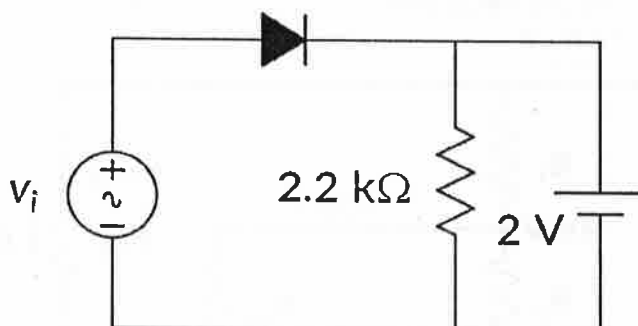


Fig. 3

**Q.4 (a)** With proper circuit diagram show the conditions required for balanced Wheatstone bridge.

**(b)** For the diode circuit shown in Fig. 4,  $D_1$  and  $D_2$  are silicon diodes having saturation currents of 5 nA and 10 nA respectively, at 300 K. Given that both the diodes are forward biased. Find the values of  $R$  for which the current is 15 mA. [5+5]

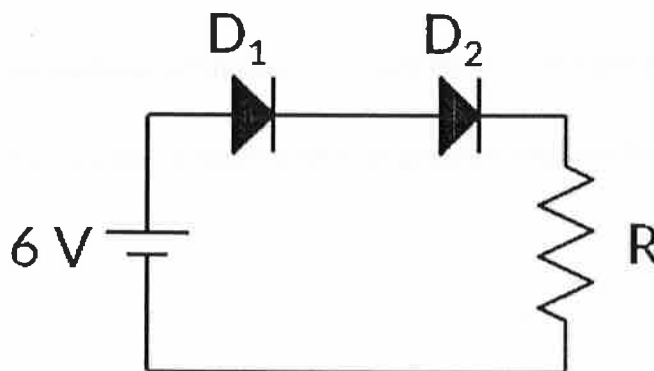


Fig. 4

**Q.5 (a)** For the given Boolean expression prove that  $AB + \bar{A}C + BC = AB + \bar{A}C$

**(b)** For the circuits shown in Fig. 5, find the equivalent resistance  $R_T$  between nodes A and B. Assume that each resistor has value of  $1\text{ k}\Omega$  resistance. [5+5]

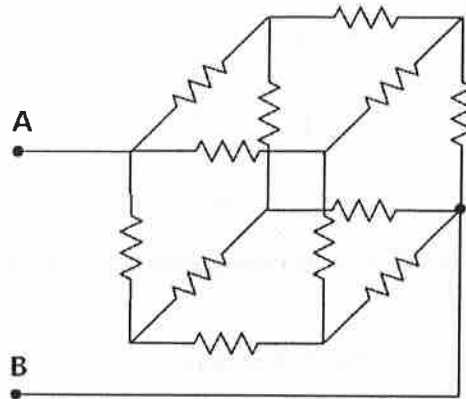


Fig. 5

**Q.6 (a)** Draw the circuit diagram of High Pass RC Filter. Derive the transfer function and cut-off frequency.

**(b)** In Fig. 6, draw the equivalent circuits in positive and negative halves. Also draw the output waveform ( $v_{out}$ ) taken across  $R_L$ . Consider that the diodes are ideal. [5+5]

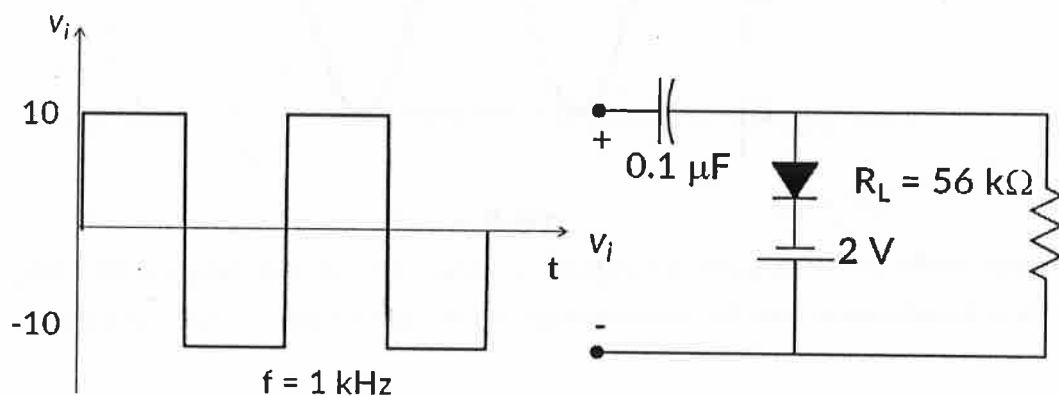


Fig. 6

**Q.7 (a)** Using superposition principle (superposition theorem) in the circuit shown in Fig. 7, find the current flowing through  $2\text{ }\Omega$  resistor.

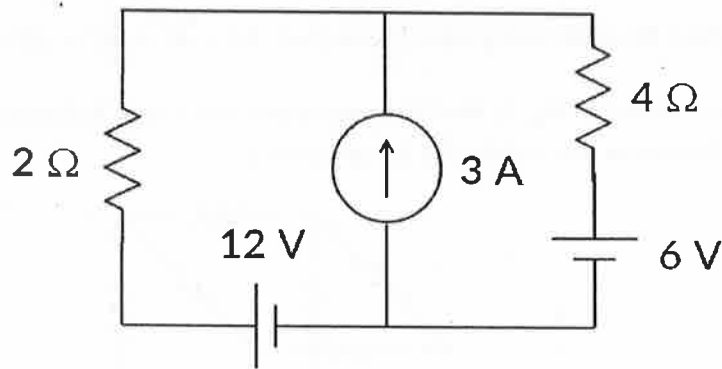


Fig. 7

(b) Convert  $AB + \bar{A}C + B + A\bar{B}C$  into Standard Sum-of-Product (SOP) form. [5+5]

Q.8 Consider the signals shown in Fig. 8. Evaluate:

(a) Peak value, peak amplitude, peak to peak value

(b) Over one period, find average value and RMS value [5+5]

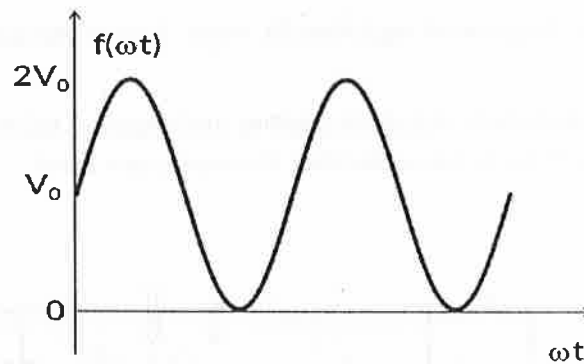


Fig. 8

Q.9 (a) Draw the circuit diagram of a positive clamper and explain its working Principle.

(b) Using Nodal analysis, find the current through and voltages across 5 Ω resistor in Fig 9. [5+5]

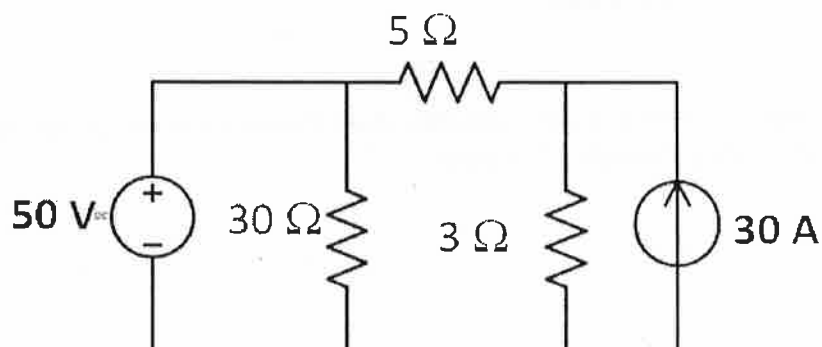


Fig. 9

**Q.10** Consider the circuit shown in Fig. 10. Given that,  $V_{in} = 40\text{ V}$ ,  $R = 50\ \Omega$ ,  $R_L = 100\ \Omega$  and  $V_Z = 20\text{ V}$ . Answer the following questions.

- i) Compute the voltage drop across the load resistance  $R_L$ ?
- ii) Calculate the current through the load resistor  $R_L$ .
- iii) Calculate the current through  $R$ .
- iv) What is the current through the Zener diode?
- v) What is the power consumed by Zener diode?

[2+2+2+2+2]

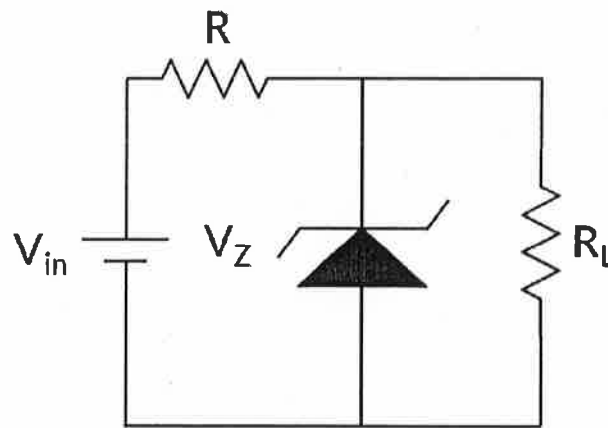


Fig. 10

