

Question 1

Correct


Mark 2.00 out of

2.00



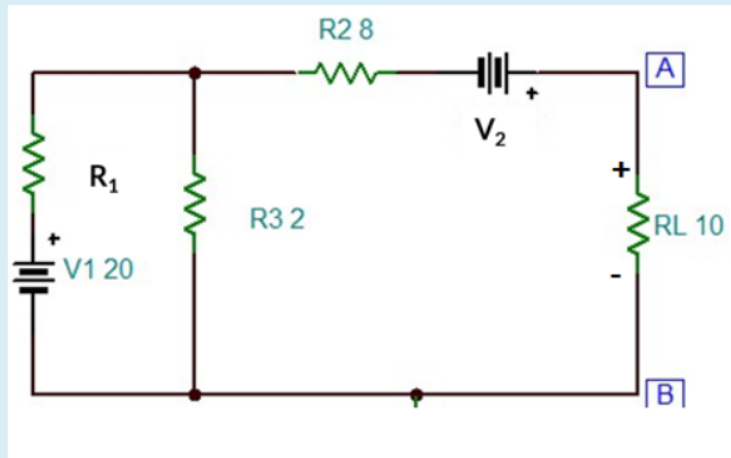question

Find the voltage (in Volt) across the resistor R_L for the circuit shown below when $R_1=6\ \Omega$ and $V_2=13\text{ V}$. (All resistances are in Ω)



Answer: 9.23



The correct answer is: 9.231

Question 2

Correct


Mark 1.50 out of

1.50



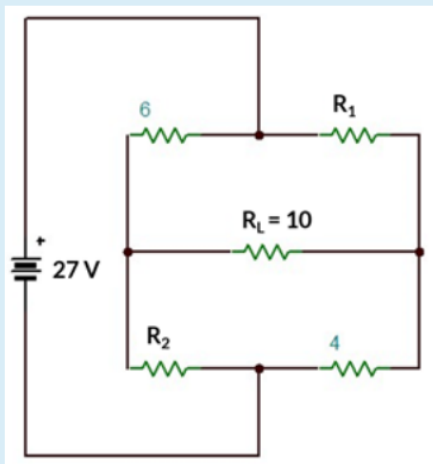question

Find the Thevenin's equivalent resistance (R_{th} in Ω) for the circuit shown in Figure below when $R_1=12.9 \Omega$ and $R_2=18.8 \Omega$. (All resistances are in Ω)



Select one:


- ☐ 22.80
- ☐ 15.20
- ☒ 7.60 ✓
- ☐ 3.80

Question 3


Incorrect

Mark 0.00 out of

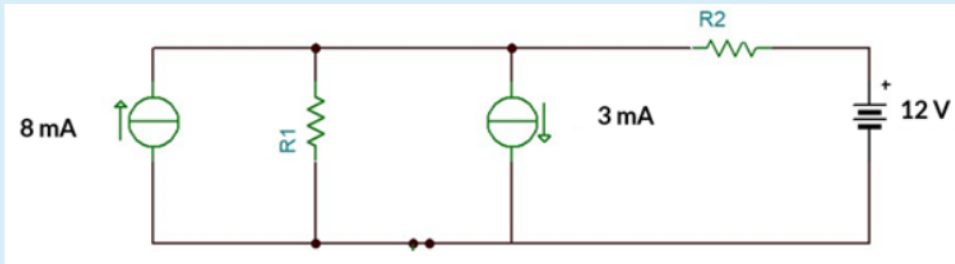1.50

 Flag
question

For the circuit shown below, calculate the voltage (in Volt) across the resistor R_1 when $R_1=9\text{ k}\Omega$ and $R_2=8\text{ k}\Omega$



Answer: 62.5



The correct answer is: 27.529