

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-I Cohort 2020-24
> EECE105L-Odd 2020 > 11 December - 17 December > Quiz 4

Started on Friday, 5 February 2021, 7:05 PM

State Finished

Completed on Friday, 5 February 2021, 7:29 PM

Time taken 24 mins 17 secs

Grade 5.00 out of 5.00 (100%)


Question 1

Correct

Mark 3.00 out of

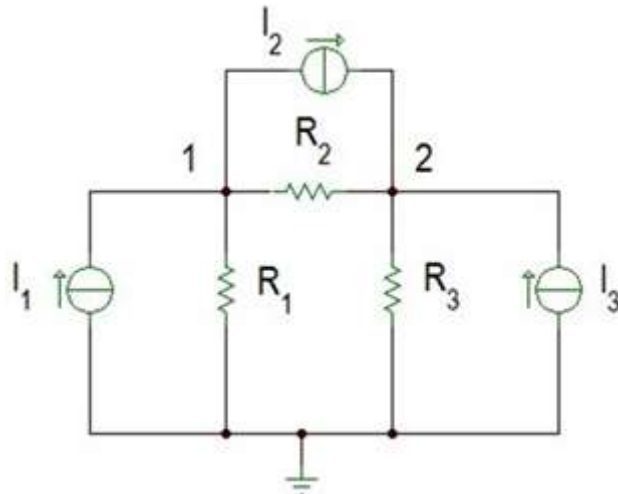3.00

In the following circuit, determine the node voltages V_1 and V_2 (in Volts). Given $I_1=6$ mA, $I_2=9$ mA, $I_3=8$ mA, $R_1=5$ k Ω , $R_2=6$ k Ω , $R_3=5$ k Ω



Select one:

- ☒ V_1 is 16.25 and V_2 is 53.75 ✓
- ☐ V_1 is 50.00 and V_2 is 20.00
- ☐ V_1 is 50.00 and V_2 is 53.75
- ☐ V_1 is 16.25 and V_2 is 20.00

Your answer is correct.

The correct answer is: V_1 is 16.25 and V_2 is 53.75


Question 2

Correct

Mark 2.00 out of

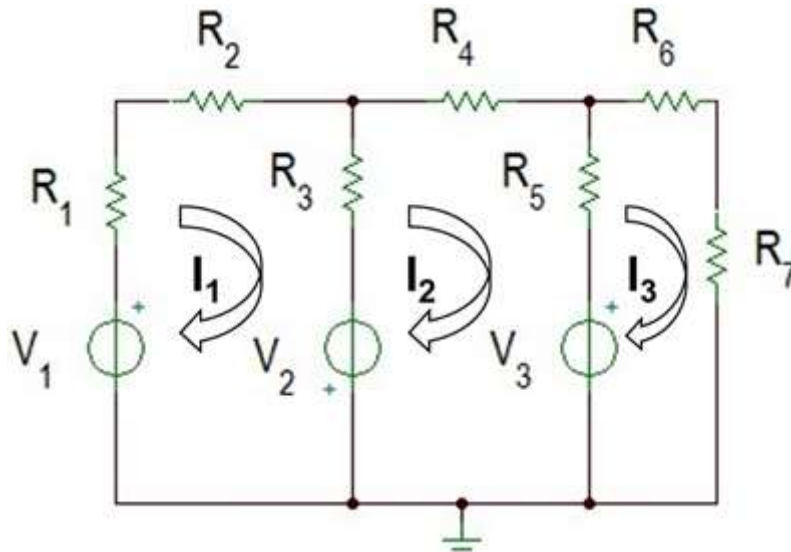2.00

In the following circuit, the mesh currents are I_1 A, I_2 A and I_3 A. Given $V_1 = 7$ V, $V_2 = 5$ V, $V_3 = 5.6$ V, $R_1 = 10\ \Omega$, $R_2 = 8\ \Omega$, $R_3 = 6\ \Omega$, $R_4 = 8\ \Omega$, $R_5 = 10\ \Omega$, $R_6 = 9\ \Omega$ and $R_7 = 7\ \Omega$,



The mesh equations can be represented as following:

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

Which of the option below correctly lists ***a11***, ***a22*** and ***a33***, respectively.

Select one:

- ☐ a_{11} is 24.00 a_{22} is 24.00 and a_{33} is 12.00
- ☐ a_{11} is 12.00 a_{22} is 24.00 and a_{33} is 26.00
- ☐ a_{11} is 24.00 a_{22} is 4.00 and a_{33} is 26.00
- ☒ a_{11} is 24.00 a_{22} is 24.00 and a_{33} is 26.00 ✓

Your answer is correct.

The correct answer is: a_{11} is 24.00 a_{22} is 24.00 and a_{33} is 26.00