

Dashboard > Courses > School Of Engineering & Applied Sciences > B.Tech. > B.Tech. Cohort 2020-2024 > Semester-II Cohort 2020-24  
> ECSE108L-Even2021 (Group - I & Group - II) > 5 June - 11 June > Midterm

**Started on** Monday, 7 June 2021, 1:02 PM

**State** Finished

**Completed on** Monday, 7 June 2021, 1:47 PM

**Time taken** 45 mins 1 sec

**Marks** 24.00/35.00

**Grade** 6.86 out of 10.00 (69%)

### Question 1

Correct

Mark 1.00 out of  
1.00

A half adder has

Select one:

- ☐ a. 3 inputs and 2 outputs
- ☐ b. 2 inputs and 1 outputs
- ☒ c. 2 inputs and 2 outputs ✓
- ☐ d. 2 inputs and 3 outputs

The correct answer is: 2 inputs and 2 outputs

### Question 2

Correct

Mark 1.00 out of  
1.00

Each term in SOP form is called min term

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.




**Question 3**

Correct

Mark 1.50 out of

 1.50

For the MUX shown here, let all D inputs be 0110, both S inputs be HIGH, and the EN input be HIGH. What will be the status of the Y output?



Select one:

- ☐ a. Don't care
- ☒ b. Low ✓
- ☐ c. High Impedance
- ☐ d. HIGH

The correct answer is: Low

**Question 4**

Not answered

Marked out of

2.00

For 4 bit parallel addition, we need minimum \_\_\_\_\_ half adder(s) and \_\_\_\_\_ full adder(s). Assume no previous carry

Select one:

- ☐ a. 2 HA and 2 FA
- ☐ b. 0 HA and 3 FA
- ☐ c. 4 HA and 0 FA
- ☐ d. 1 HA and 3 FA

The correct answer is: 1 HA and 3 FA



### Question 5

Correct

Mark 1.00 out of

1.00

In reference to the truth table of SR latch, how many valid entries are there?

Select one:

- ☒ a. 3 ✓
- ☐ b. 2
- ☐ c. 4
- ☐ d. 0
- ☐ e. 1

The correct answer is: 3


### Question 6

Correct


Mark 2.00 out of

2.00


Match The following

 

XNOR

 

XNOR

 


XOR



XNOR




The correct answer is:

 

→ XNOR,



→ XNOR,

 

→ XOR,



→ XNOR



**Question 7**

Correct

Mark 1.00 out of

1.00

An n variable K-map can have.

Select one:

- ☐ a.  $2 \cdot n$  cell
- ☐ b.  $n$  pow  $n$  cell
- ☒ c.  $2$  pow  $n$  cell ✓
- ☐ d.  $n$  pow  $2$  cell

The correct answer is:  $2$  pow  $n$  cell

**Question 8**

Incorrect

Mark 0.00 out of

1.50

The equivalent minimum expression for the expression  $f(X, Y, Z) = XY + YZ' + XZ'$  is:

Select one:

- ☐ a.  $m_2 + m_4 + m_6 + m_7$
- ☐ b.  $m_0 + m_1 + m_3 + m_5$
- ☒ c.  $m_2 + m_3 + m_4 + m_5$  ✗
- ☐ d.  $m_0 + m_1 + m_6 + m_7$

The correct answer is:  $m_2 + m_4 + m_6 + m_7$



**Question 9**

Correct

Mark 2.00 out of

2.00

In a look-ahead carry generator, the carry generate function  $G_i$  and the carry propagate function  $P_i$  for inputs  $A_i$  and  $B_i$  are given by:

$$P_i = A_i \oplus B_i \text{ and } G_i = A_i B_i$$

The expressions for the sum bit  $S_i$  and the carry bit  $C_{i+1}$  of the look-ahead carry adder are given by:

$$S_i = P_i \oplus C_i \text{ and } C_{i+1} = G_i + P_i C_i, \text{ where } C_0 \text{ is the input carry.}$$

Consider a two-level logic implementation of the look-ahead carry generator. Assume that all  $P_i$  and  $G_i$  are available for the carry generator circuit and you can choose AND and OR gates with **any number of inputs**. The minimum number of AND gates and OR gates needed for carry generator for a 4-bit adder to generate  $C_4, C_3, C_2, C_1$  as its outputs.

Select one:

- ☐ a. 6 AND , 3 OR
- ☐ b. 15 AND , 10 OR
- ☐ c. 6 AND , 4 OR
- ☒ d. 10 AND , 4 OR ✓

The correct answer is: 10 AND , 4 OR

**Question 10**

Incorrect

Mark 0.00 out of

2.00

11001, 1001, and 111001 correspondings to the 2's complement representation of the following set of numbers. Assume the first bit represents the sign

Select one:

- ☐ a. -7, -7 and -7 respectively
- ☐ b. -25, -9 and -57 respectively
- ☒ c. 25, 9 and 57 respectively ✗
- ☐ d. -7, -6 and -7 respectively

The correct answer is: -7, -7 and -7 respectively



**Question 11**

Correct

Mark 1.50 out of

1.50

Latches constructed with NOR and NAND gates tend to remain in latched condition due to which configuration feature?

Select one:

- ☐ a. Synchronous operation
- ☐ b. Gate impedance
- ☒ c. Cross Coupling ✓
- ☐ d. Low Input Voltage

The correct answer is: Cross Coupling

**Question 12**

Correct

Mark 1.50 out of

1.50

What would happen to the output if the Q=0 in S-R flip-flop?

Select one:

- ☒ a. RESET ✓
- ☐ b. Current state
- ☐ c. SET
- ☐ d. Previous State

The correct answer is: RESET

**Question 13**

Correct

Mark 1.00 out of

1.00

A combinational logic circuit does not have feedback from output to input.

Select one:

- ☒ True ✓
- ☐ False

The correct answer is 'True'.



**Question 14**

Correct

Mark 1.50 out of

1.50

What is one of the major issue in the ripple-carry adder?

Select one:

- ☐ a. None of the given
- ☐ b. The interconnections are more complex
- ☒ c. It is slow due to propagation time ✓
- ☐ d. Extra stages are required to a full adder

The correct answer is: It is slow due to propagation time

**Question 15**

Correct

Mark 1.50 out of

1.50

Which Boolean function can be represented by following truth table?

A	B	<u>F(A,B)</u>
0	0	0
0	1	0
1	1	1
1	0	1

Select one:

- ☐ a. A XOR B
- ☐ b. B
- ☒ c. A ✓
- ☐ d. A and B

The correct answer is: A




**Question 16**

Incorrect

Mark 0.00 out of

 1.50

For the MUX shown here, let all D inputs be 1001, both S inputs be HIGH, and the EN input be HIGH. What will be the status of the Y output?



Select one:

- ☒ a. LOW ✖
- ☐ b. Don't care
- ☐ c. High Impedance
- ☐ d. HIGH

The correct answer is: HIGH

**Question 17**

Correct

Mark 1.00 out of

1.00

Which gate will generate the high output when one input is high and other is low?

Select one:

- ☐ a. Only OR gate
- ☐ b. Only NAND Gate
- ☐ c. Only AND GATE
- ☒ d. Both OR and NAND ✔

The correct answer is: Both OR and NAND





**Question 18**

Incorrect

Mark 0.00 out of  
1.50

If in a base number system,  $5+3=12$ , what is the base of the number is?

Select one:

- ☐ a. 6
- ☒ b. 8 ✖
- ☐ c. 4
- ☐ d. 10

The correct answer is: 6

**Question 19**

Correct

Mark 1.00 out of  
1.00

What will be the Boolean expression for the Half adder for input X and Y?

Select one:

- ☐ a. Sum = x AND y ; carry = x OR y
- ☐ b. Sum = x NOR y ; carry = x NOT y
- ☐ c. Sum = x AND y ; carry = x AND y
- ☒ d. Sum = x XOR y ; carry = x AND y ✔

The correct answer is: Sum = x XOR y ; carry = x AND y

**Question 20**

Correct

Mark 1.50 out of  
1.50

Which logic gates can be used to construct a basic S-R flip-flop?

Select one:

- ☐ a. AND or NOR gates
- ☐ b. AND or OR gates
- ☒ c. NOR or NAND gates ✔
- ☐ d. XOR or XNOR gates

The correct answer is: NOR or NAND gates



**Question 21**

Incorrect

Mark 0.00 out of

1.00

In Karnaugh map an octet eliminates \_\_\_\_\_variables.

Select one:

- ☐ a. Two
- ☐ b. None
- ☒ c. one ✖
- ☐ d. Three

The correct answer is: Three

**Question 22**

Correct

Mark 1.00 out of

1.00

Which gate used for even parity check?

Select one:

- ☐ a. NAND
- ☒ b. XOR ✔
- ☐ c. None of the given
- ☐ d. OR
- ☐ e. NOR

The correct answer is: XOR

**Question 23**

Correct

Mark 2.00 out of

2.00

Which of the following logic expressions is incorrect?

Select one:

- ☐ a.  $1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 = 1$
- ☐ b.  $1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 0$
- ☒ c.  $1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 1$  ✔
- ☐ d.  $0 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 1 = 0$

The correct answer is:  $1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 \oplus 1 \oplus 0 = 1$



**Question 24**

Correct

Mark 1.00 out of

1.00

Which mapping is related to a Demultiplexer?

Select one:

- ☐ a. one to one
- ☐ b. None of the mentioned
- ☐ c. many to one
- ☒ d. one to many ✓

The correct answer is: one to many

**Question 25**

Incorrect

Mark 0.00 out of

1.50

A multiplexers is a combinational logic circuit need to perform the operations\_\_\_\_\_

Select one:

- ☐ a. XOR-NAND
- ☐ b. OR-OR
- ☒ c. NOR-OR ✗
- ☐ d. AND-OR

The correct answer is: AND-OR

