



## 1. Shift Registers:

is a type of digital circuit using cascade of flip flop where the output of one flip flop is connected to input of the next.

### Types of Shift Register:

1. Serial in / Serial out

2. Serial in / Parallel out

3. Parallel in / Serial out

4. Universal parallel-in / parallel out

→ data storage

2. Timing diagrams are graphical representation that show timing and sequencing of digital signals in a shift register