

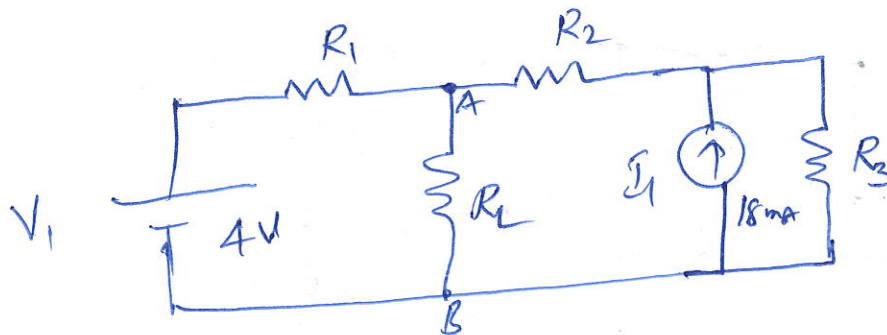


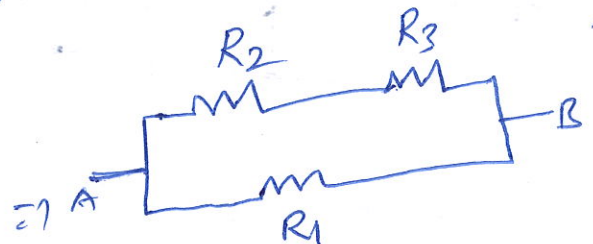- 1) For the circuit shown below, calculate the value of P_{R_L} (in mW) such that the power delivered to the resistor is maximized.



$$\begin{aligned} R_2 &= 7 \text{ k}\Omega \\ R_3 &= 9 \text{ k}\Omega \\ R_L &= 2 \text{ k}\Omega \end{aligned}$$

To find R_{TH} between A and B nodes:

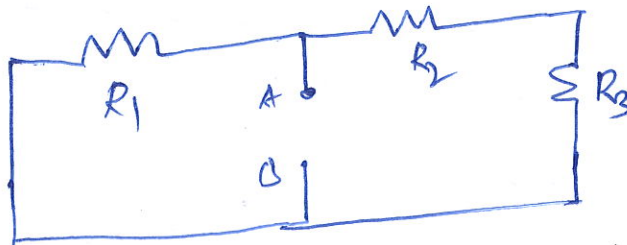


$$R_{TH} = R_1 \parallel (R_2 + R_3)$$

$$R_{TH} = R_L = 2 \text{ k}\Omega = R_1 \parallel (16 \text{ k}\Omega)$$

$$\frac{1}{2} = \frac{1}{R_1} + \frac{1}{16} \quad \frac{1}{R_1} = \frac{1}{2} - \frac{1}{16} = \frac{14}{2 \times 16}$$

$$R_1 = \frac{16}{7} \text{ k}\Omega$$

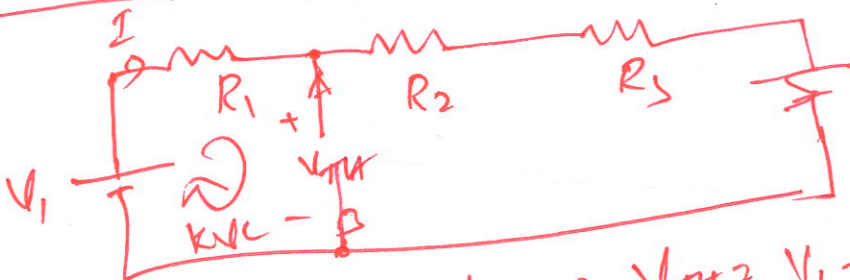To find V_{TH} : Use source transformation.



$$I = \frac{4 - 18 \text{ mA} \times 9 \times 10^3}{\left(\frac{16}{7} + 7 + 9\right) \text{ k}} \quad I \cdot R_3$$

$$\text{KVL} \quad V_1 = I R_1 + V_{TH} \Rightarrow V_{TH} = V_1 - I R_1 = 95 \text{ V} = -8.64 \text{ mA}$$

$$R_L = R_{TH} = 2 \text{ k}\Omega$$

$$P_{R_L} = \frac{V_{TH}^2}{4 R_L} = 70.51 \text{ mW}$$